

ECE 209 — Exam # 1

Estimated time for completion: <1.25 hour
29 September 2016

Rules of the Exam

Rule 1: The examination period begins at 11:00am on Thursday 29 September 2016 and ends at 12:15pm on Thursday 29 September 2016.

Rule 2: There are four problems.

Rule 3: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes and a calculator.

Rule 4: To receive full credit for an answer include the units along with the numerical answer.


Rule 5: Show all work - answers without supporting work will not receive credit.

Answer Key

Name

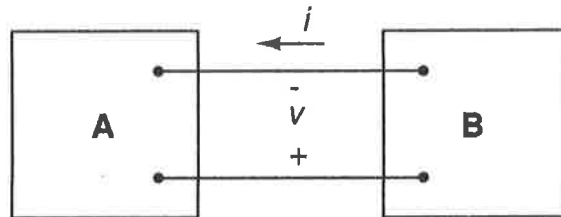Problem 1 (20 points)

Two electric circuits, represented by boxes **A** and **B**, are connected as shown in the figure below. The reference direction for the current i and the reference polarity of the voltage v are also shown.




For each set of values of i and v in the table below, calculate the absolute value of the power associated with circuit **B** and indicate if circuit **B** is generating or absorbing power.

Condition	i	v	Power	Generating or Absorbing
1	10 A	5 V	50W	Absorbing
2	5 A	-24 V	120W	Generating
3	-12 A	24 V	288W	Generating
4	-2.5 A	-1 V	2.5W	Absorbing

Problem 2 (20 points)

Consider the circuit below:

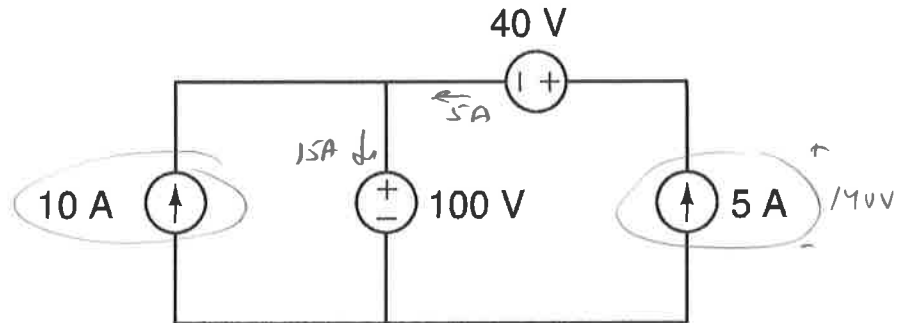




Is the interconnection valid (yes/no)? Yes

If the interconnection is valid, identify the voltage and current sources that generate power by circling them in the figure above.

If the circuit is not valid, explain why:

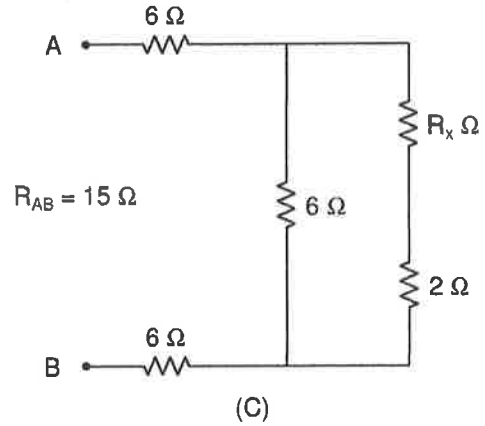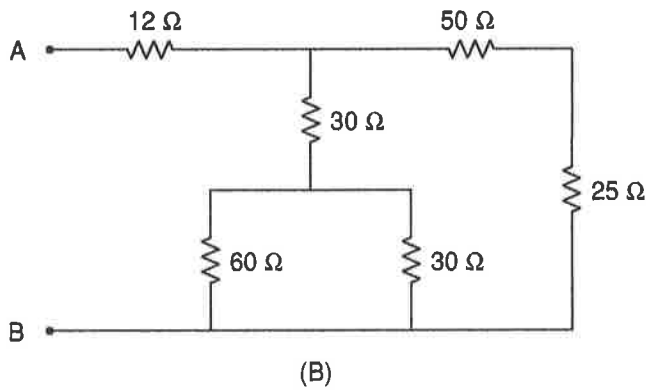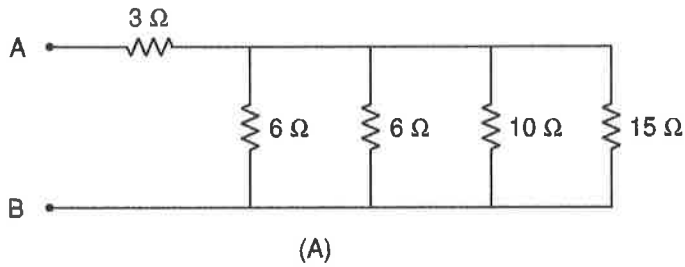Problem 3 (30 points)

Consider the three series and parallel resistor combinations below:



For circuits (A) and (B), calculate R_{ab} , the equivalent resistance between terminals A and B:


R_{ab} for circuit (A): 5 Ω $15 \parallel 10 \parallel 6 \parallel 6 + 3$
 R_{ab} for circuit (B): 42 Ω $75 \parallel 50 + 12$

For circuit (C), calculate the value of R_x that produces an equivalent resistance between terminals A and B of 15Ω .

R_x for circuit (C): 4 Ω

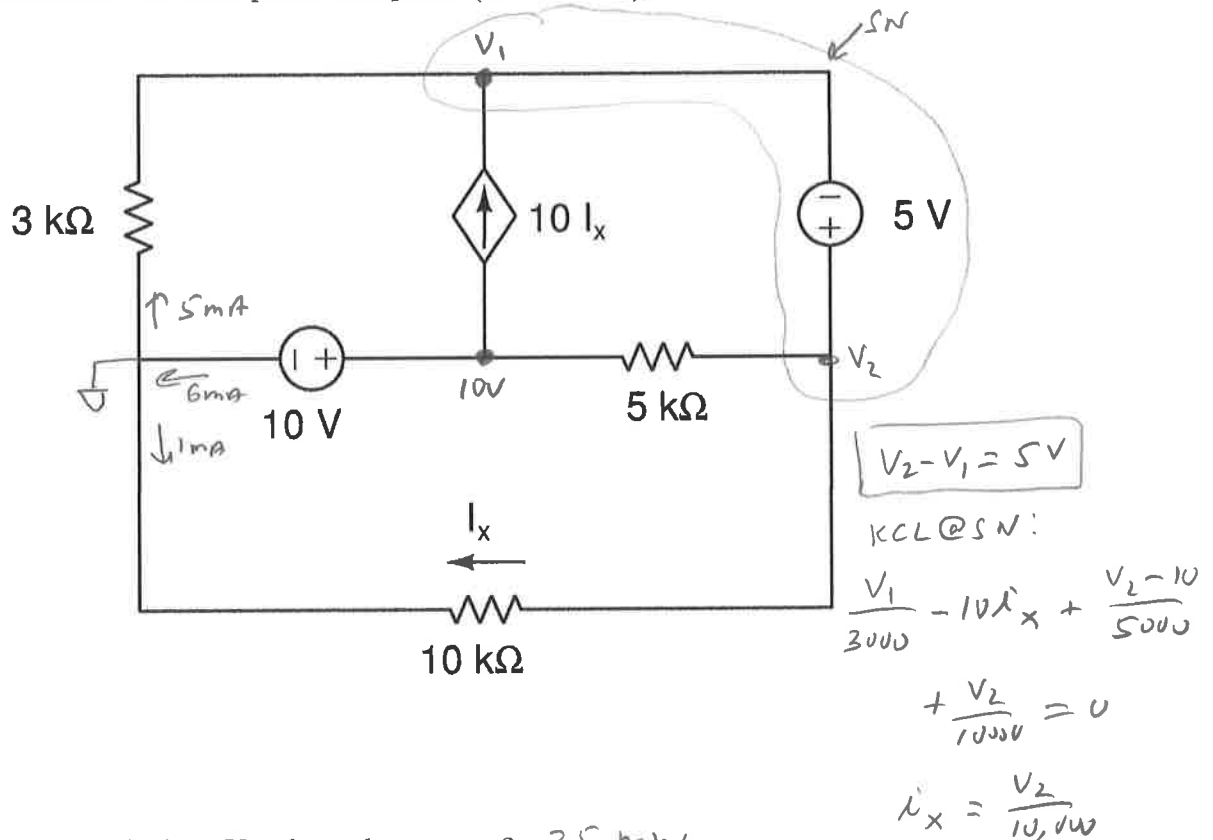Problem 4 (30 points)

In the circuit shown below, calculate the power associated with each circuit component, the total power generated and the total power dissipated (or absorbed).



Power associated with the 5 V independent source? 25 mW

Power associated with the 10 V independent source? 60 mW

Power associated with the $10I_x$ dependent current source? -250 mW

Power associated with the $3k\Omega$ resistor? 75 mW

Power associated with the $5k\Omega$ resistor? 80 mW

Power associated with the $10k\Omega$ resistor? 10 mW

How much power is generated in the circuit? 250 mW


How much power is dissipated or absorbed in the circuit? 250 mW

$I_x = -1 \text{ mA}$

$V_1 = -15 \text{ V}$

$V_2 = -10 \text{ V}$

Problem 4 by mesh

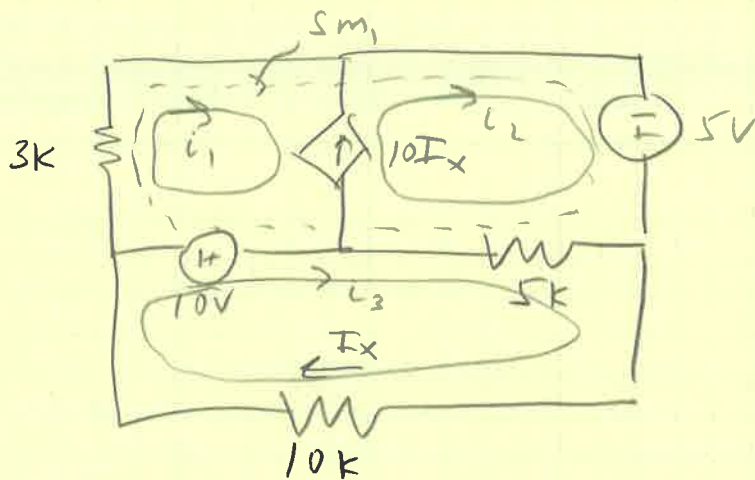

$$I_x = i_3$$

sm: Constraint: $i_2 - i_1 = 10i_3$

KVL $-5 + 5000(i_2 - i_3) + 10 + 3000i_1 = 0$

KVL @ i_3 : $-10 + 5000(i_3 - i_2) + 10,000i_3 = 0$

3 equations; 3 unknowns

$$i_1 = +5 \text{ mA}$$

$$i_2 = -5 \text{ mA}$$

$$i_3 = -1 \text{ mA}$$