

ECE 209 — Exam # 3

Estimated time for completion: <75 minutes
22 November 2016

Rules of the Exam


Rule 1: The examination period begins at 11:00pm on Tuesday 24 November 2015 and ends at 12:15pm on Tuesday 24 November 2015.

Rule 2: There are three problems.

Rule 3: Show all work and state all assumptions. Make sure to include the units along with a numerical answer. Answers without support when needed will not receive credit.

Rule 4: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes. You may use a calculator.


Answer Key _____
Name

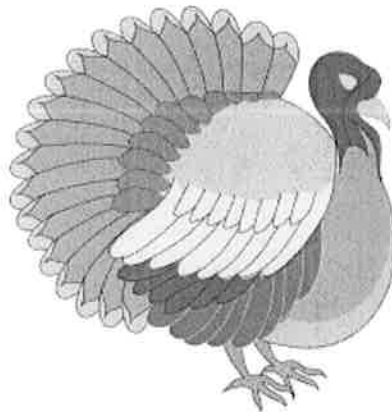

Happy Thanksgiving!

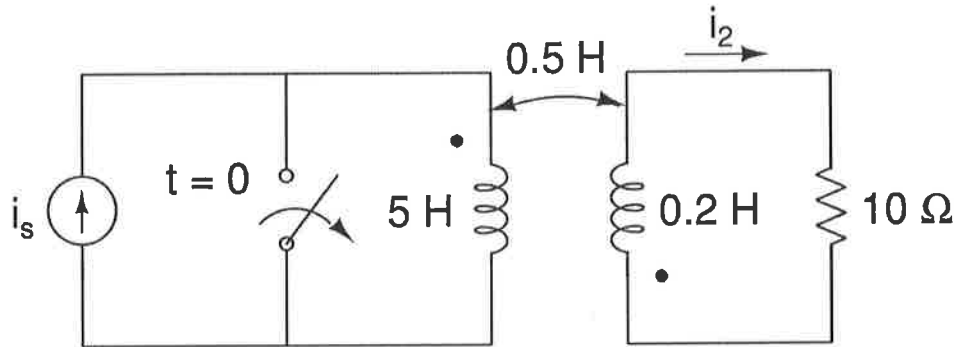Problem 1 (20 points)

In the circuit below, the switch has been closed for a very long time and opens at $t = 0$. There is no energy stored in the circuit at the time the switch opens.



What is $i_2(0^-)$ 0 A


What is $i_2(0^+)$ 0 A

What is the differential equation that describes the behavior of $i_2(t)$ for $t \geq 0$? (Note: you do not need to solve the equation.)

$$10i_2 + 0.2 \frac{di_2}{dt} + 0.5 \frac{di_s}{dt} = 0$$

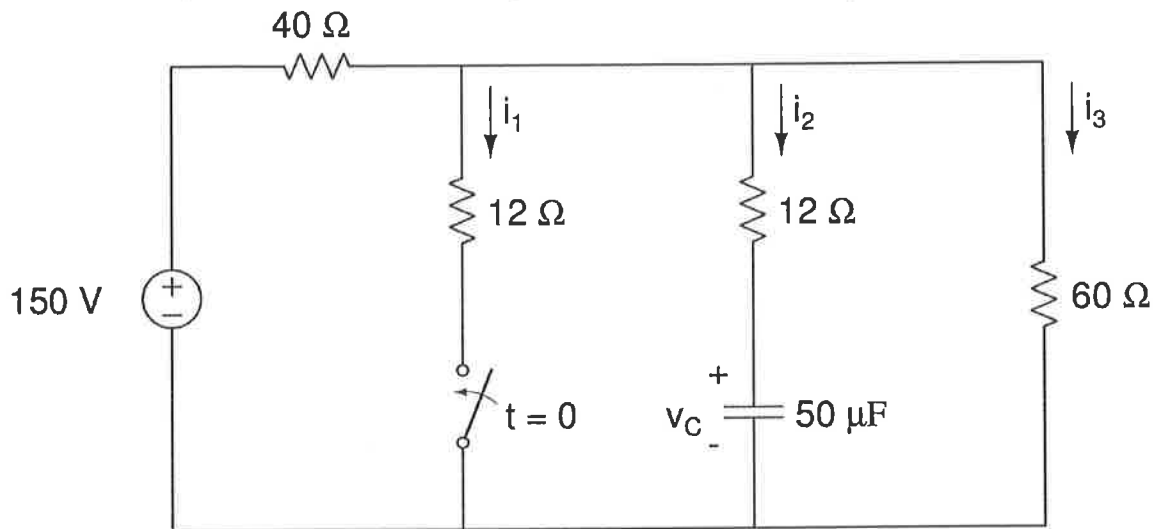Problem 2 (40 points)

In the circuit below, the switch has been open for a very long time and closes at $t = 0$.



R_{Th} seen by capacitor: $60 \parallel 12 \parallel 40 + 12 = 20 \Omega$

What is the time constant of the circuit for $t > 0$? 1ms

See Page 6

Complete the table below:

	$t = 0^-$	$t = 0^+$	$t = 4 \text{ ms}$	$t = \infty$
i_1	0 A	4.5 A	2.54 A	2.5 A
i_2	0 A	-3.0 A	-0.055 A	0 A
i_3	1.5 A	0.9 A	0.507 A	0.5 A
v_C	90 V	90 V	31.1 V	30 V

@ $t = 4 \text{ ms}$

$i_1 = 2.5 + [4.5 - 2.5]e^{-4} = 2.54 \text{ A}$


$i_3(4 \text{ ms}) = 0.5 + [0.9 - 0.5]e^{-4} = 0.507 \text{ A}$

$i_2(4 \text{ ms}) = -3e^{-4} = -0.055 \text{ A}$

$v_C(4 \text{ ms}) = 30 + 60e^{-4} = 31.1 \text{ V}$

Problem 3 (40 points)

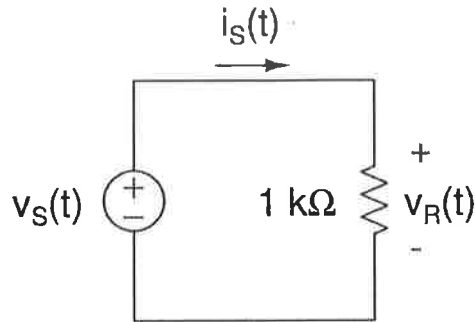Part A. For the circuit below the voltage source $v_s(t) = 150 \cos(2513t - 55^\circ)$ V



What is the peak voltage across the resistor? 150 V

What is $v_s(4\text{ms})$? -141.77 V

What is $i_s(4\text{ms})$? -141.77 mA

What is the frequency of $V_R(t)$ in Hz? 400 Hz

What is the average power dissipated by the resistor? 11.25 W

Part B. What is the Phasor representation of the following time-domain signals?

$v(t) = 120 \cos(360t - 37^\circ)$ mV $120 \angle -37^\circ$ mV



$i(t) = 75 \sin(450t + 40^\circ)$ A $75 \angle -50^\circ$ A

Part C. What is the time-domain representation of the following Phasor signals when the frequency is 3 MHz?

$V = 25 \angle -50^\circ$ V $25 \cos(6\pi \times 10^6 t - 50^\circ)$ V

$I = 0.3 \angle 15^\circ$ A $0.3 \cos(6\pi \times 10^6 t + 15^\circ)$ A

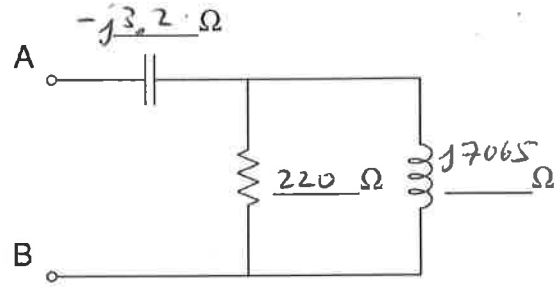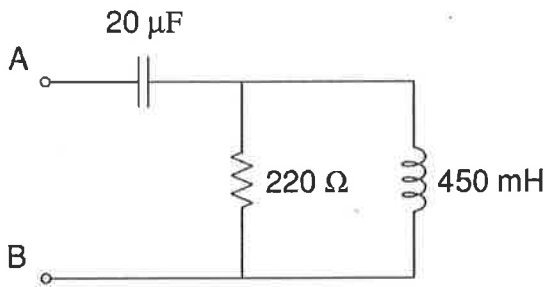Part D. Convert the circuit below on the left to the frequency domain when the frequency is 2.5 kHz.



Frequency Domain

At what radian frequency, ω , is the impedance Z_{AB} purely resistive? 456 rad/s

$$\begin{aligned}
 Z_{AB} &= -\frac{j}{\omega C} + R \parallel j\omega L \\
 &= -\frac{j}{\omega C} + \frac{j\omega LR}{R + j\omega L} \frac{R - j\omega L}{R - j\omega L} \\
 &= -\frac{j}{\omega C} + \frac{j\omega LR^2 + \omega^2 L^2 R}{R^2 + \omega^2 L^2}
 \end{aligned}$$

For Z_{AB} to be purely resistive: $-\frac{j}{\omega C} + \frac{j\omega LR^2}{R^2 + \omega^2 L^2} = 0$

$$\omega^2 L C R^2 - R^2 - \omega^2 L^2 = 0$$


$$\omega^2 (L C R^2 - L^2) = R^2$$

$$\omega^2 = \frac{R^2}{(L C R^2 - L^2)}$$

$$\omega = \frac{R}{\sqrt{L C R^2 - L^2}}$$

Name: _____

@ $t = 0^+$

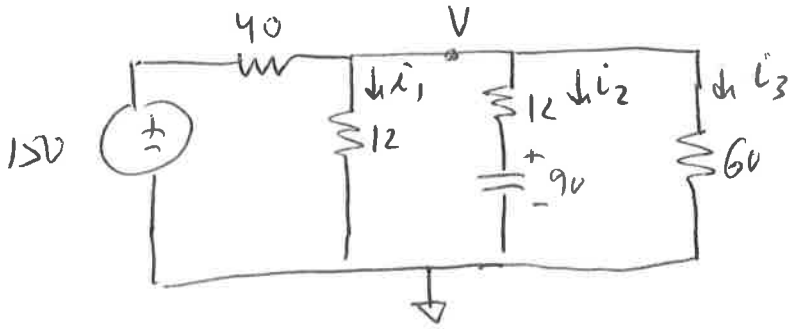

$$\text{KCL @ } V: \frac{V-150}{40} + \frac{V}{12} + \frac{V}{60} + \frac{V-90}{12} = 0$$

$$V = 54 \text{ V}$$

$$i_1 = \frac{V}{12}$$

$$i_2 = \frac{V-90}{12}$$

$$i_3 = \frac{V}{60}$$

Name: _____