

## ECE 209 — Exam # 3

Estimated time for completion: <1.25 hour  
26 November 2019

### Rules of the Exam

**Rule 1:** The examination begins at 9:30am on Tuesday, 26 November 2019, and ends at 10:45pm on Tuesday, 26 November 2019.

**Rule 2:** There are three problems plus one extra credit problem.

**Rule 3:** The exam is closed book and closed notes. You may use an 8.5" x 11" sheet of paper with notes, a ruler, and a calculator.


**Rule 4:** Do not leave the room until you have completed the exam.

**Rule 5:** To receive full credit for an answer include the units along with the numerical answer.

**Rule 6:** Show all work - answers without supporting work will not receive credit.

Answer Key  
\_\_\_\_\_  
Name

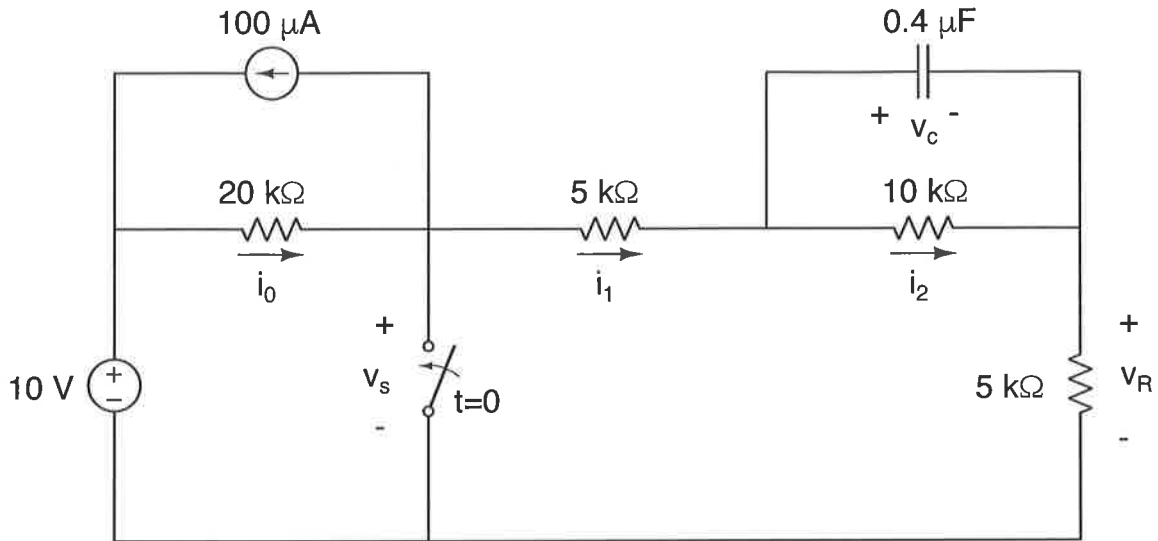**Problem 1** (30 points). In the circuit below, the switch has been open for a very long time, and closes at  $t = 0$ .




Complete the table below:

	$t = 0^-$	$t = 0^+$	$t = \infty$
$i_0$	0.3 mA	0.5 mA	0.5 mA
$i_1$	0.2 mA	-0.2 mA	0V
$i_2$	0.2 mA	0.2 mA	0V
$v_s$	4V	0V	0V
$v_c$	2V	→ 2V	0V
$v_R$	1V	-1V	0V

What is the time constant of the circuit for  $t > 0$ ? 2 ms

For  $t \geq 0^+$

$$V_s = 0$$

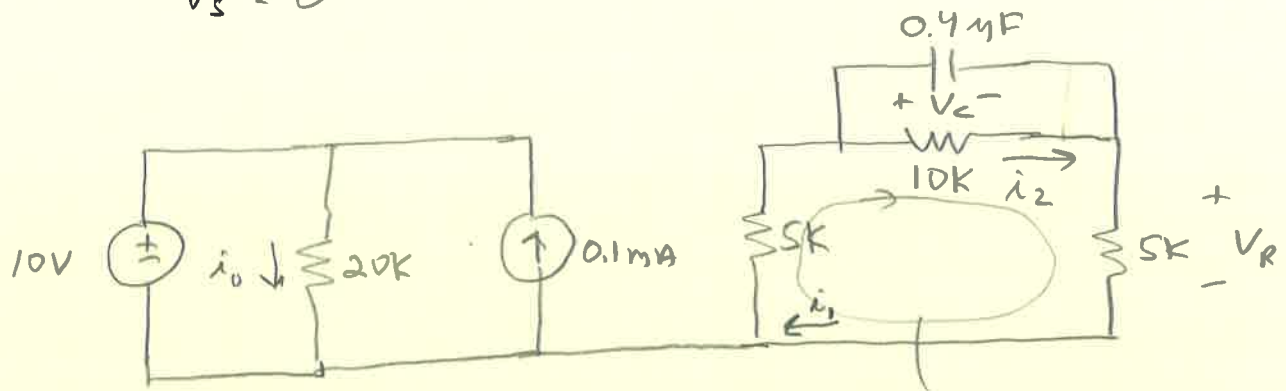

$$V_c(0^+) = V_c(0^-) = 2V$$

$$i_2(0^+) = V_c(0^+) / 10k = 2mA$$

$$i_1(0^+) = -2mA$$

$$V_R(0^+) = -2mA \cdot 5k = -1V$$

$$i_0(0^+) = 10V / 20k = 0.5mA$$

$$\text{@ } t=0^+ \text{ KVL: } 10k \cdot i_2 + 10k \cdot i_1 = 0$$

$$\therefore i_1(0^+) = -i_2(0^+)$$


$$\text{@ } t=\infty \quad i_1 = i_2 = V_R = V_c = V_s = 0$$

$$i_0 = 10V / 20k = 0.5mA$$

$$\tau = RC = [10k \parallel (5k + 5k)] \cdot 0.4\mu$$

$$= 5k \cdot 0.4\mu = 2 \times 10^{-3} = \underline{\underline{2ms}}$$

For  $t \leq 0^-$

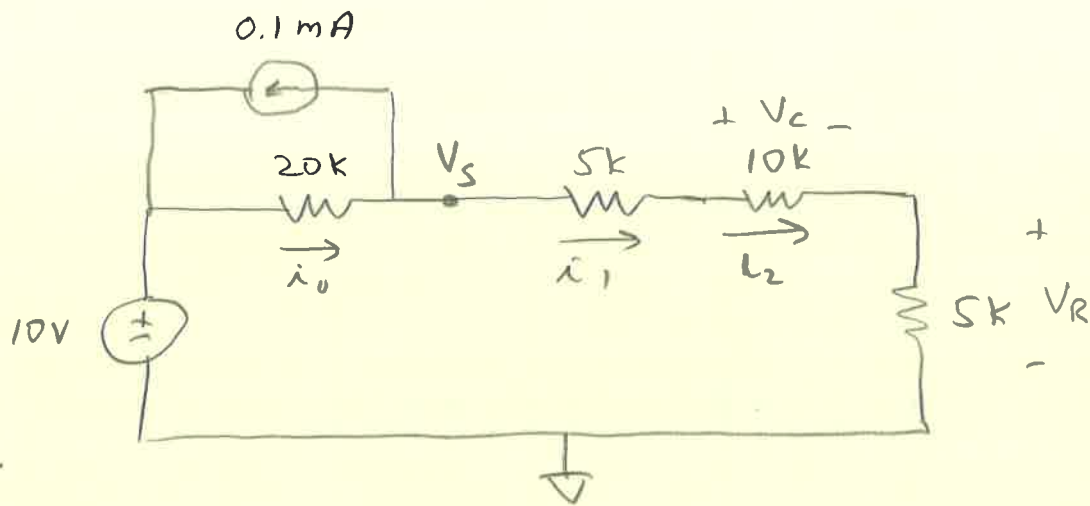

$$\text{KCL @ } V_S: \frac{V_S - 10}{20\text{k}} + 0.1\text{m} + \frac{V_S}{20\text{k}} = 0$$

$$V_S = 4\text{V}$$

$$i_0 = \frac{10 - V_S}{20\text{k}} = \frac{10 - 4}{20\text{k}} = \frac{6}{20\text{k}} = 0.3\text{mA}$$


$$i_1 = i_2 = \frac{V_S}{20\text{k}} = \frac{4}{20\text{k}} = 0.2\text{mA}$$

$$V_R = i_2 \times 5\text{k} = 1\text{V}$$

$$V_C = i_2 \times 10\text{k} = 2\text{V}$$

Problem 2 (35 points). The voltage waveform shown below can be described by the equation:


$$V(t) = V_m \cos(\omega t + \phi)$$

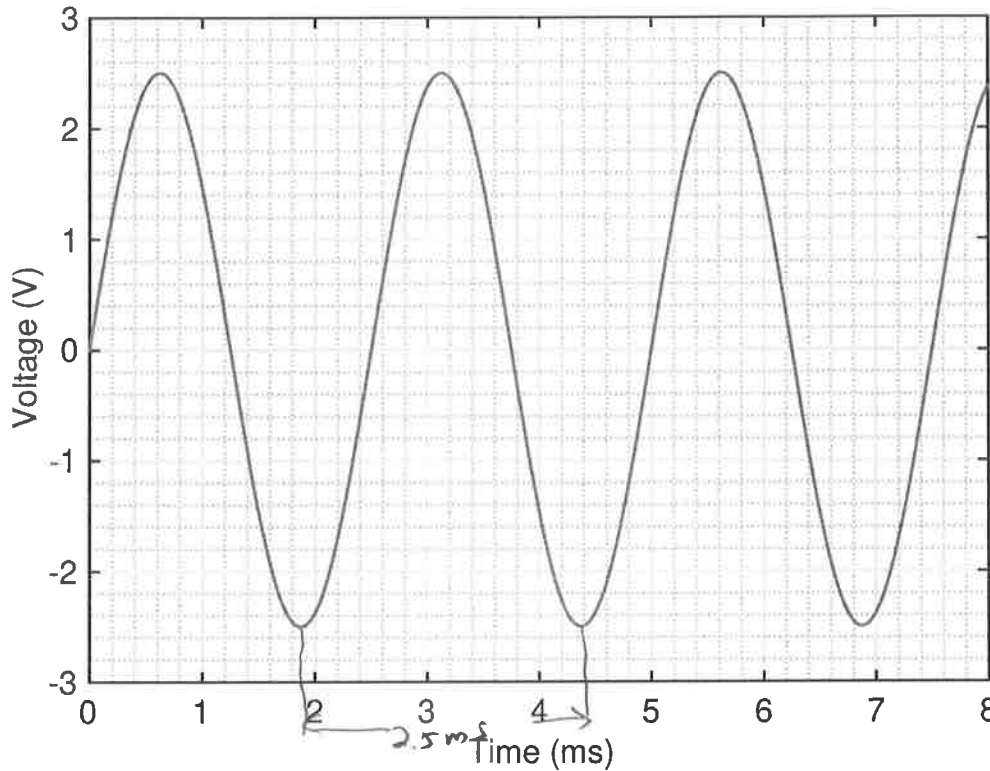

$T = 2.5 \text{ ms}$   
 $f = 400 \text{ Hz}$


- What is  $V_m$ ? 2.5 V
- What is  $\omega$ ?  $800\pi = 2513.3 \text{ rad/s}$
- What is  $\phi$ ?  $-90^\circ$  or  $-\frac{\pi}{2}$  radians
- What is the peak-to-peak voltage? 5 V
- What is  $V_{\text{RMS}}$ ?  $\frac{2.5}{\sqrt{2}} = 1.77 \text{ V}$
- What is  $\mathbf{V}$ , the Phasor representation of  $v(t)$ ?  $2.5 \angle -90^\circ$

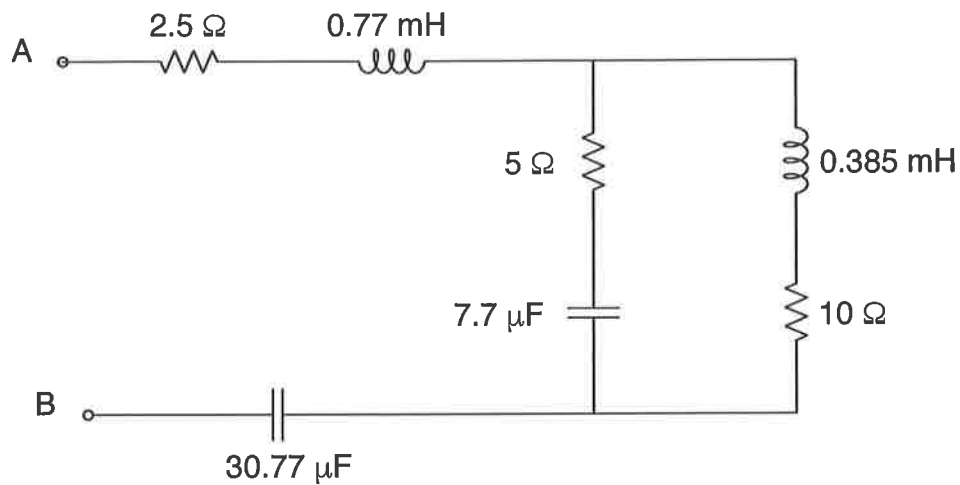Problem 3 (35 points). Consider the circuit below operating at a frequency of 2,069 Hz.



$$\omega = 2\pi f = 13,100 \text{ rad/s}$$

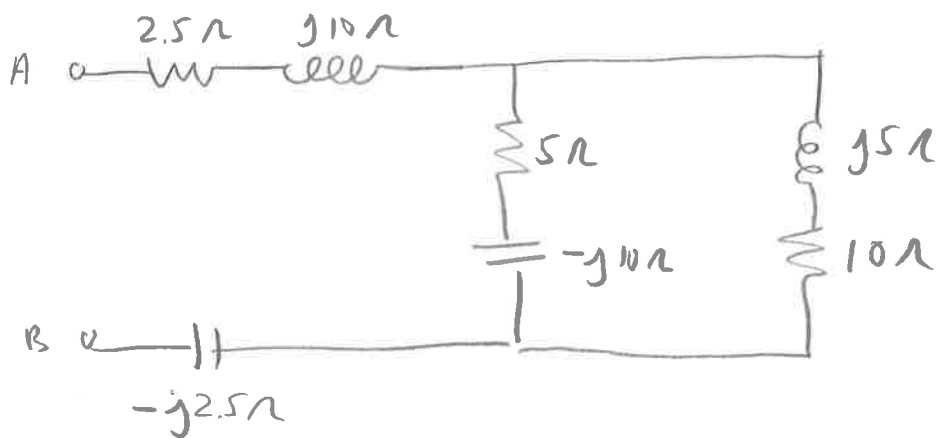Draw the frequency domain representation of this circuit.



$$Z = 2.5 + j10 - j2.5 + \underbrace{(5 - j10) \parallel (10 + j5)}_{7.5 - j2.5}$$

$$= 10 + j5$$

Calculate the equivalent impedance between terminals A and B

$$\underline{10 + j5 \Omega}$$

Calculate the equivalent admittance between terminals A and B

$$\underline{Y = \frac{1}{Z} = 0.08 - j0.04 \Omega^{-1}}$$

What is the equivalent resistance between terminals A and B?

$$\underline{10 \Omega}$$

What is the equivalent reactance between terminals A and B?

$$\underline{5 \Omega}$$


What is the equivalent conductance between terminals A and B?

$$\underline{0.08 \Omega^{-1}}$$

What is the equivalent susceptance between terminals A and B?

$$\underline{-0.04 \Omega^{-1}}$$

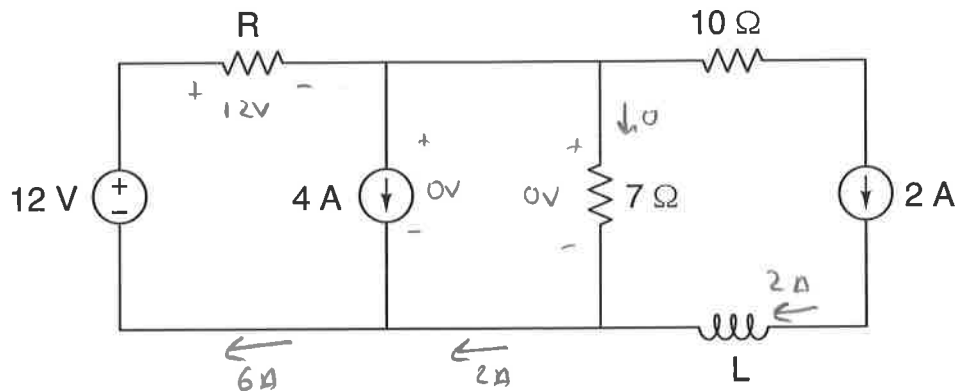**Bonus Problem** (6 points). In the circuit below, the 4A source delivers no power and absorbs no power. There is 10 mJ of energy stored in the inductor. Determine the values of R and L.



$$R = \underline{2\ \Omega}$$

$$L = \underline{5\text{ mH}}$$

$$\begin{aligned} \text{Energy} &= \frac{1}{2} L i^2 \\ &= \frac{1}{2} L 4 = 10^{-2} \\ L &= 10^{-2} / 2 = 5 \times 10^{-3} \text{ H} \\ L &= 5\text{ mH} \end{aligned}$$