

ECE 214 Linear Circuits Lab — Exam # 2

3 April 2012

Rules of the Exam


- Rule 1:** Each question is multiple choice and has equal weight.
- Rule 2:** Circle the correct answer.
- Rule 3:** You have 75 minutes to complete the exam.
- Rule 4:** The exam is open book, open notes, and open laboratory notebook. You may use a calculator.
- Rule 5:** Show all work and **intermediate steps** in your solutions. Clearly state all assumptions. Be neat!!!

Name

Try and Have a Good Time!!!

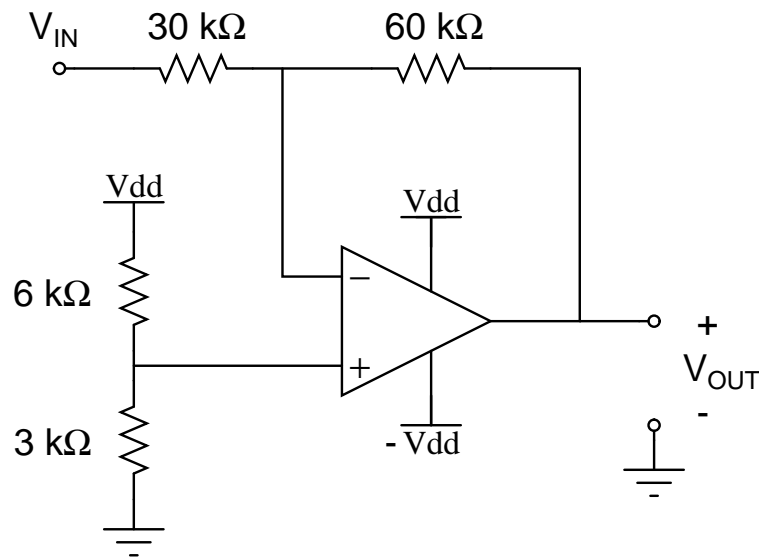Problem 1: OpAmp Circuit #1

Consider the OpAmp circuit shown below. Assume the OpAmp is ideal and $V_{dd} = 9\text{ V}$.



1. What is the function of this circuit?
 - (a) inverting amplifier
 - (b) non-inverting amplifier
 - (c) comparator
 - (d) Schmitt trigger
 - (e) inverting integrator
 - (f) none of the above
2. V_{IN} is a triangular waveform with 1 V peak-to-peak voltage and 0 V DC offset. What type of waveform is V_{OUT} ?
 - (a) sinusoidal waveform
 - (b) triangular waveform
 - (c) square waveform
 - (d) DC output equal to 0 V
 - (e) DC output equal to V_{dd}
 - (f) DC output equal to $-V_{dd}$

3. $V_{\text{IN}} = 0 \text{ V}$. What is V_{OUT} ?

- (a) -15 V (b) -9 V (c) -6 V (d) -3 V (e) 0 V (f) 3 V (g) 6 V (h) 9 V (i) 15 V

4. $V_{\text{IN}} = -3 \text{ V}$. What is V_{OUT} ?


- (a) -15 V (b) -9 V (c) -6 V (d) -3 V (e) 0 V (f) 3 V (g) 6 V (h) 9 V (i) 15 V

5. $V_{\text{IN}} = 3 \text{ V}$. What is V_{OUT} ?

- (a) -15 V (b) -9 V (c) -6 V (d) -3 V (e) 0 V (f) 3 V (g) 6 V (h) 9 V (i) 15 V

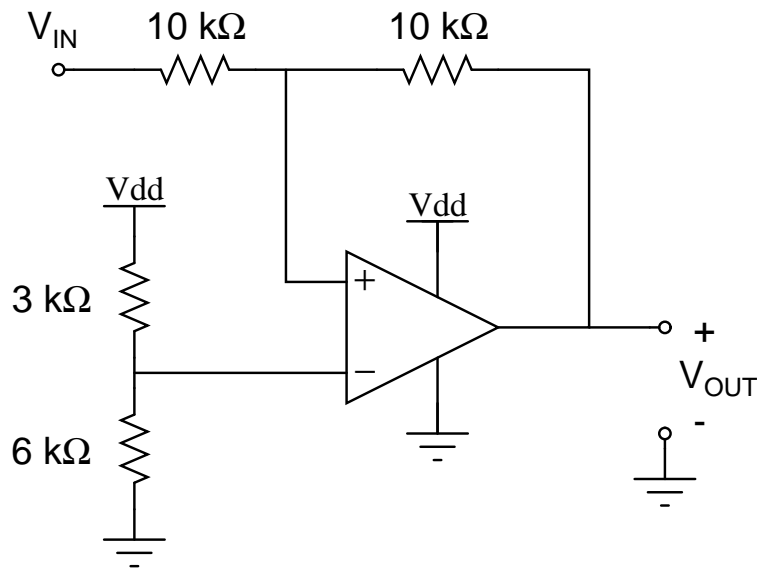Problem 2: OpAmp Circuit #2

Consider the OpAmp circuit shown below. Assume the OpAmp is ideal and $V_{dd} = 9\text{ V}$.



6. What is the function of this circuit?
- (a) inverting amplifier
 - (b) non-inverting amplifier
 - (c) comparator
 - (d) Schmitt trigger
 - (e) inverting integrator
 - (f) none of the above
7. V_{IN} is a triangular waveform with 1 V peak-to-peak voltage and 0 V DC offset. What type of waveform is V_{OUT} ?
- (a) sinusoidal waveform
 - (b) triangular waveform
 - (c) square waveform
 - (d) DC output equal to 0 V
 - (e) DC output equal to V_{dd}
 - (f) DC output equal to $-V_{dd}$

8. $V_{\text{IN}} = 2 \text{ V}$. What is V_{OUT} ?

- (a) -9 V (b) 0 V (c) 1 V (d) 3 V (e) 5 V (f) 7 V (g) 9 V (h) 12 V
(i) can not be determined (j) none of the others

9. $V_{\text{IN}} = 12 \text{ V}$. What is V_{OUT} ?


- (a) -9 V (b) 0 V (c) 1 V (d) 3 V (e) 5 V (f) 7 V (g) 9 V (h) 12 V
(i) can not be determined (j) none of the others

10. $V_{\text{IN}} = 9 \text{ V}$. What is V_{OUT} ?

- (a) -9 V (b) 0 V (c) 1 V (d) 3 V (e) 5 V (f) 7 V (g) 9 V (h) 12 V
(i) can not be determined (j) none of the others

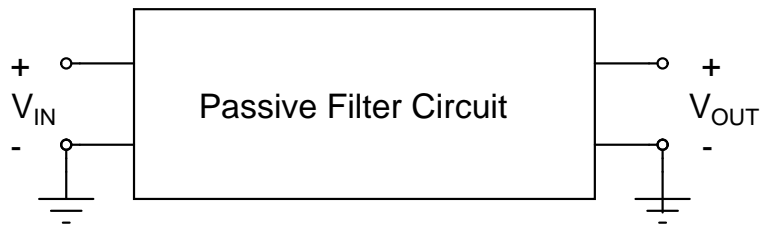Problem 3: Filter Circuit

Consider the passive filter circuit shown below:



11. V_{IN} is a square wave with a 50% duty cycle, a frequency of 10 kHz and a peak-to-peak voltage of 6 V. What type of filter could be used to generate V_{OUT} that is a sinusoidal waveform with a frequency of 30 kHz?
 - (a) low pass filter
 - (b) band pass filter
 - (c) band reject filter
 - (d) high pass filter
 - (e) no filter can produce the desired output waveform
12. For the conditions in question 11, what would be the maximum peak-to-peak voltage of the 30 kHz signal?
 - (a) 0 V (b) 1 V (c) 1.5 V (d) 2 V (e) 2.5 V (f) 3 V (g) 4 V (h) 5 V
13. V_{IN} is a sinusoidal wave with a frequency of 10 kHz and a peak-to-peak voltage of 5 V. What type of filter could be used to generate V_{OUT} that is a sinusoidal waveform with a frequency of 30 kHz?
 - (a) low pass filter
 - (b) band pass filter
 - (c) band reject filter
 - (d) high pass filter
 - (e) no filter can produce the desired output waveform

14. V_{IN} is a square wave with a 50% duty cycle, a frequency of 50 kHz and a peak-to-peak voltage of 10 V. What type of filter could be used to generate V_{OUT} that is a sinusoidal waveform with a frequency of 100 kHz?
- (a) low pass filter
 - (b) band pass filter
 - (c) band reject filter
 - (d) high pass filter
 - (e) no filter can produce the desired output waveform
15. V_{IN} is a square wave with a 50% duty cycle, a frequency of 1 kHz and a peak-to-peak voltage of 10 V. The filter is a low pass filter. What is the minimum required order of the filter such that the 11th harmonic is at least 40 dB below the fundamental frequency?
- (a) 0th order
 - (b) 1st order
 - (c) 2nd order
 - (d) 3rd order
 - (e) 4th order
 - (f) can not be done