

## ECE 214 — Exam # 2

Estimated time for completion: <1.25 hour  
16 April 2013

### Rules of the Exam

**Rule 1:** The examination period begins at 8:00am on Tuesday 16 April 2013 and ends at 9:15am on Tuesday 16 April 2013.

**Rule 2:** There are three problems. All problems have equal weight.

**Rule 3:** The exam is closed book and closed notes but you may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.

**Rule 4:** Show all work and intermediate steps in your solutions. Clearly state all assumptions. Be neat!!!

---

Name

**Problem 1** The op-amp below is ideal. The input signal is  $V_{in}$ .

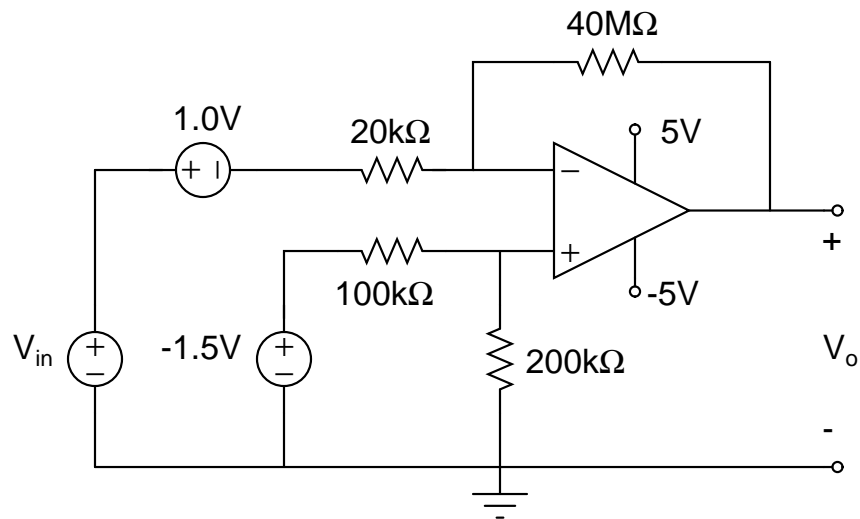


Figure 1: Circuit #1

Which of the following best describes Circuit #1?

1. Inverting OpAmp with DC offset
2. Non-Inverting OpAmp with DC offset
3. Inverting Integrator
4. Non-Inverting Integrator
5. Schmitt Trigger

Write the equation for the output voltage  $V_o$  as a function of the input voltage  $V_{in}$ ? Sketch the output voltage  $V_o$  for the given input voltage  $V_{in}$  shown on the next page. Make sure to label the “Y-axis” of the graph.

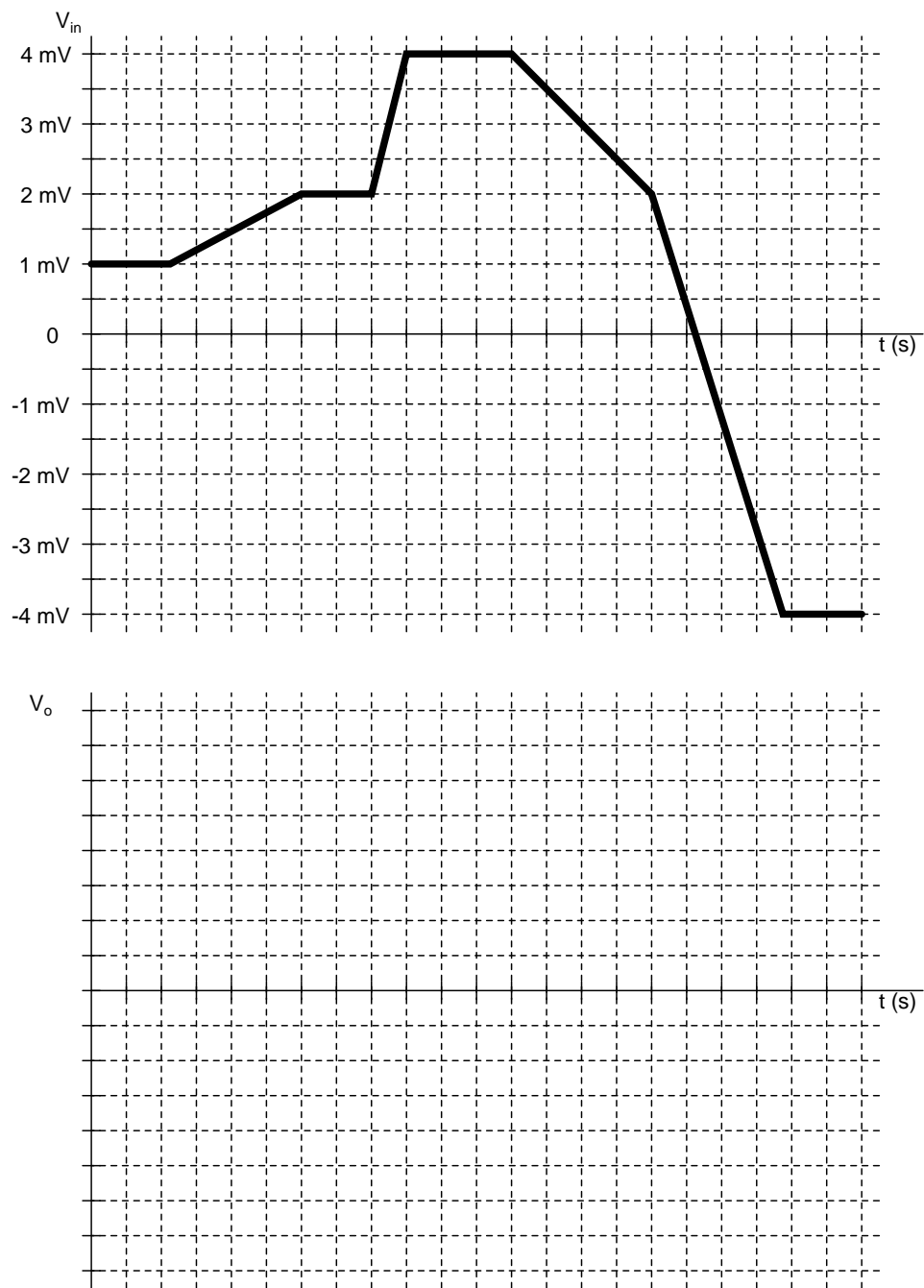


Figure 2: Input and output voltages for Circuit #1

**Problem 2** The op-amp below is ideal. The input signal is  $V_{in}$ .

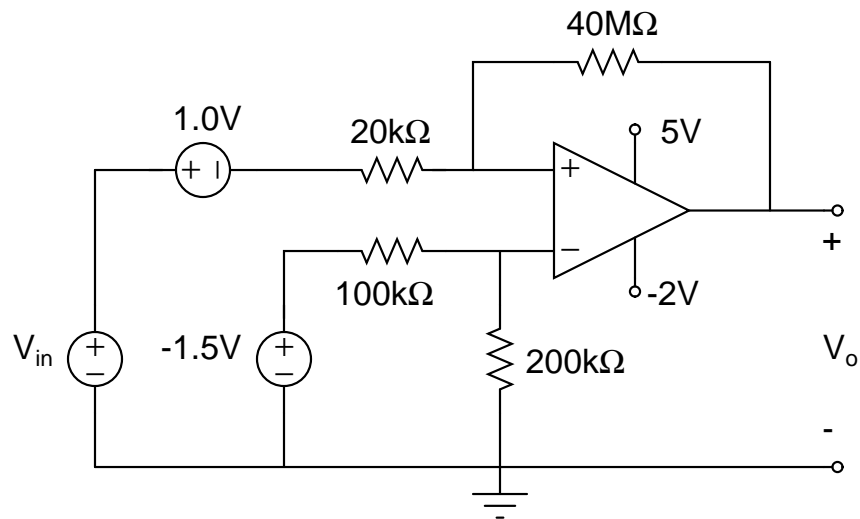


Figure 3: Circuit #2

Which of the following best describes Circuit #2?

1. Inverting OpAmp with DC offset
2. Non-Inverting OpAmp with DC offset
3. Inverting Integrator
4. Non-Inverting Integrator
5. Schmitt Trigger

Write the equation for the output voltage  $V_o$  as a function of the input voltage  $V_{in}$ ? Sketch the output voltage  $V_o$  for the given input voltage  $V_{in}$  shown on the next page. Make sure to label the “Y-axis” of the graph.


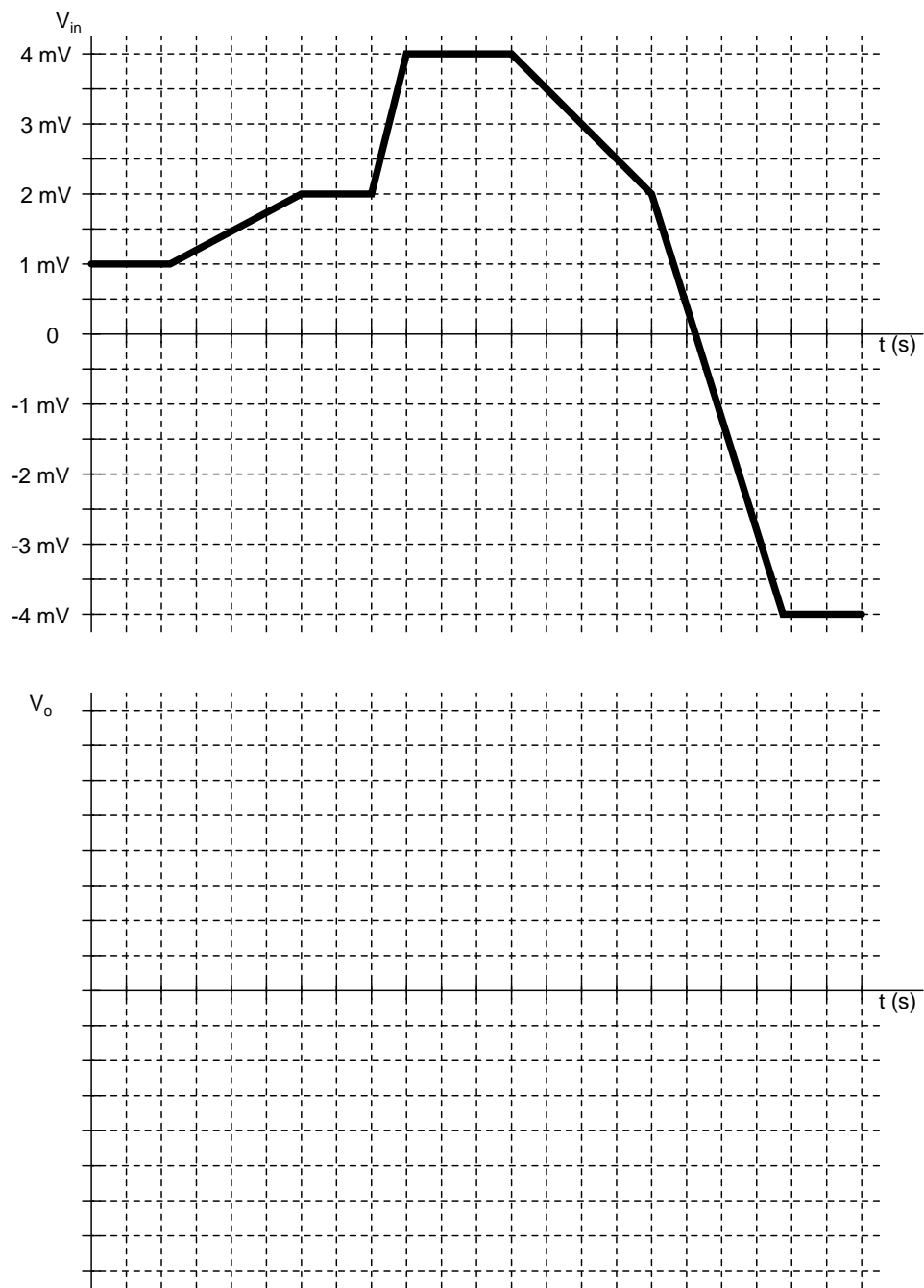


Figure 4: Input and output voltages for Circuit #2
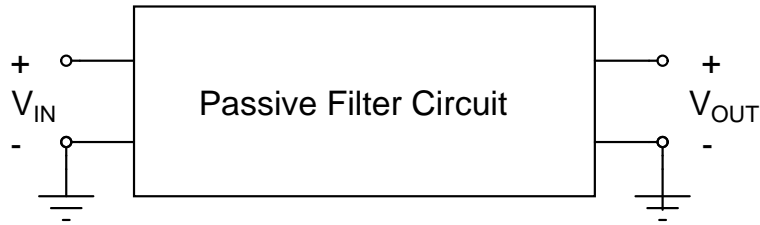
### Problem 3: Filter Circuit

Consider the ideal passive filter circuit shown below:



For the questions below circle the most correct answer:

1.  $V_{IN}$  is a square wave with a 50% duty cycle, a frequency of 25 kHz and a peak-to-peak voltage of 5 V.  $V_{OUT}$  is a sinusoidal waveform with a single frequency of 50 kHz. What type of filter could be used to generate  $V_{OUT}$ ?
  - (a) low pass filter
  - (b) band pass filter
  - (c) band reject filter
  - (d) high pass filter
  - (e) none of the above
2.  $V_{IN}$  is a square wave with a 50% duty cycle, a frequency of 25 kHz and a peak-to-peak voltage of 5 V.  $V_{OUT}$  that is a sinusoidal waveform with a single frequency of 75 kHz? What type of filter could be used to generate  $V_{OUT}$ ?
  - (a) low pass filter
  - (b) band pass filter
  - (c) band reject filter
  - (d) high pass filter
  - (e) none of the above

3.  $V_{IN}$  is a triangular wave with a frequency of 20 kHz and the filter is a low pass filter with a cutoff frequency of 60 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental at the output of the filter?
- (a) -22.08 dB
  - (b) -19.08 dB
  - (c) -16.08 dB
  - (d) -12.54 dB
  - (e) -3 dB
  - (f) +3 dB
  - (g) none of the above
4.  $V_{IN}$  is a triangular wave with a frequency of 20 kHz and the filter is a high pass filter with a cutoff frequency of 20 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental at the output of the filter?
- (a) -22.08 dB
  - (b) -19.08 dB
  - (c) -16.08 dB
  - (d) -12.54 dB
  - (e) -3 dB
  - (f) +3 dB
  - (g) none of the above
5.  $V_{IN}$  is a triangular wave with a frequency of 20 kHz and the filter is a high pass filter with a cutoff frequency of 60 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental at the output of the filter?
- (a) -22.08 dB
  - (b) -19.08 dB
  - (c) -16.08 dB
  - (d) -12.54 dB
  - (e) -3 dB
  - (f) +3 dB
  - (g) none of the above