

ECE 214 — Exam # 1

Estimated time for completion: ≤ 1.25 hour
25 February 2014

Rules of the Exam

- Rule 1:** The examination period begins at 8:00am on Tuesday 25 February 2014 and ends at 9:15am on Tuesday 25 February 2014.
- Rule 2:** There are five problems with a total of 26 answers. Each answer is worth four points. There are four bonus points!
- Rule 3:** For all answers, make sure to include the units along with the numerical answer and show all work.
- Rule 4:** There is minimal partial credit.
- Rule 5:** The exam is closed book and closed notes but you may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.

Name


Problem 1 Oscilloscope traces for two voltage waveforms

$$V_1(t) = A_1 \cos(\omega t + \phi_1) + V_{DC1}$$

and

$$V_2(t) = A_2 \cos(\omega t + \phi_2) + V_{DC2}$$

are shown below.

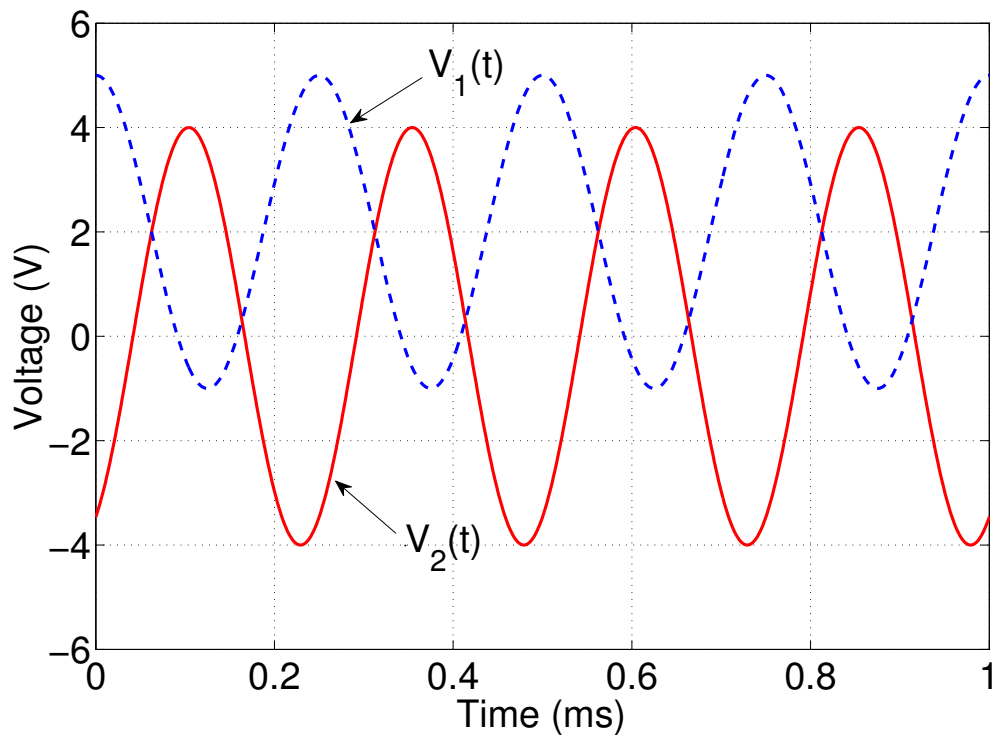

- (a) What is A_1 ? _____
- (b) What is A_2 ? _____
- (c) What is ω ? _____
- (d) What is $|\phi_1 - \phi_2|$? _____
- (e) What is V_{DC1} ? _____
- (f) What is V_{DC2} ? _____
- (g) $V_2(t)$ is measured with a DVM, set to measure an ac voltage. What voltage is displayed on the DVM? _____


Problem 2 The Lissajous figure, using the XY-mode on the scope, produced by two voltage waveforms

$$V_x(t) = X_0 \sin(\omega t + \phi_1)$$

and



$$V_y(t) = Y_0 \sin(\omega t + \phi_2)$$

is shown below.

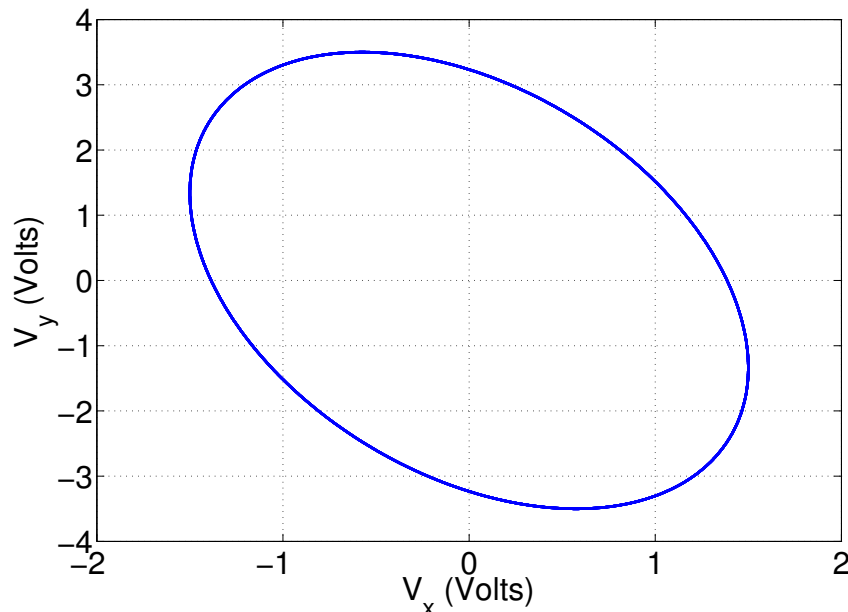

- (a) What is X_0 ? _____
- (b) What is Y_0 ? _____
- (c) What is $|\phi_1 - \phi_2|$ in degrees? _____
- (d) What is $|\phi_1 - \phi_2|$ in radians? _____

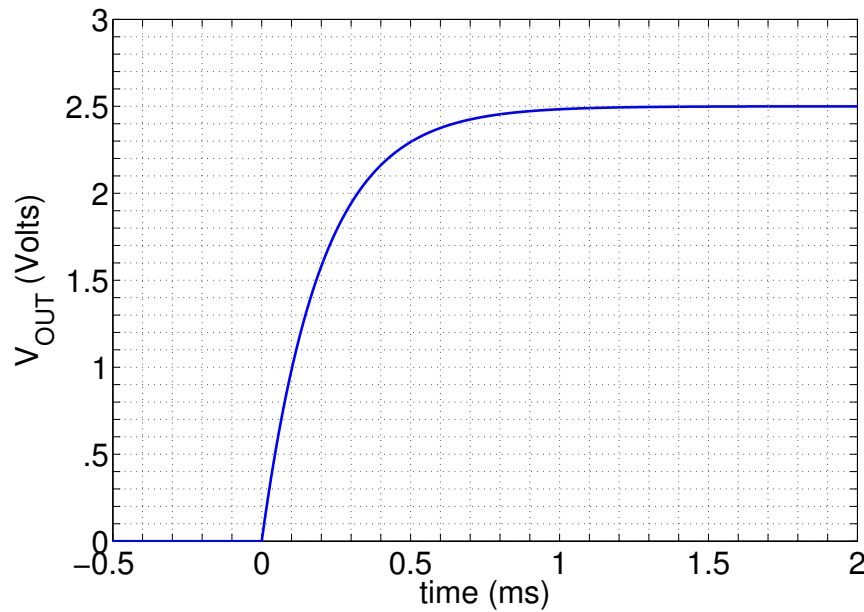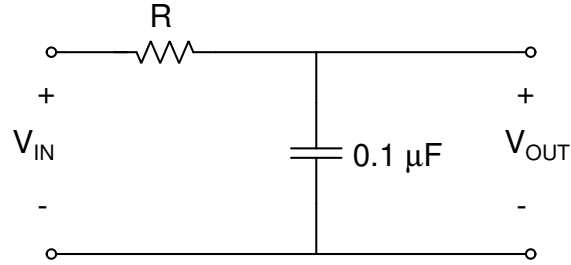
Problem 3 Consider the RC circuit and step response at $t = 0$ shown below:



The step response is given by $V_{OUT}(t) = V_0 (1 - e^{-t/\tau})$ for $t \geq 0$


- (a) What is V_0 ? _____
- (b) What is R ? _____
- (c) What is the rise-time? _____
- (d) Is this circuit a low pass, high pass, band pass or band reject filter? _____
- (e) At what frequency is $V_{OUT}/V_{IN} = -20\text{dB}$? _____
- (f) At what frequency is $V_{OUT}/V_{IN} = -28\text{dB}$? _____

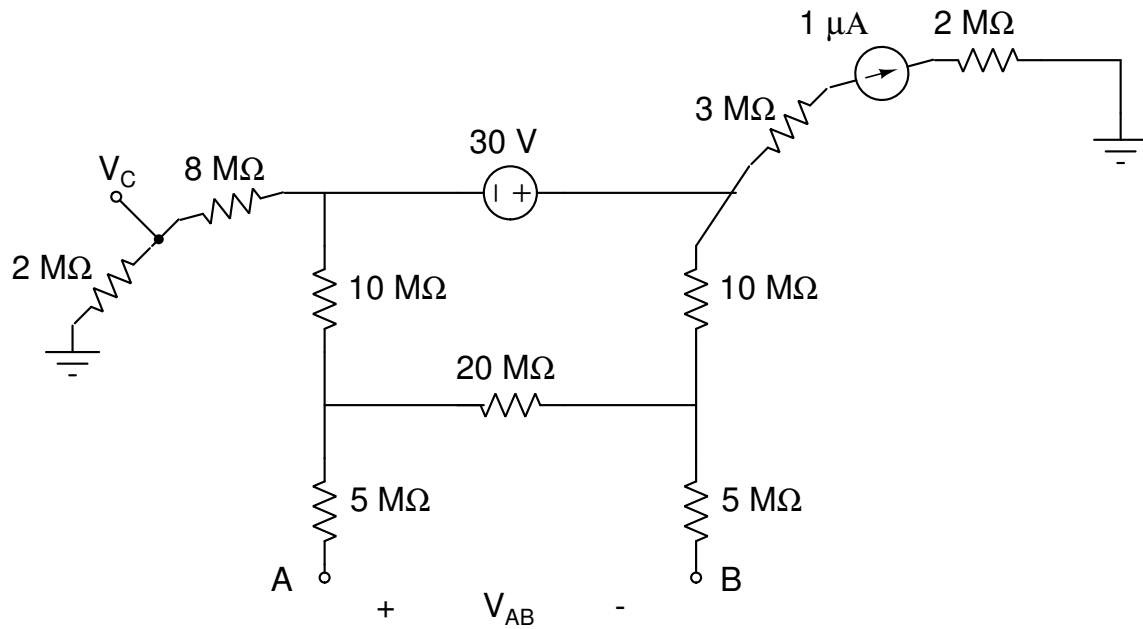Problem 4 A digital volt meter (DVM), having an input resistance of $10\text{ M}\Omega$, is used to make measurements on the circuit below.



- (a) What is the actual voltage V_{AB} ? _____
- (b) What is the measured voltage V_{AB} ? _____
- (c) What is the actual voltage V_C with respect to ground? _____
- (d) What is the measured voltage V_C with respect to ground? _____

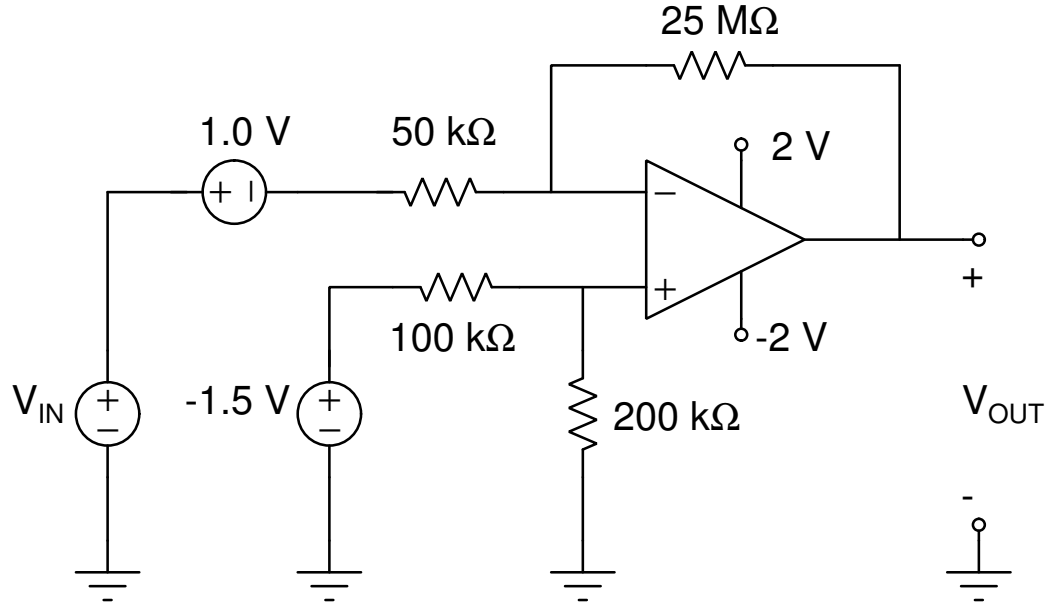Problem 5 In the schematic below, assume the OpAmp is ideal.



- Is this circuit an inverting amplifier, a non-inverting amplifier, an inverting differentiator, an inverting integrator, or a Schmitt trigger? _____
- When $V_{\text{IN}} = 1.0\text{mV}$, what is V_{OUT} ? _____
- When $V_{\text{IN}} = -1.0\text{mV}$, what is V_{OUT} ? _____
- When $V_{\text{IN}} = 10\text{mV}$, what is V_{OUT} ? _____
- When $V_{\text{IN}} = -10\text{mV}$, what is V_{OUT} ? _____