

ECE 214 — Exam 2

Estimated time for completion: \leq 1.25 hour
25 April 2017

Rules of the Exam

Rule 1: The examination period begins at 9:30am on Tuesday 25 April 2017 and ends at 10:45am on Tuesday 25 April 2017.

Rule 2: The exam is 15% of your grade.

Rule 3: There are a total of 15 answers. All answers are worth 1 point unless otherwise indicated. Circle the **most correct** answer.

Rule 4: The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.

Rule 5: Have fun!



Answer Key

Name _____

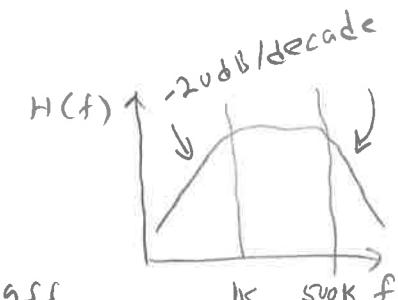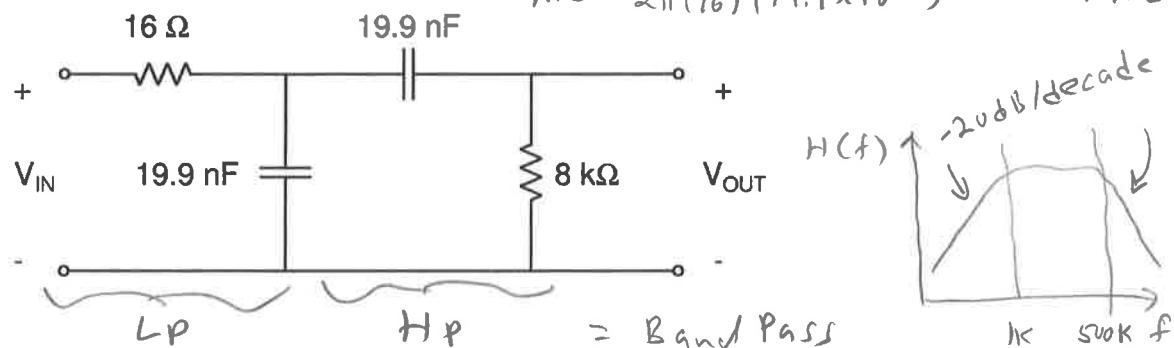Problem 1: Filter

Consider the filter shown below: High Pass $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(8 \times 10^3)(19.9 \times 10^{-9})} = 1 \text{ kHz}$

Low Pass $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(16)(19.9 \times 10^{-9})} = 500 \text{ kHz}$



1. $V_{IN} = 10 \cos(20,000\pi t)$ and $V_{OUT} = A \cos(40,000\pi t)$. What is the value of A?

- (a) 0 V $A = 0$ (There are no frequency components at $\omega = 40,000\pi$)
- (b) 0.5 V
- (c) 1 V
- (d) 2 V
- (e) 3.2 V
- (f) 5 V
- (g) 7 V
- (h) 10 V
- (i) none of the above

2. $V_{IN} = 10 \cos(40,000\pi t)$ and $V_{OUT} = A \cos(40,000\pi t)$. What is the value of A?

- (a) 0 V $f = \frac{\omega}{2\pi} = 20 \text{ kHz}$ (In the pass band)
- (b) 0.5 V
- (c) 1 V
- (d) 2 V
- (e) 3.2 V
- (f) 5 V
- (g) 7 V
- (h) 10 V
- (i) none of the above

3. $V_{IN} = 10 \cos(2,000\pi t)$ and $V_{OUT} = A \cos(2,000\pi t)$. What is the value of A?

- (a) 0 V
- (b) 0.5 V

$$f = \frac{\omega}{2\pi} = 1 \text{ kHz} \quad (\text{at the cutoff freq})$$

- (c) 1 V
- (d) 2 V
- (e) 3.2 V
- (f) 5 V
- (g) 7 V
- (h) 10 V

$$A = (-3 \text{ dB}) \times 10 \Rightarrow \frac{A}{10} = -3 \text{ dB}$$

$$20 \log\left(\frac{A}{10}\right) = -3 \Rightarrow \frac{A}{10} = 10^{-\frac{3}{20}} = 0.7$$

$$A = 7 \text{ V}$$

- (i) none of the above

4. $V_{IN} = 10 \cos(200\pi t)$ and $V_{OUT} = A \cos(200\pi t)$. What is the value of A?

- (a) 0 V
- (b) 0.5 V

$$f = \frac{\omega}{2\pi} = 100 \text{ Hz} \quad (\text{one decade below cutoff freq})$$

- (c) 1 V
- (d) 2 V
- (e) 3.2 V
- (f) 5 V
- (g) 7 V
- (h) 10 V

$$\frac{A}{10} = -2 \text{ dB}$$

$$20 \log\left(\frac{A}{10}\right) = -20 \Rightarrow \log\frac{A}{10} = -1 \Rightarrow \frac{A}{10} = 0.1$$

$$A = 1 \text{ V}$$

- (i) none of the above

5. $V_{IN} = 10 \cos(2,000,000\pi t)$ and $V_{OUT} = A \cos(2,000,000\pi t)$. What is the value of A?

- (a) 0 V
- (b) 0.5 V

$$f = \frac{\omega}{2\pi} = 10^6 \text{ Hz} \leftarrow \text{twice the cutoff freq}$$

- (c) 1 V
- (d) 2 V
- (e) 3.2 V

$$A \approx 10 \times (-20 \text{ decade})(\log(2))$$

- (f) 5 V
- (g) 7 V
- (h) 10 V

$$= 10 \times (-6 \text{ dB})$$

↑

- (i) none of the above



$$\frac{A}{10} = -6 \text{ dB}$$

$$-6 = 20 \log\left(\frac{A}{10}\right)$$

$$\log\left(\frac{A}{10}\right) = -\frac{1}{3} \Rightarrow \frac{A}{10} = 10^{-\frac{1}{3}} = 0.46$$

$$A = 4.6 \text{ V} \approx 5 \text{ V}$$

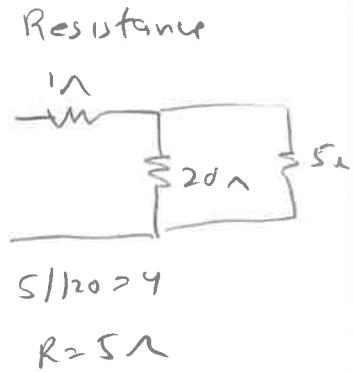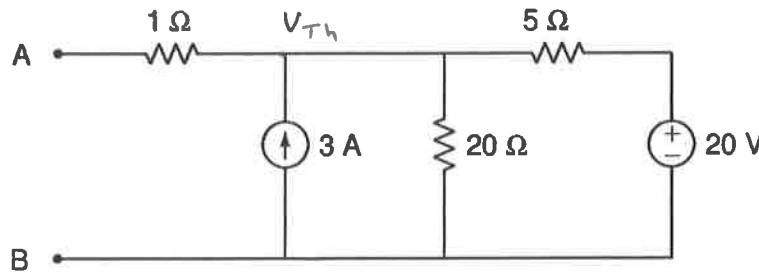Problem 2: Consider the circuit shown below:



1. What is the Thévenin Equivalent Voltage with respect to terminals A and B? (2 points)

- (a) 6.3 V
- (b) 10 V
- (c) 12.6 V
- (d) 14 V
- (e) 18 V
- (f) 28 V
- (g) None of the above

$$\frac{V_{T_h}}{20} + \frac{V_{T_h} - 20}{5} - 3 = 0$$


$$V_{T_h} = 28 \text{ V}$$

2. What is the Thévenin Equivalent Resistance with respect to terminals A and B? (2 points)

- (a) 1 Ω
- (b) 4 Ω
- (c) 5 Ω
- (d) 6 Ω
- (e) 12 Ω
- (f) 15 Ω
- (g) None of the above

3. A resistor that dissipates 32 W of power is placed between terminals A and B. What is the value of this resistor?

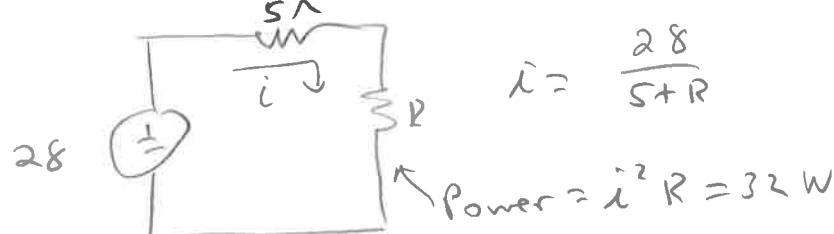- (a) 1 Ω
- (b) 1 Ω or 12.5 Ω
- (c) 2 Ω
- (d) 2 Ω or 12.5 Ω
- (e) 37 Ω
- (f) 37 Ω or 12.5 Ω
- (g) None of the above



$$Power = \left(\frac{28}{5+R} \right)^2 R = 32$$

$$(28)^2 R = 32(5+R)^2$$


$$R = 2 \text{ or } 12.5$$

$$= 32(25 + 10R + R^2)$$

$$32R^2 + (320 - 784)R + 800 = 0$$



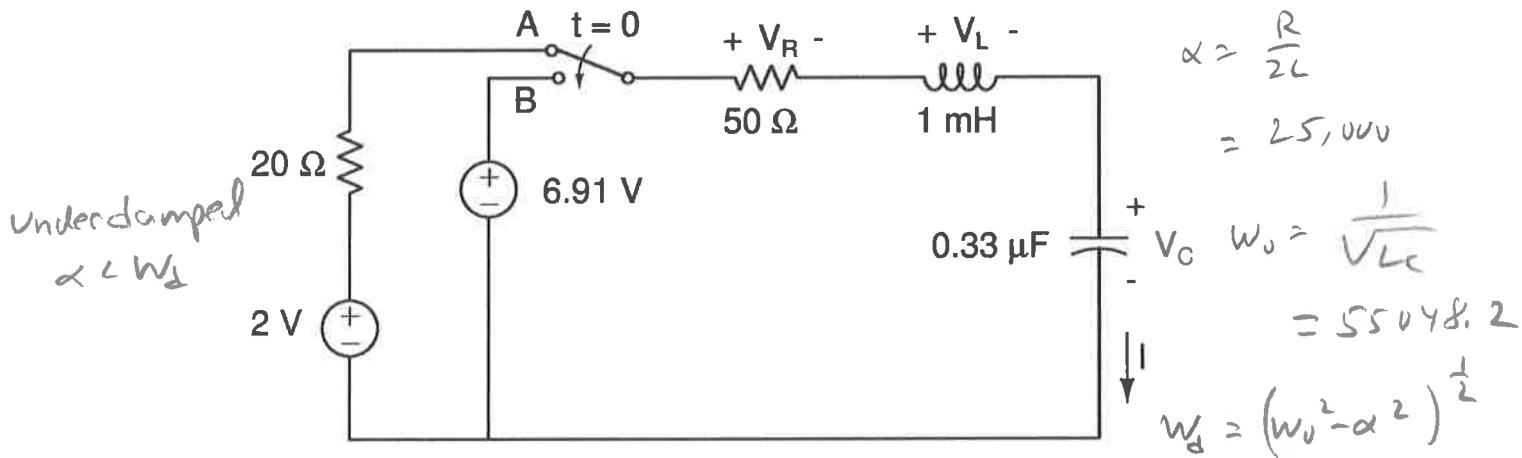Problem 3: In the series RLC circuit shown below, the switch has been in position 'A' for a very long time and moves to position 'B' at $t=0$.



1. What is $V_C(0^+)$?

- (a) 0 V
- (b) 1.1 V
- (c) 1.7 V
- (d) 2.0 V
- (e) 4.91 V
- (f) 6.91 V
- (g) None of the above

$$t < 0 \quad V_C = 2 V$$

$$i = 0$$

$$V_R = 0$$

$$V_L = 0$$

$$= 49043.9$$

2. What is $V_L(0^+)$?

- (a) 0 V
- (b) 1.1 V
- (c) 1.7 V
- (d) 2.0 V
- (e) 4.91 V
- (f) 6.91 V
- (g) None of the above

$$t = 0^+ \quad V_C = 2 V$$

$$V_R = 0$$

$$i = 0$$

$$V_L = 4.91$$

3. What is $V_R(0^+)$?

- (a) 0 V
(b) 1.1 V
(c) 1.7 V
(d) 2.0 V
(e) 4.91 V
(f) 6.91 V
(g) None of the above

4. What is $V_R(\infty)$?

- (a) 0 V
(b) 1.1 V
(c) 1.7 V
(d) 2.0 V
(e) 4.91 V
(f) 6.91 V
(g) None of the above

5. What is $V_R(40\mu)$?

- (a) 0 V
(b) 1.1 V
(c) 1.7 V
(d) 2.0 V
(e) 4.91 V
(f) 6.91 V
(g) None of the above

$$i(t) = i(\infty) + B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$i(0) = 0 = B_1$$

$$i(t) = B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{N_c(0^+)}{L} = \frac{4.91 \times 10^3}{L} = B_2 \omega_d$$

$$B_2 = \frac{4.91 \times 10^3}{\omega_d} = 0.1$$

$$i(t) = 0.1 e^{-\alpha t} \sin(\omega_d t)$$

$$i(40\mu s) = 34 \text{ mA}$$

$$V_R(40\mu s) = 50 \times 34 \text{ mA} = 1.7 \text{ V}$$

Extra Credit:

1. What is the part number of the transistor used in Lab #9?

- (a) IRFD113
- (b) IRFD400
- (c) IRFD100
- (d) 2N7801
- (e) 2N7000
- (f) 2N7001
- (g) None of the above

2. What is the part number of the inductor used in Lab #6?

- (a) 32102C
- (b) L1000
- (c) L1mltd
- (d) h1298d
- (e) 21C098
- (f) 420d2
- (g) None of the above