

ECE 214 — Final Exam


Estimated time for completion: \ll 2.0 hour
11 May 2017

Rules of the Exam

- Rule 1:** The examination period begins at 8:00am on Thursday 11 May 2017 and ends at 10:00am on Thursday 11 May 2017.
- Rule 2:** The exam is 15% of your grade. There are two questions, each with equal weight. There is one bonus question.
- Rule 3:** To receive credit, all work must be shown. Answers without supporting work will not receive credit. Make sure to include the units along with the numerical answer.
- Rule 4:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook and a calculator.
- Rule 5:** Turn in your ECE 214 Laboratory Notebook with the Final Exam.

Name


Problem 1: The OpAmp is ideal.

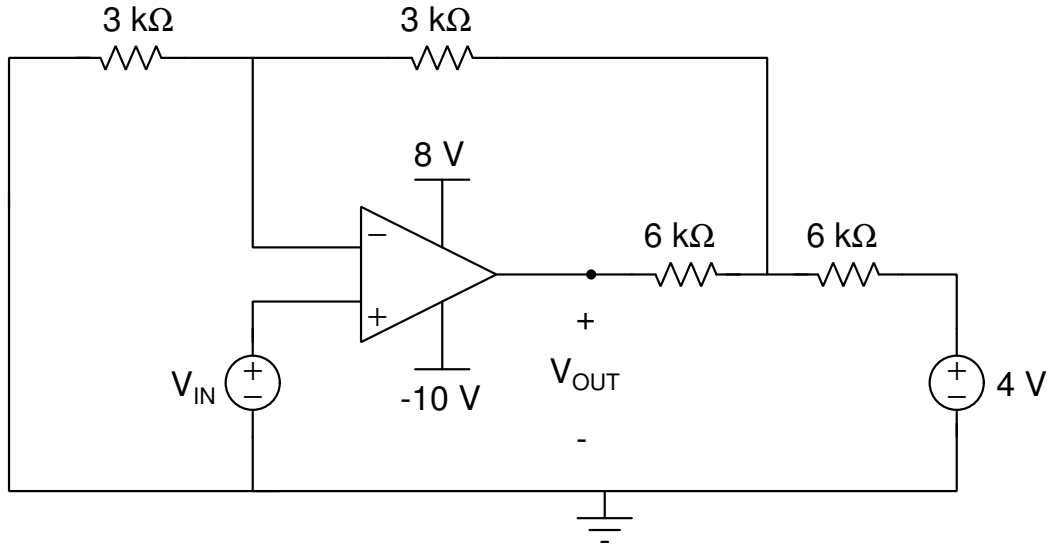

(a) Derive the equation for V_{OUT} as a function of V_{IN} .

(b) What is the maximum value of V_{IN} that will keep the output of the OpAmp (V_{OUT}) from saturating?

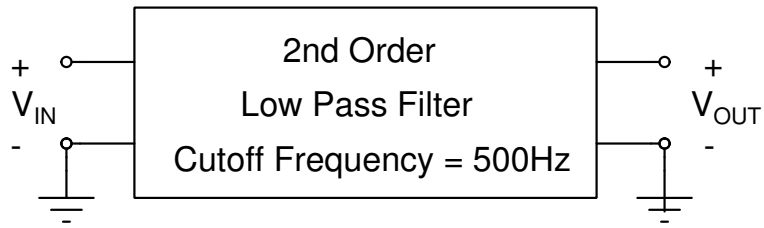Problem 2: Consider a 2nd order ideal low pass filter. The cutoff frequency is 500 Hz. The input (V_{IN}) is a sine wave at frequency f .




What are the approximate frequencies that correspond to the attenuations listed in the table below?

$\frac{V_{OUT}}{V_{IN}}$	frequency
-3 dB	
-6 dB	
-20 dB	
-40 dB	
-60 dB	
-80 dB	

Bonus Question: (5 points)

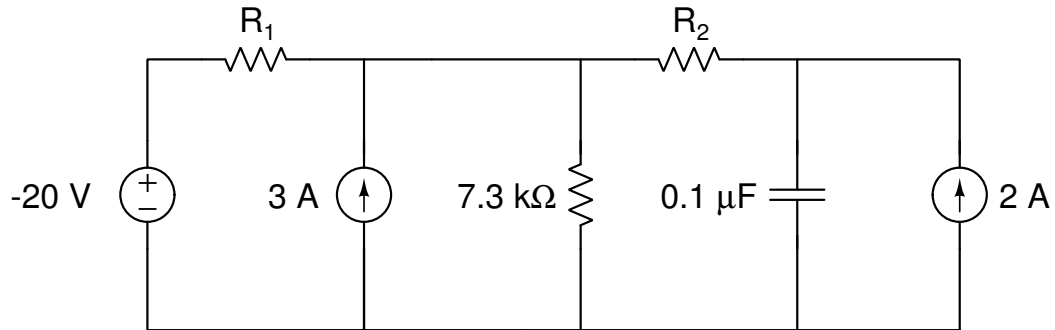In the circuit below, the 3A current source delivers no power and absorbs no power. The circuit dissipates a total of 200 W of power.



What is R_1 ? _____

What is R_2 ? _____

Name: _____

Name: _____

Name: _____