

## ECE 214 — Exam #1

Estimated time for completion:  $\leq 1.25$  hour  
6 March 2018


### Rules of the Exam

- Rule 1:** The examination period begins at 11:00 am on Tuesday, 6 March 2018 and ends at 12:15 pm on Tuesday, 6 March 2018.
- Rule 2:** The exam is worth 15 points.
- Rule 3:** There are a total of 18 answers. Each answer is worth 1 point. The maximum score is 18 out of 15.
- Rule 4:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.
- Rule 5:** To receive credit for an answer include the units along with the numerical answer.
- Rule 6:** Show all work - answers without supporting work will not receive credit.
- Rule 7:** Do not leave the room until you have completed the exam.

---

Name

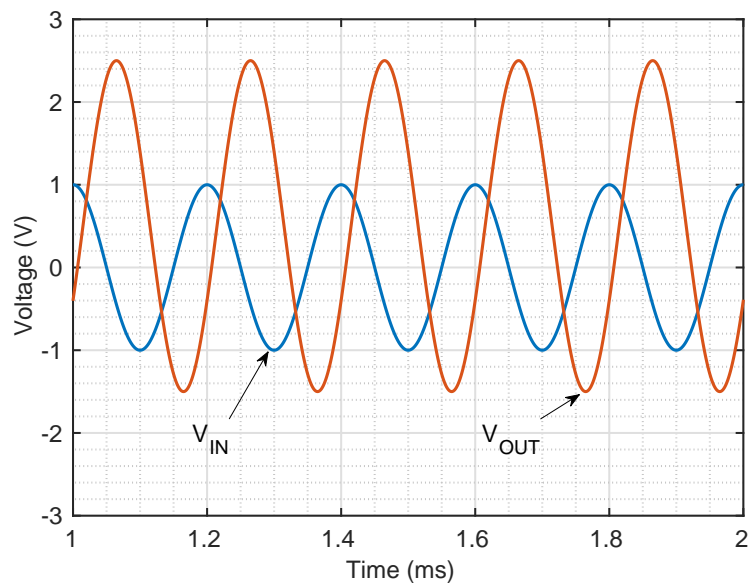**Problem 1:** The input and output signals from an amplifier circuit are shown below:



The input signal is described by:







$$V_{\text{IN}}(t) = V_1 \cos(\omega t) \quad (1)$$

and, the output signal by:

$$V_{\text{OUT}}(t) = V_2 \cos(\omega t + \phi) + V_{2_{DC}} \quad (2)$$


1. What is  $V_1$ ? \_\_\_\_\_
2. What is the voltage gain  $= \left| \frac{V_2}{V_1} \right|$ ? \_\_\_\_\_
3. What is  $\omega$ ? \_\_\_\_\_
4. What is  $\phi$ ? \_\_\_\_\_
5. What is  $V_{2_{DC}}$ ? \_\_\_\_\_
6. When  $V_{\text{IN}}(t)$  is measured by a DVM set to measure an ac voltage, what value would the DVM indicate? \_\_\_\_\_

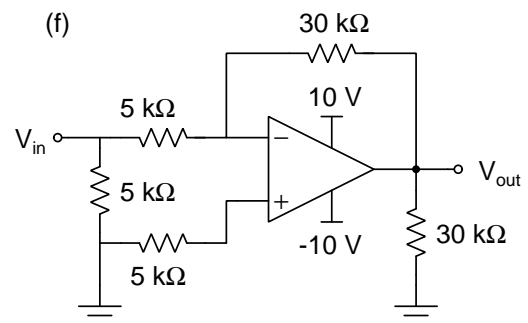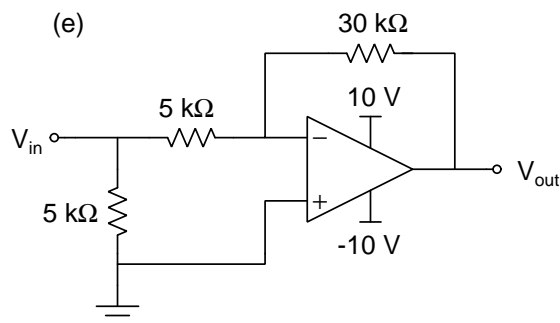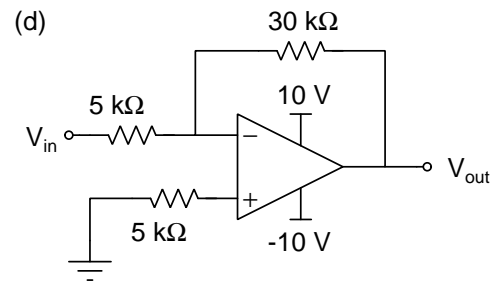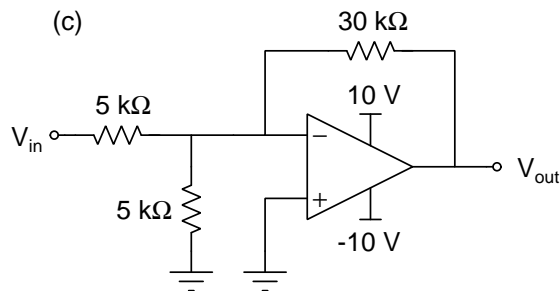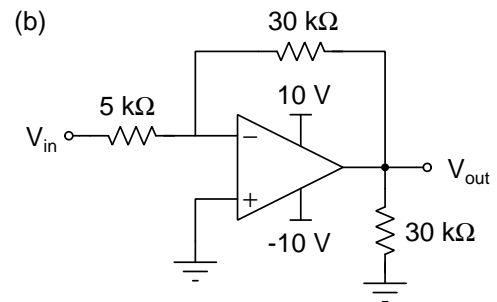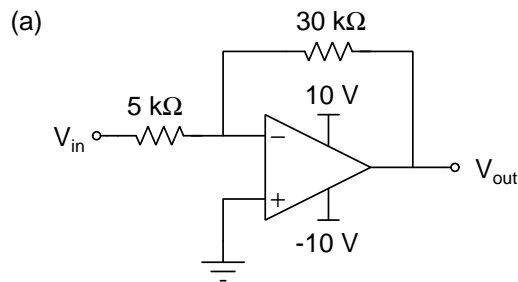**Problem 2:** For the OpAmp circuits below, calculate the output voltage,  $V_{out}$ , when the input voltage  $V_{in} = 1$  V. The OpAmps are ideal.



OpAmp	$V_{out}$	OpAmp	$V_{out}$
(a)		(b)	
(c)		(d)	
(e)		(f)	

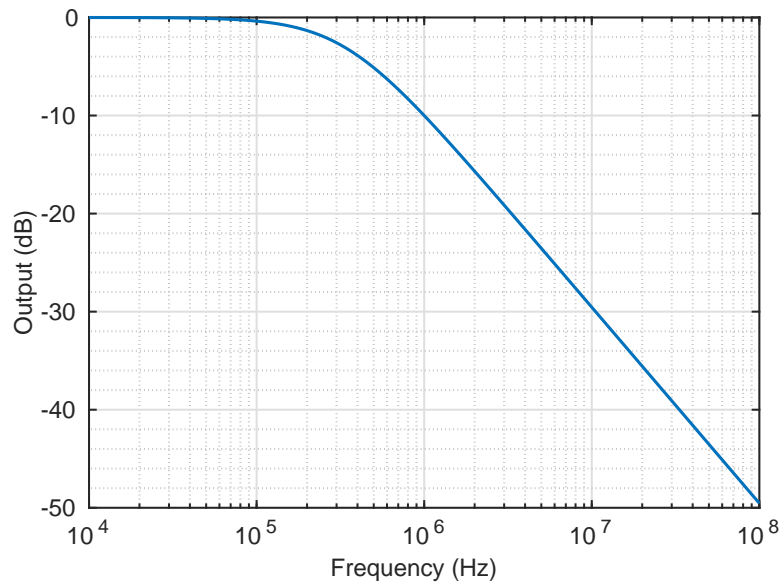**Problem 3:** The frequency response of a filter is shown below.



1. What type of filter is this?

- (a) Low pass filter
- (b) High pass filter
- (c) Band pass filter
- (d) Band reject filter
- (e) None of the above

2. What order filter is this?

- (a) 1st order filter
- (b) 2nd order filter
- (c) 3rd order filter
- (d) none of the above

3. What is the cut-off frequency? \_\_\_\_\_

4. When the input signal is a square wave with a period of  $1\ \mu\text{s}$ , what is the magnitude of the 3rd harmonic relative to the fundamental frequency at the output of the filter? \_\_\_\_\_

5. When the input signal is a square wave with a period of  $10\ \mu\text{s}$ , what is the magnitude of the 3rd harmonic relative to the fundamental frequency at the output of the filter? \_\_\_\_\_

6. When the input signal is a square wave with a period of  $100\ \mu\text{s}$ , what is the magnitude of the 3rd harmonic relative to the fundamental frequency at the output of the filter? \_\_\_\_\_

Blank page for calculations.

Name: \_\_\_\_\_

Blank page for calculations.

Name: \_\_\_\_\_

Blank page for calculations.

Name: \_\_\_\_\_