

ECE 214 — Exam #1


Estimated time for completion: ≤ 1.25 hour
5 March 2020

Rules of the Exam

- Rule 1:** The examination period begins at 9:30 am on Thursday, 5 March 2020, and ends at 10:45 am on Thursday, 5 March 2020.
- Rule 2:** The exam is worth 20% of your grade.
- Rule 3:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.
- Rule 4:** To receive credit for an answer, include the units along with the numerical answer.
- Rule 5:** Show all work - answers without supporting work will not receive credit.
- Rule 6:** Do not leave the room until you have completed the exam.

Name

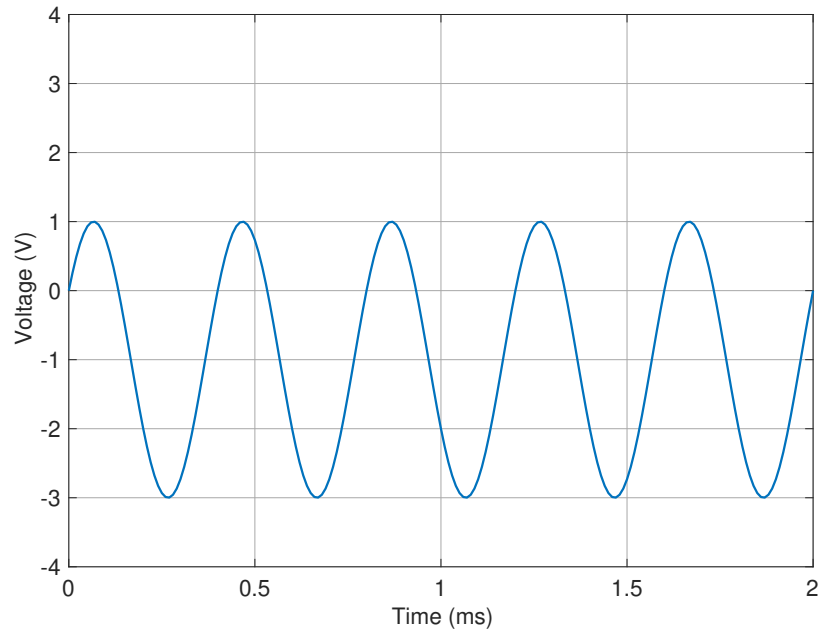Problem 1 (6 points): Consider the voltage signal $V(t)$ shown below:




This signal can be described as:

$$V(t) = A_1 \cos(\omega_1 t + \phi_1) + V_{DC1}.$$

1. What is A_1 ? _____
2. What is ω_1 ? _____
3. What is V_{DC1} ? _____
4. What is ϕ_1 in degrees? _____
5. What is ϕ_1 in radians? _____
6. If $V(t)$ is measured using a DVM with a $5\text{ M}\Omega$ input resistance, and set to measure an AC voltage, what voltage would the DVM measure? _____

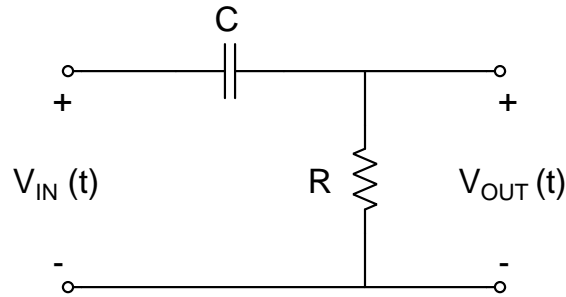Problem 2 (6 points): In the filter circuit shown below, $C = 400 \text{ pF}$ and $R = 80 \text{ k}\Omega$.



The voltage input signal $V_{IN}(t)$ is given by:


$$V_{IN}(t) = 5 \cos(9,940\pi t + 45^\circ) + 2 \text{ V},$$

and the voltage output signal $V_{OUT}(t)$ by:

$$V_{OUT}(t) = A_2 \cos(\omega_2 t + \phi_2) + V_{DC2}$$

1. What is A_2 ? _____
2. What is ω_2 ? _____
3. What is ϕ_2 ? _____
4. What is V_{DC2} ? _____
5. Is this circuit a high-pass, band-pass, band-reject, or low-pass filter? _____
6. If $V_{OUT}(t)$ is connected to an oscilloscope having an input resistance of $1 \text{ M}\Omega$ and an input capacitance of 13 pF , with a cable having a capacitance of 27 pF , what is the approximate value of A_2 that is measured? _____

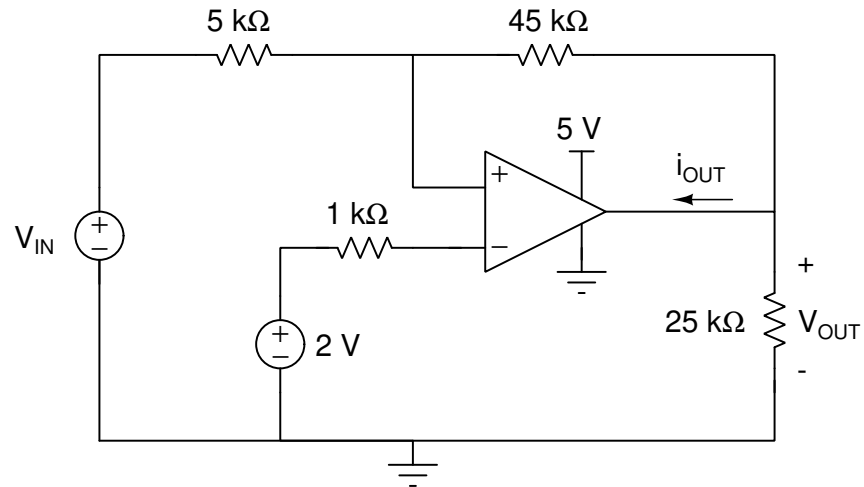Problem 3a (4 points): Consider the OpAmp circuit shown below. The OpAmp is ideal.




What type of circuit is this? Circle one: inverting amplifier, inverting amplifier with DC offset, noninverting amplifier, noninverting amplifier with DC offset, differentiator, integrator, Schmitt trigger.

Complete the table below:

V_{IN}	V_{OUT}	i_{OUT}
0 V		
1 V		
5 V		

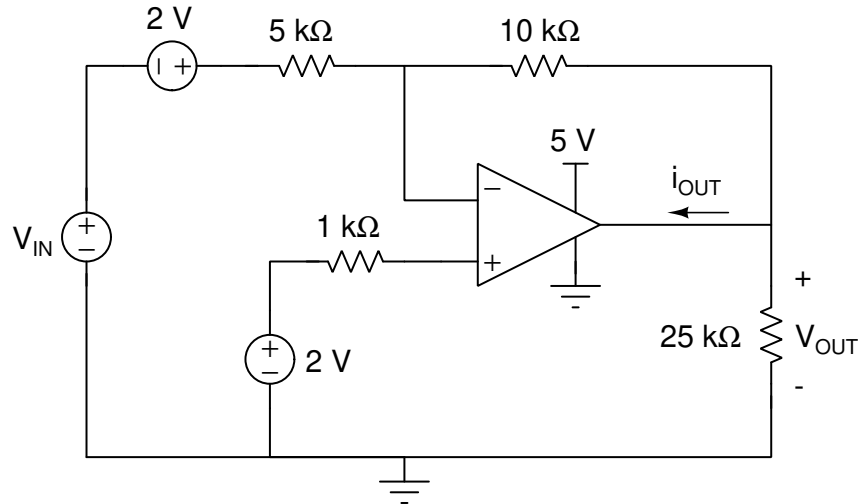Problem 3b (4 points): Consider the OpAmp circuit shown below. The OpAmp is ideal.




What type of circuit is this? Circle one: inverting amplifier, inverting amplifier with DC offset, noninverting amplifier, noninverting amplifier with DC offset, differentiator, integrator, Schmitt trigger.

Complete the table below:

V_{IN}	V_{OUT}	i_{OUT}
0 V		
1 V		
5 V		

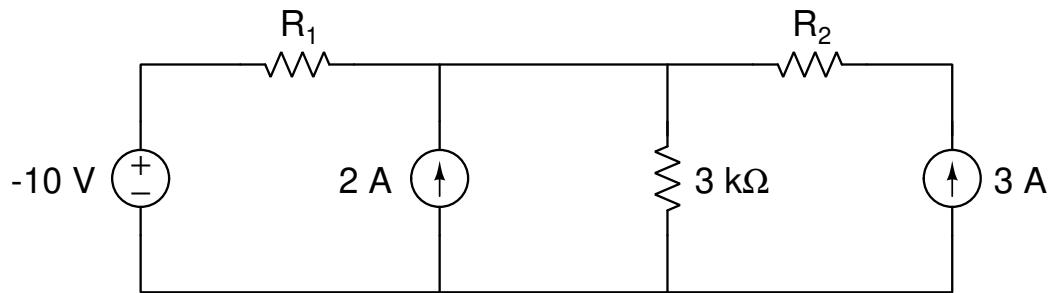Bonus Question (2 points): In the circuit below, the 2A source delivers no power and absorbs no power. The circuit dissipates a total of 320 W. Determine the values of R_1 and R_2 .



$R_1 =$ _____

$R_2 =$ _____

Blank page for calculations.

Name: _____

Blank page for calculations.

Name: _____