

32 in class
+ 2
34

ECE 214 — Exam #1

Estimated time for completion: ≤ 1.25 hour
5 March 2020


Rules of the Exam

- Rule 1:** The examination period begins at 9:30 am on Thursday, 5 March 2020, and ends at 10:45 am on Thursday, 5 March 2020.
- Rule 2:** The exam is worth 20% of your grade.
- Rule 3:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.
- Rule 4:** To receive credit for an answer, include the units along with the numerical answer.
- Rule 5:** Show all work - answers without supporting work will not receive credit.
- Rule 6:** Do not leave the room until you have completed the exam.

Answer Key

Name

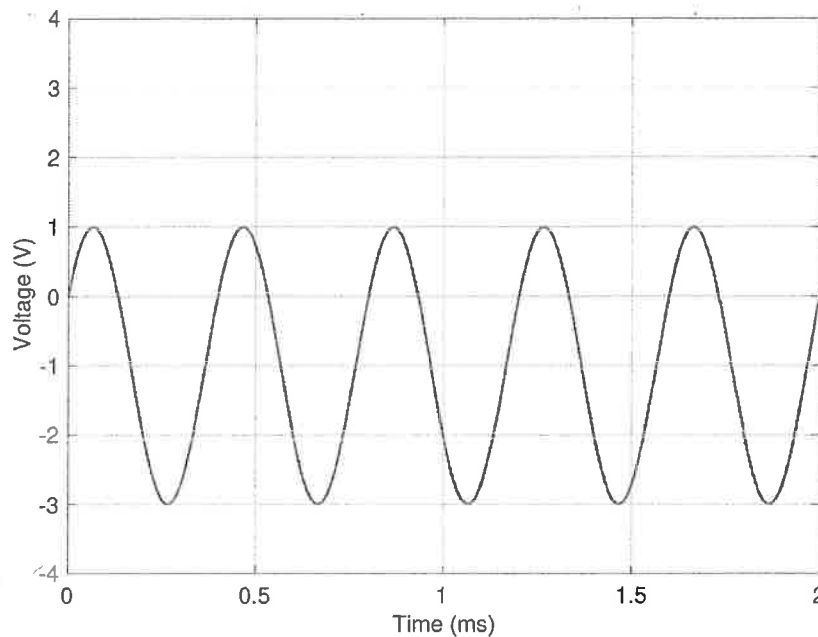Problem 1 (6 points): Consider the voltage signal $V(t)$ shown below:



This signal can be described as:

$$V(t) = A_1 \cos(\omega_1 t + \phi_1) + V_{DC1}.$$

$$T = 0.4 \text{ ms}$$

$$f = 2.5 \text{ kHz}$$

1. What is A_1 ? 2V

2. What is ω_1 ? 5000π or 15708 rad/s

3. What is V_{DC1} ? -1V

4. What is ϕ_1 in degrees? -60°

5. What is ϕ_1 in radians? $-\frac{\pi}{3}$ or -1.05 radians


$$V(t) = 0 = 2 \cos(\phi_1) - 1$$

$$2 \cos(\phi_1) = 1$$

$$\cos(\phi_1) = 1/2$$

6. If $V(t)$ is measured using a DVM with a $5 \text{ M}\Omega$ input resistance; and set to measure an AC voltage, what voltage would the DVM measure? $\frac{2}{\sqrt{2}} = 1.414 \text{ V}$

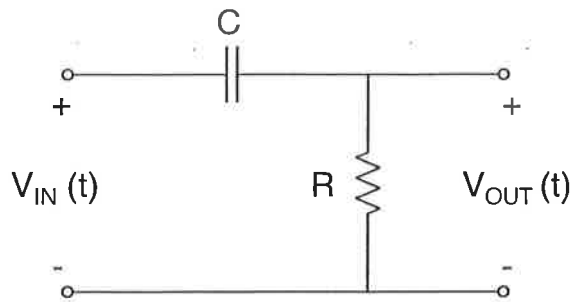Problem 2 (6 points): In the filter circuit shown below, $C = 400 \text{ pF}$ and $R = 80 \text{ k}\Omega$.



The voltage input signal $V_{IN}(t)$ is given by:

$$V_{IN}(t) = 5 \cos(9,940\pi t + 45^\circ) + 2 \text{ V},$$

$$= 5 \angle 45^\circ$$

$$\omega = 9940\pi$$

and the voltage output signal $V_{OUT}(t)$ by:

$$V_{OUT}(t) = A_2 \cos(\omega_2 t + \phi_2) + V_{DC2}$$

$$Z_C = -\frac{j}{\omega C} = -j80,000 = -j80 \text{ k}\Omega$$

1. What is A_2 ? 3.53 V

2. What is ω_2 ? 9940π or 31227.4

3. What is ϕ_2 ? 90°

4. What is V_{DC2} ? 0 V



$$V_{OUT}(t) = 5 \angle 45^\circ \left[\frac{80}{80 - j80} \right]$$

$$= 3.53 \angle 90^\circ$$

5. Is this circuit a high-pass, band-pass, band-reject, or low-pass filter? _____

6. If $V_{OUT}(t)$ is connected to an oscilloscope having an input resistance of $1 \text{ M}\Omega$ and an input capacitance of 13 pF , with a cable having a capacitance of 27 pF , what is the approximate value of A_2 that is measured? 3.24 V

$$40 \text{ pF} \Rightarrow Z_C = -j800 \text{ k}\Omega$$




$$\left(\frac{1}{80} + \frac{1}{1000} - \frac{1}{j800} \right)^{-1} = 73.4 - j6.8$$

$$73.8 \angle -5.3^\circ \text{ k}\Omega$$

$$5 \angle 45^\circ \left(\frac{73.8 \angle -5.3^\circ}{73.8 \angle -5.3^\circ - j80} \right) = 3.24 \angle 89.4^\circ$$

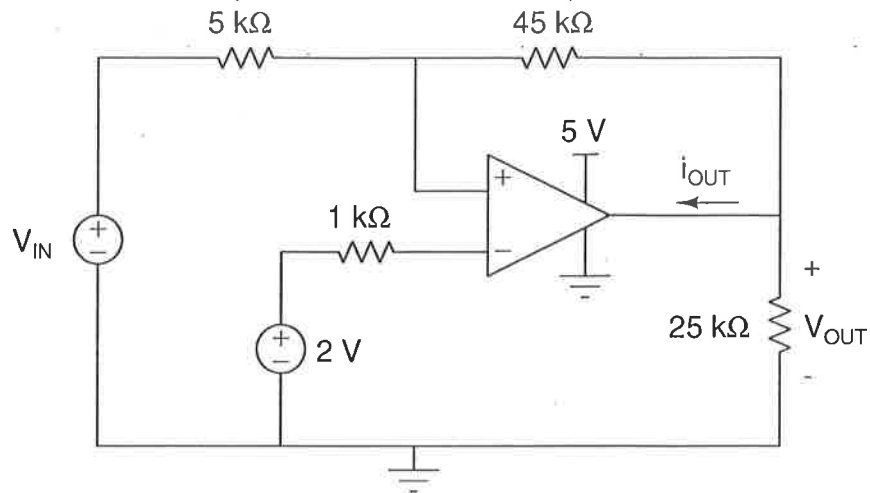Problem 3a (4 points): Consider the OpAmp circuit shown below. The OpAmp is ideal.



What type of circuit is this? Circle one: inverting amplifier, inverting amplifier with DC offset, noninverting amplifier, noninverting amplifier with DC offset, differentiator, integrator, Schmitt trigger.

Complete the table below:

V_{IN}	V_{OUT}	i_{OUT}
0 V	0	0
1 V	0	+200 μ A
5 V	5	-200 μ A

$$i_{OUT} = \frac{1}{50K}$$

$$i_{OUT} = -\frac{5}{25K}$$


$$\frac{V_{t1} - 2}{5K} = \frac{2 - 5}{45K} \Rightarrow 9V_{t1} - 18 = -3$$

$$V_{t1} = \frac{15}{9} V = 1.67V$$

$$\frac{V_{t2} - 2}{5K} = \frac{2}{45K} \Rightarrow 9V_{t2} - 18 = 2$$

$$V_{t2} = \frac{20}{9} V = 2.22V$$

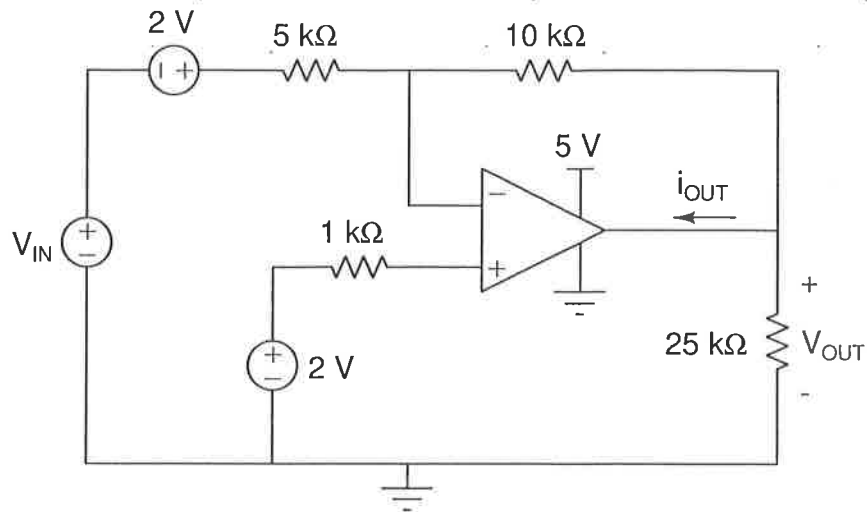Problem 3b (4 points): Consider the OpAmp circuit shown below. The OpAmp is ideal.



What type of circuit is this? Circle one: inverting amplifier, inverting amplifier with DC offset, noninverting amplifier, noninverting amplifier with DC offset, differentiator, integrator, Schmitt trigger.

Complete the table below:

V_{IN}	V_{OUT}	i_{OUT}
0 V	2 V	-80 μ A
1 V	0 V	+ 200 μ A
5 V	0 V	+ 467 μ A

$$i_{OUT} = -\frac{2}{25K}$$

$$i_{OUT} = \frac{2}{10K}$$


$$i_{OUT} = \frac{7}{15K}$$

$$\frac{V_{in}}{5K} = \frac{2 - V_{out}}{10K}$$

$$2V_{in} = 2 - V_{out}$$

$$V_{out} = 2 - 2V_{in}$$

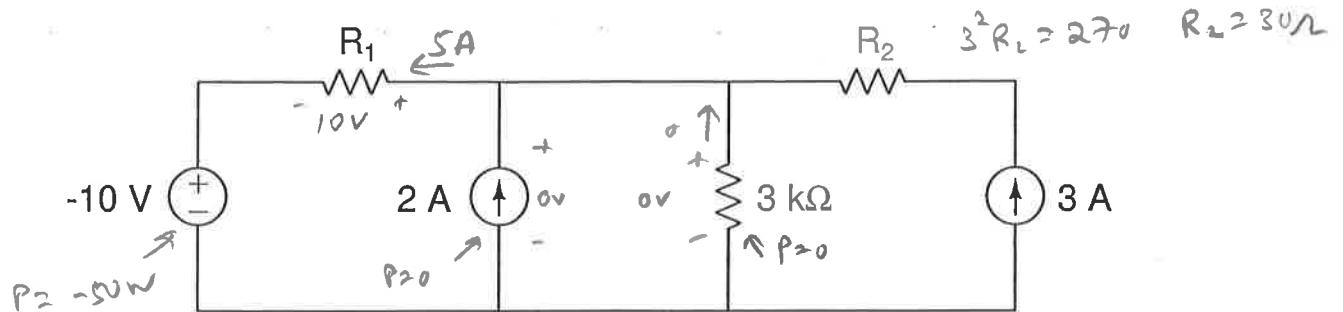Bonus Question (2 points): In the circuit below, the 2A source delivers no power and absorbs no power. The circuit dissipates a total of 320 W. Determine the values of R_1 and R_2 .



$$R_1 = \underline{2\Omega}$$

50W

$$R_1 = \frac{10V}{5A} = 2\Omega$$

$$R_2 = \underline{30\Omega}$$

270W

Blank page for calculations.

Name: _____

Blank page for calculations.

Name: _____