

Remaining Topic

- Semiconductor Memory
 - Overall structure of DRAM and SRAM
 - Flash memory

Classifications

	<u>Volatile</u>	<u>Speed</u>	<u>Density</u>
SRAM	Yes	High	Moderate
DRAM	Yes	Moderate	High
ROM	No	High	Moderate
EPROM	No	Low	Low
Flash	No	Low	High
MRAM	No	High	Moderate
FeRAM	No	High	Moderate

“Ware-out” Issue

	<u>Volatile</u>	<u>Speed</u>	<u>Density</u>
SRAM	Yes	High	Moderate
DRAM	Yes	Moderate	High
ROM	No	High	Moderate
EPROM	No	Low	Low
Flash	No	Low	High
MRAM	No	High	Moderate
FeRAM	No	High	Moderate



Memory Classification


Stand Alone Memory

- DRAM, ROM, SRAM, FLASH, EPROM
- MRAM, FeRAM



Embedded Memory

- SRAM for cache
- DRAM
- ROM

4Gb DRAM

 


AMD Dual-Core Athlon

  

Memory Market



SIA Memory Market Summary

 Historical Cost of Computer Memory and Storage




Memory Density

Cell Size

 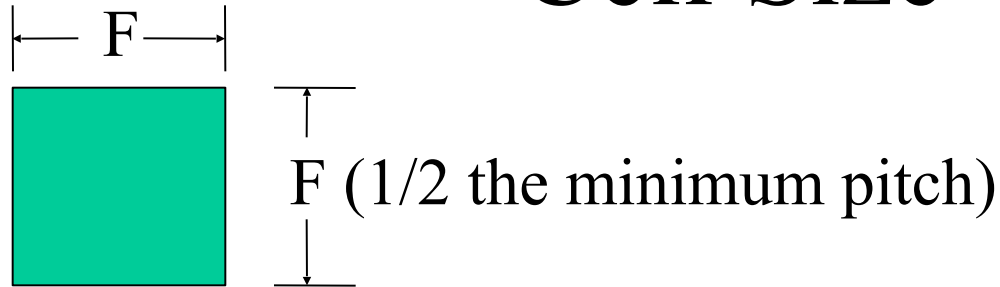

SRAM 6-T cell:
40-100 F^2 cell

 DRAM 1-T, 1-C cell:
5-10 F^2 cell; most common $8F^2$ cell




Memory Circuits

Memory Core - typically stores 1-bit
- can have multilevel cores)


Peripheral Circuits

- row and column decoders
- sense amplifiers
- column precharge circuits
- data buffers
- read/write (R/W) circuits
- ...


Typical Memory Organization

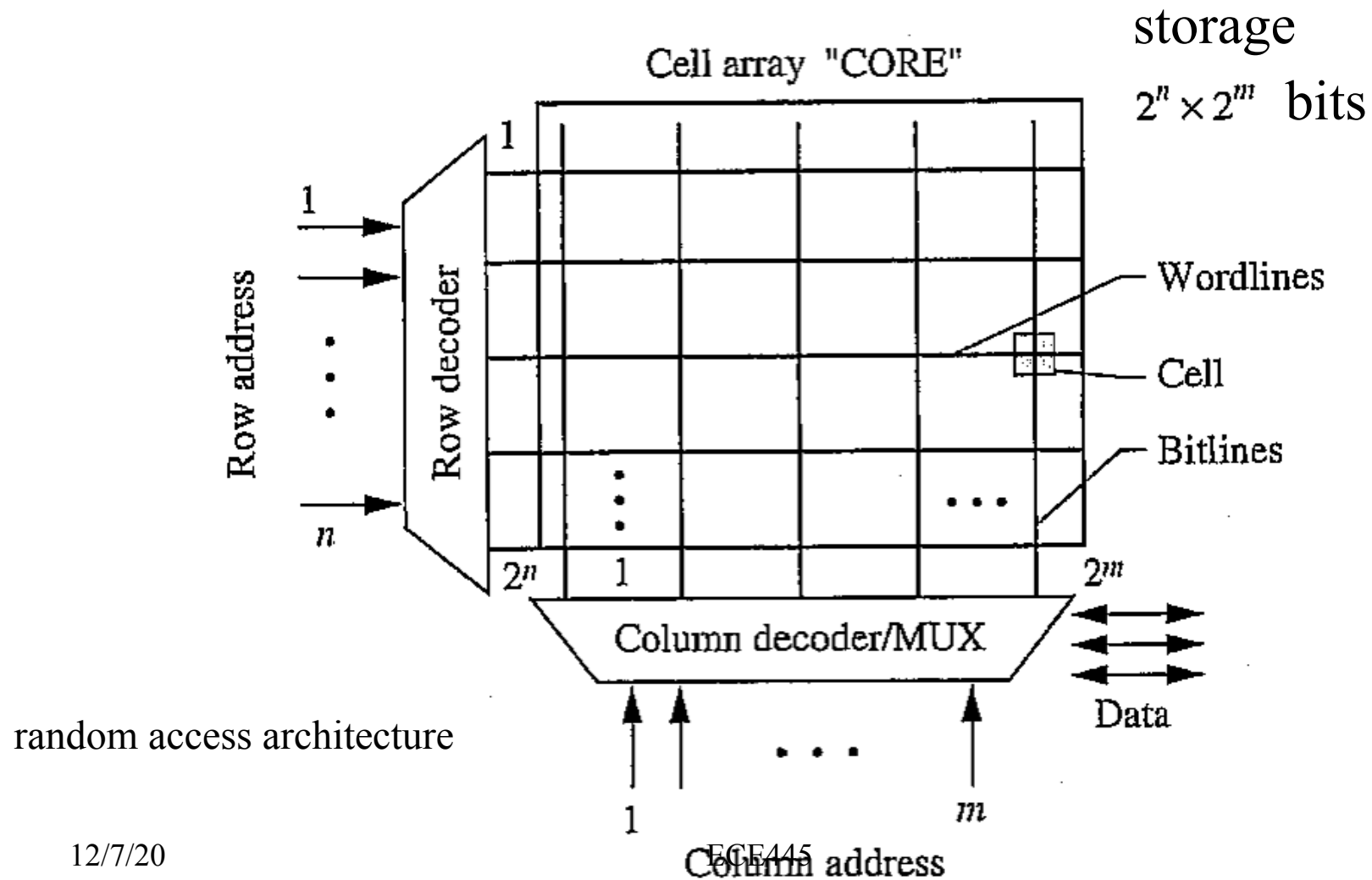

Row Decoder (n=2)

 

(a) AND-based decoder

 

(b) NOR-based decoder

Cascade Decoder

An n-bit decoder $\rightarrow 2^n$ logic gates each with n inputs



For n=6 \rightarrow requires 64, 6-input NAND gates and 64 Inverters

To minimize delay caused by large series resistances \rightarrow cascade


- predecode stage
- final decode stage

Allows intermediate signals from the predecode stage to be reused by the final decoding stage


Alternative 6-input NAND

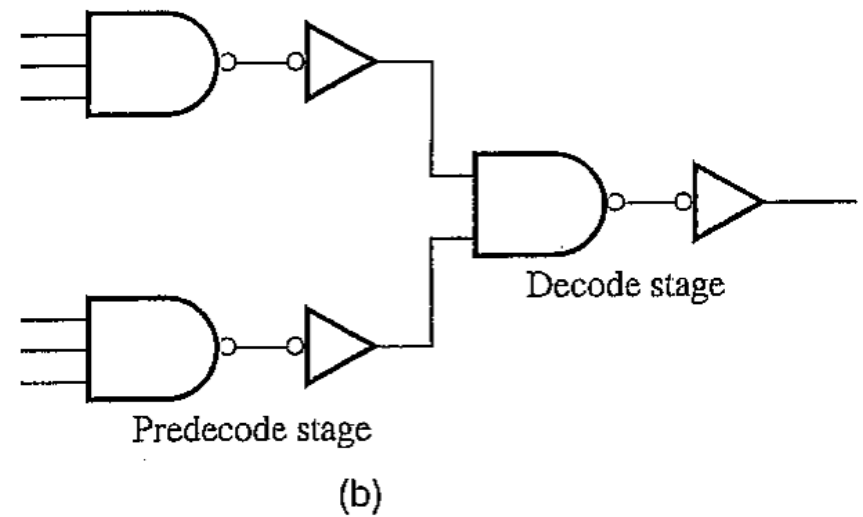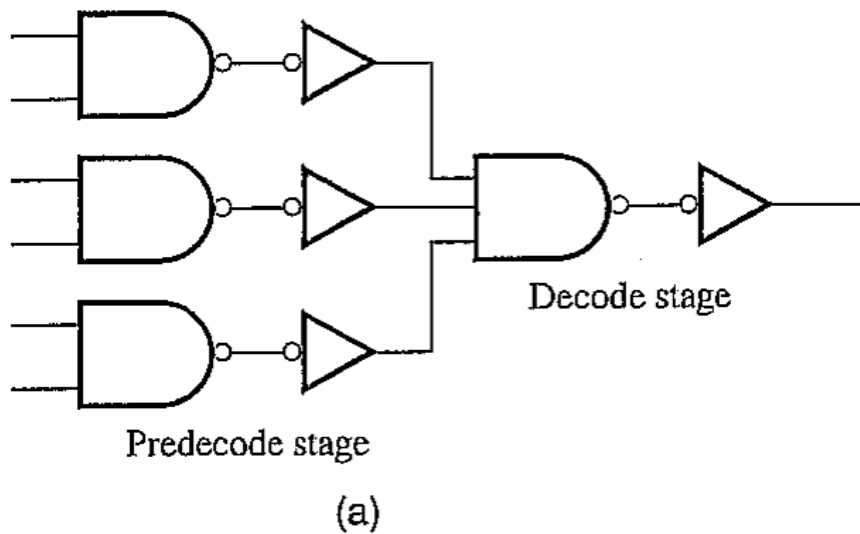

Reuse of Intermediate Signals

 

Sizing Using Logical Effort

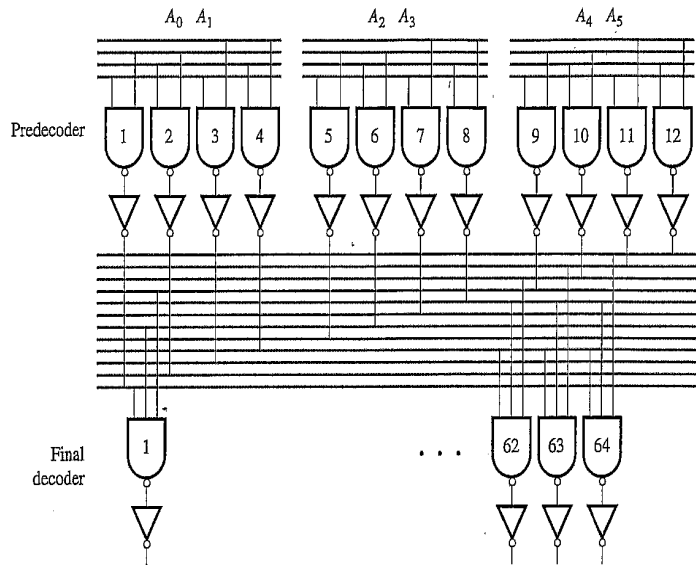


Size the decoder assuming:

- normalized output load = 1
- fan-out = 4


Work backwards from the output to the input:

- Normalized output has a size =
- Inverter input capacitance =
- The Logical Effort of the 3-input NAND =
- Input capacitance of 3-input NAND =
- Branching effort at output of predecoder =
- Input capacitance of the inverter =
- The 2-input NAND has an input capacitance =

Decoder Size by Logical Effort

 


1T DRAM Cell

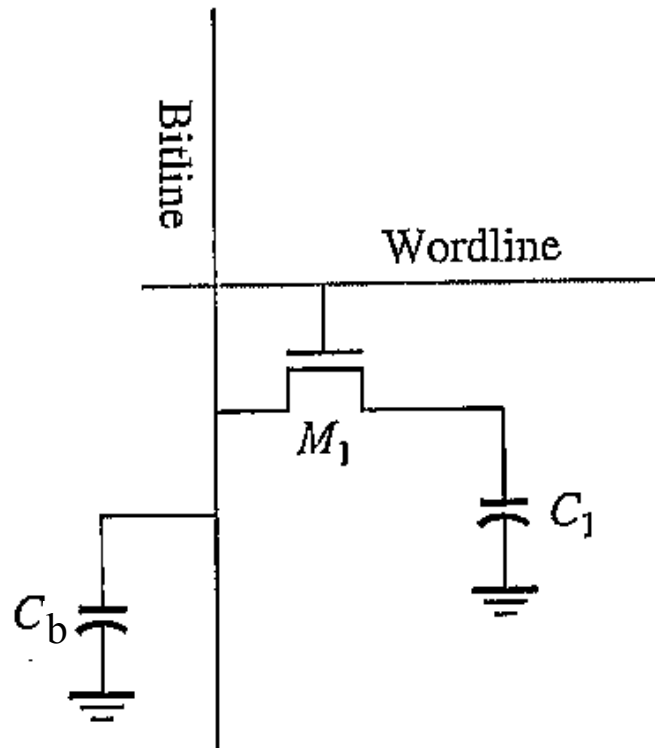

DRAM Trench Capacitor

 Extendibility of Established Device Structures




12/7/20

PC 445


20

DRAM - Dynamic Circuit

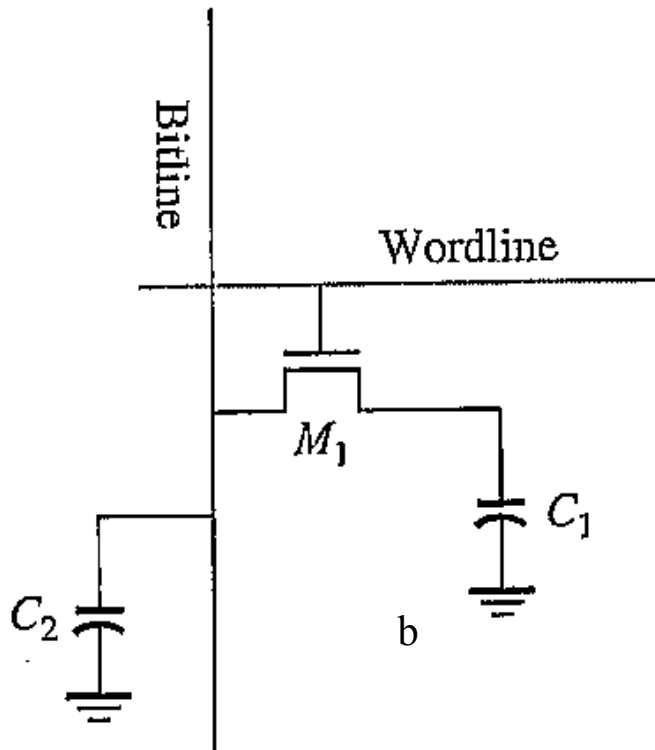

- Destructive Read - requires rewrite after every read
- Leakage \rightarrow requires refresh cycle

DRAM Array Configuration

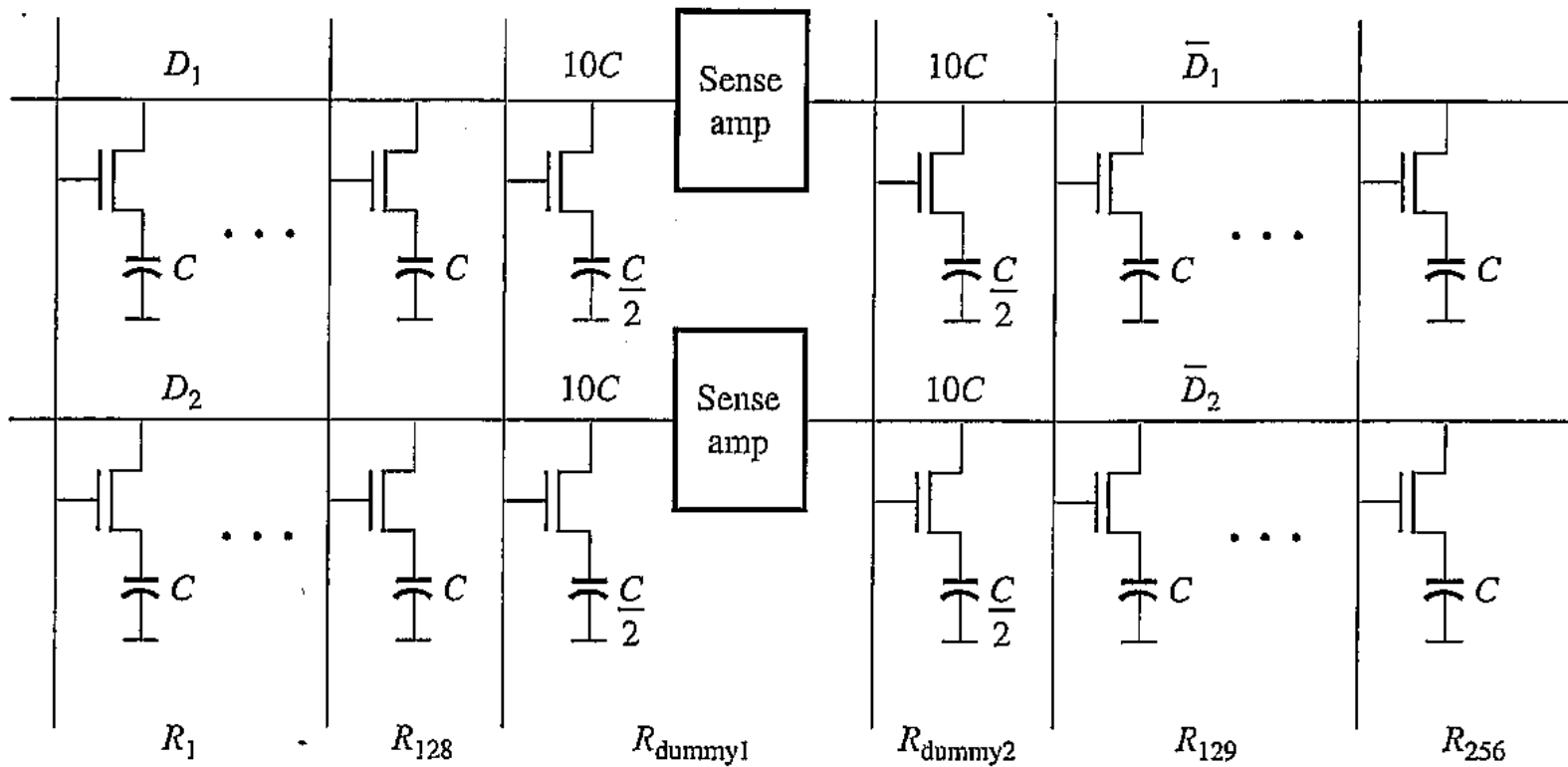

Redundancy

Redundancy is always used on standalone DRAMs and frequently for embedded DRAMs.

Implemented via on chip fuses in which fuses are blown either by a laser pulse or by an electrical pulse during wafer test.

Normally a few rows and columns of redundancy are offered on a large DRAM embedded macro. Smaller macros require less redundancy (or no redundancy)

Redundancy can also be implemented to some extent in the logic part of the circuits. To implement a spare decoder, for example, switches can be used that shift all decoder connections by one to bypass the faulty decoder.

Memory Standards

Most memory standards are controlled by the **JEDEC** Solid State Technology Association (Once known as the **Joint Electron Device Engineering Council**). JEDEC is the semiconductor engineering standardization body of the Electronic Industries Alliance (EIA), a trade association that represents all areas of the electronics industry and was originally created in 1960 to cover the standardization of discrete semiconductor devices and later expanded in 1970 to include integrated circuits.

JEDEC does its work through its 48 committees/ subcommittees that are overseen by the **JEDEC** Board of Directors. Presently there are about 300 member companies in **JEDEC** including both manufacturers and users of semiconductor components and others allied to the field.

DRAM Architecture

More than 10 Different Types of DRAM

Page Mode DRAM

Fast Page Mode DRAM

Extended Data Output DRAM

Burst Extended Data Output DRAM

Enhanced DRAM

Synchronous DRAM

PC100 Synchronous DRAM

Enhanced Synchronous DRAM

Double Data Rate DRAM

Direct Rambus DRAM

Synchronous Link DRAM

.....

DRAM

FPM DRAM

EDO DRAM

BEDO DRAM

EDRAM

SDRAM

PC100 SDRAM


ESDRAM

DDR DRAM

DRDRAM

SLDRAM


SRAM (Static RAM) Cell

 


(a)

Basic SRAM Cell

Voltage Transfer Characteristics

 

6-T Configuration

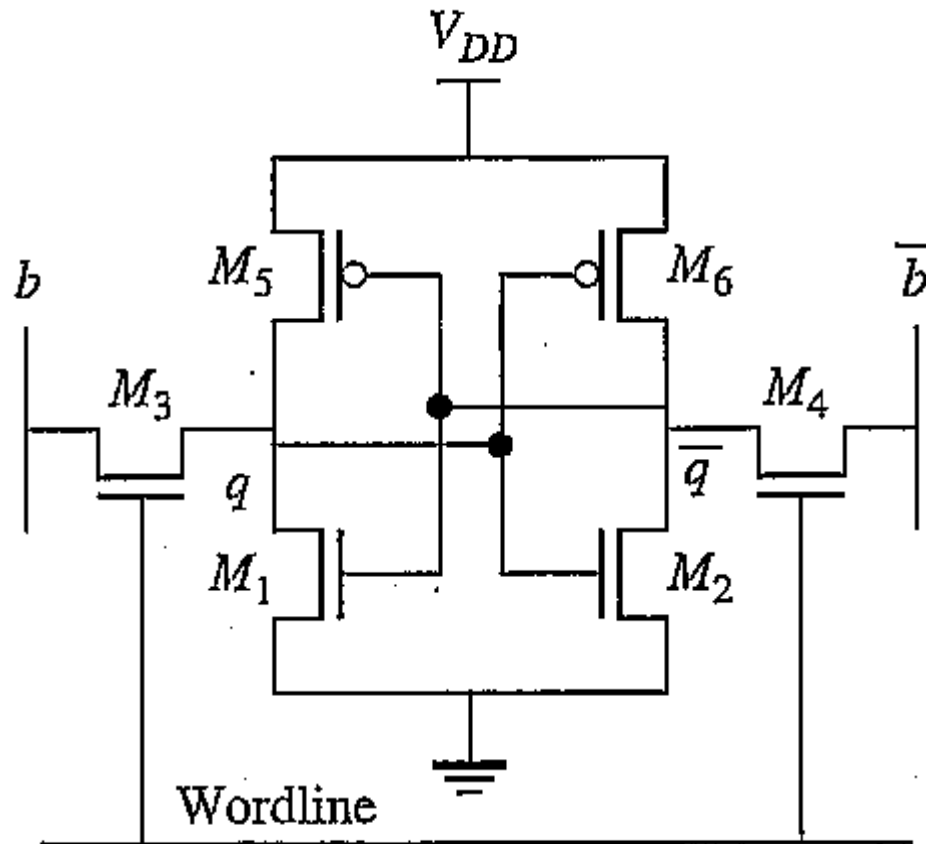


Cell Design Considerations

1. Minimize Cell Area \leftrightarrow Increase cell density
 - replace load resistors (M5 and M6) with transistors
 - utilize TFTs for M5 and M6
 - reduce wasted area
2. Minimize static power \rightarrow Increase V_t and sub- V_t slope
3. Differential bitlines \rightarrow improved noise immunity

SRAM Array (simplified)



$$C_{\text{WORD}} = 2 (C_G + C_{\text{WIRE}}) \times \# \text{ columns}$$
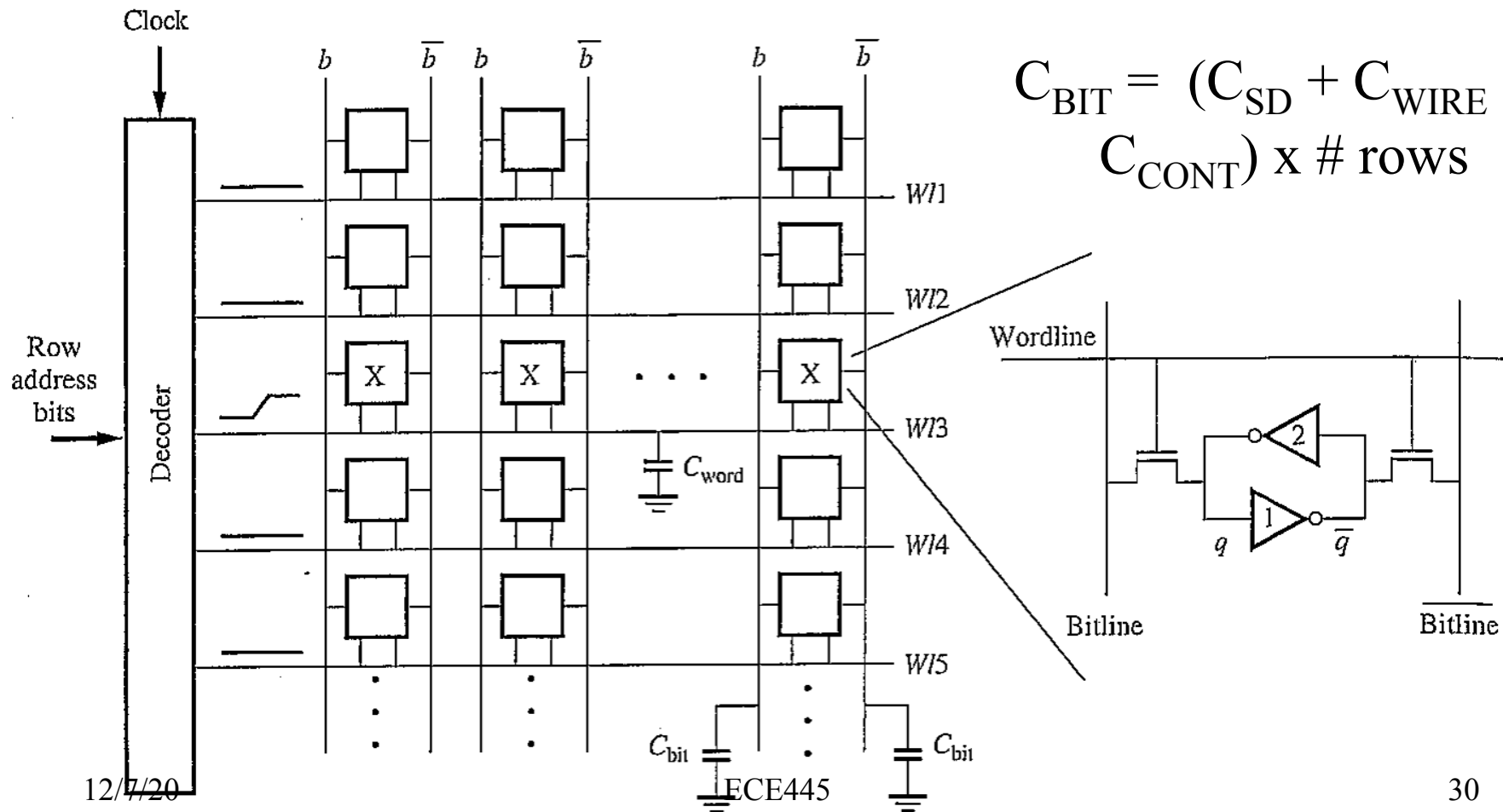
$$C_{\text{BIT}} = (C_{\text{SD}} + C_{\text{WIRE}} + C_{\text{CONT}}) \times \# \text{ rows}$$



12/7/20

SRAM Write Operation

  

1. Force either b or \bar{b} low
2. Turn on appropriate word line
3. Node q or \bar{q} is driven low causing the state to switch


Transistor Sizing Guidelines

1. During read: need to ensure stored value is not disturbed – voltage can not drop below V_S
2. Make conductance of M1, M2 greater than M3, M4
3. Need to supply enough I_{CELL} to discharge C_{BIT} sufficiently in 20-30% of a clock cycle
4. Can estimate I_{CELL}

$$I_{CELL} = C_{BIT} \Delta V / \tau$$



5. During write: make conductance of M3, M4 greater than M5, M6

Cell Layout

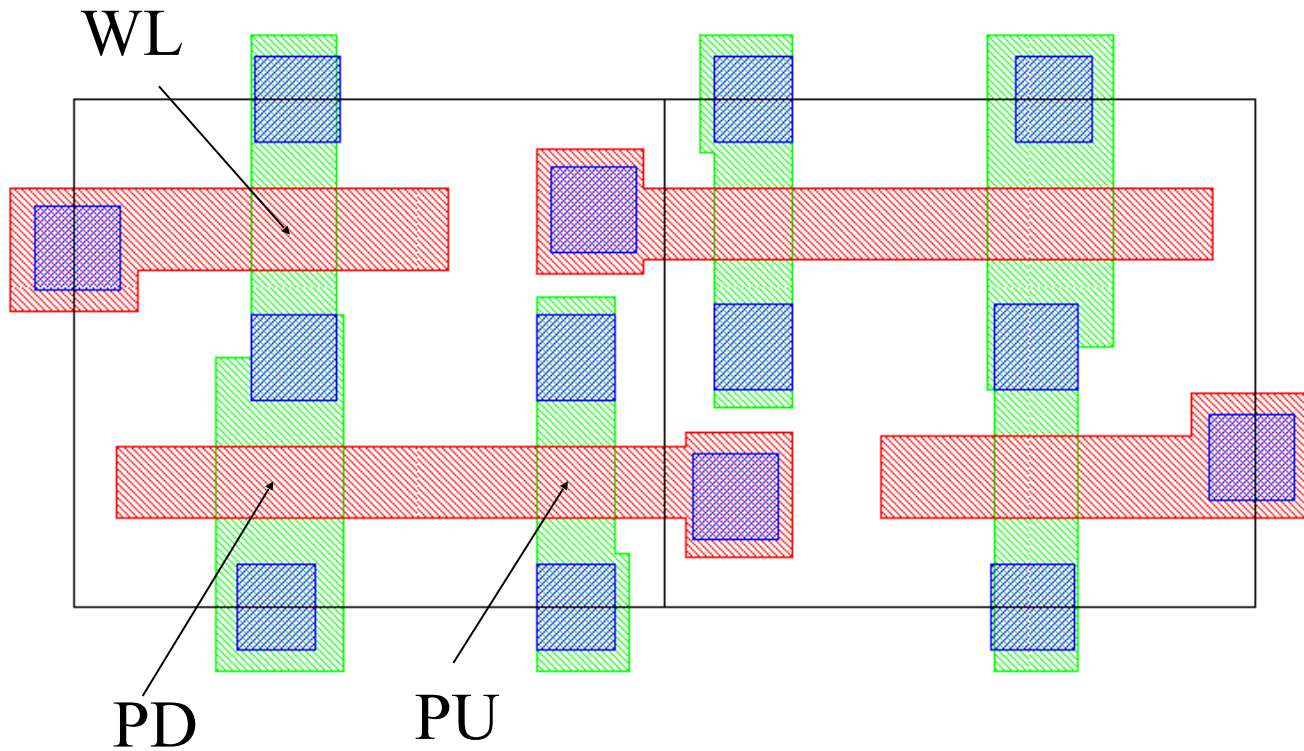

Column Pull-up Circuitry

Dynamic Logic Precharge P

 
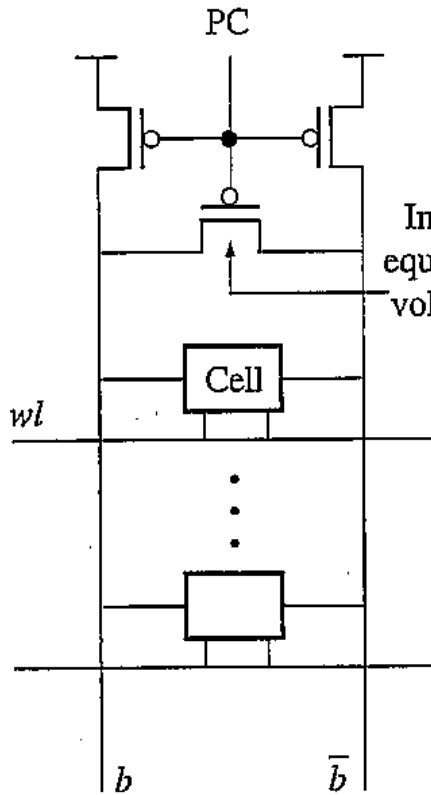


12/7/20

(a)

seudo-NMOS Precharge



Important to equalize bitline voltage before reads

  

ECE445


(b)

NMOS Saturated Enhancement Load

 
 


(c)


Write Driver Circuitry

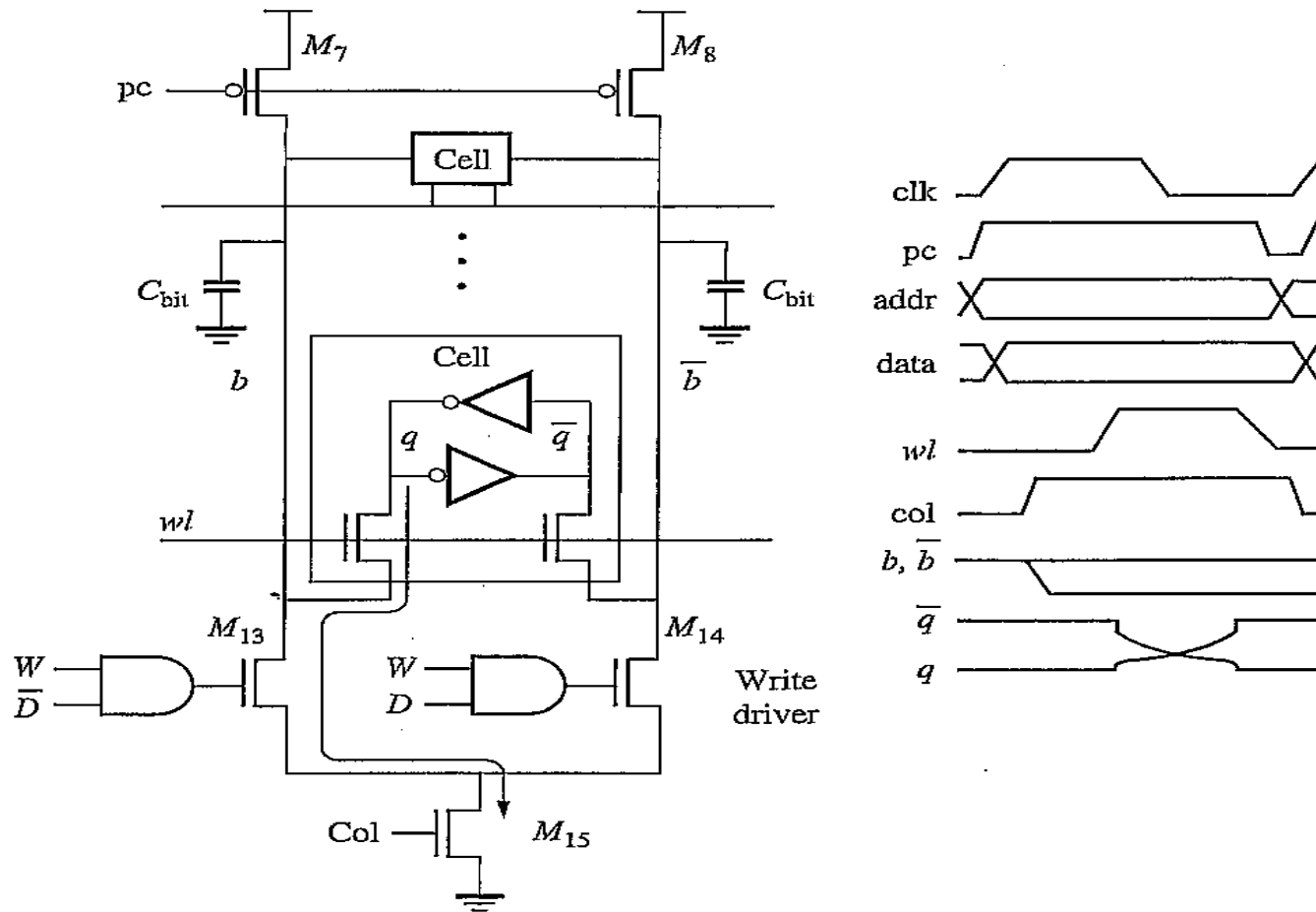


Basic Read Circuitry

 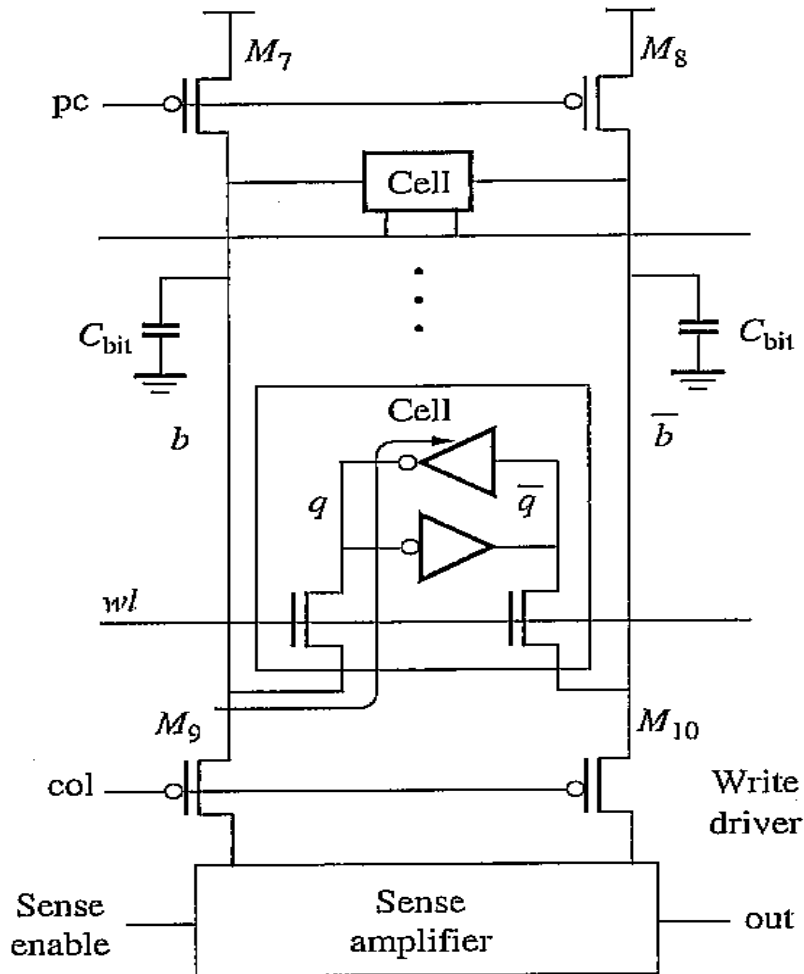

Detection of '0' and '1'

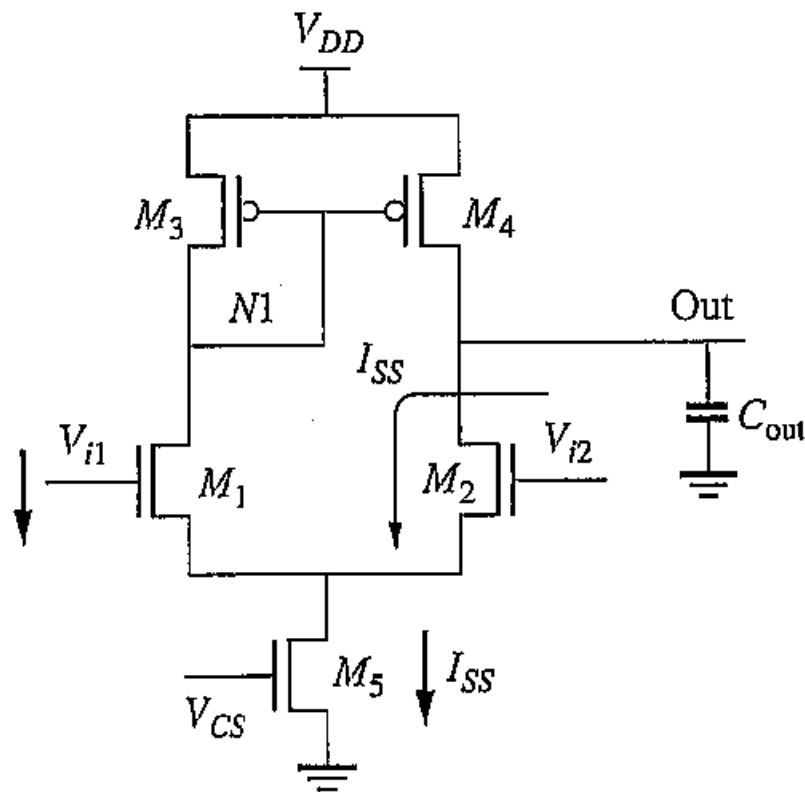


(a) Discharging output

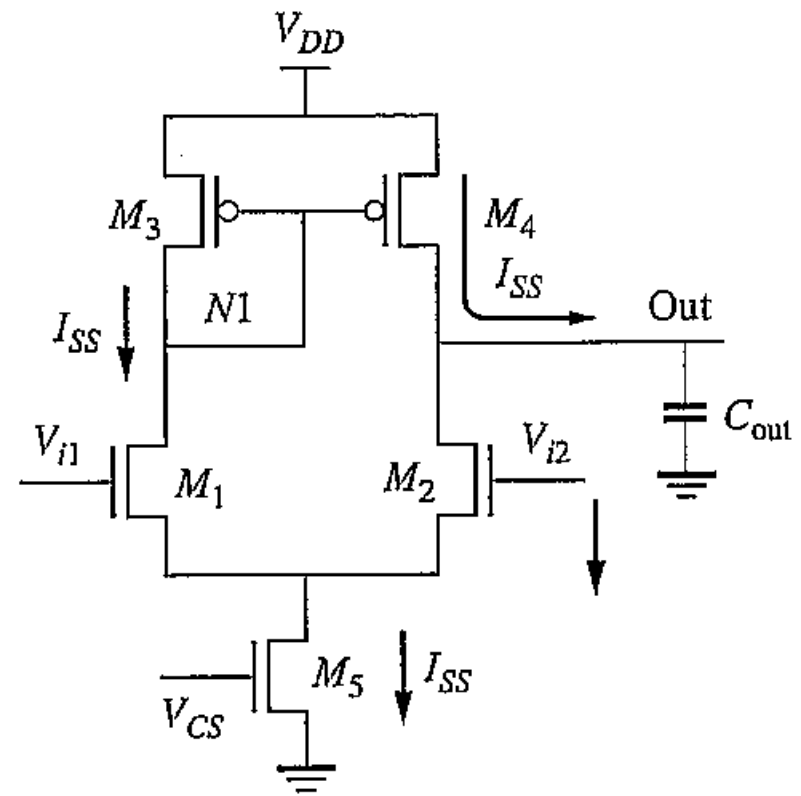


(b) Charging output

Memory Architecture


Basic Memory Architecture

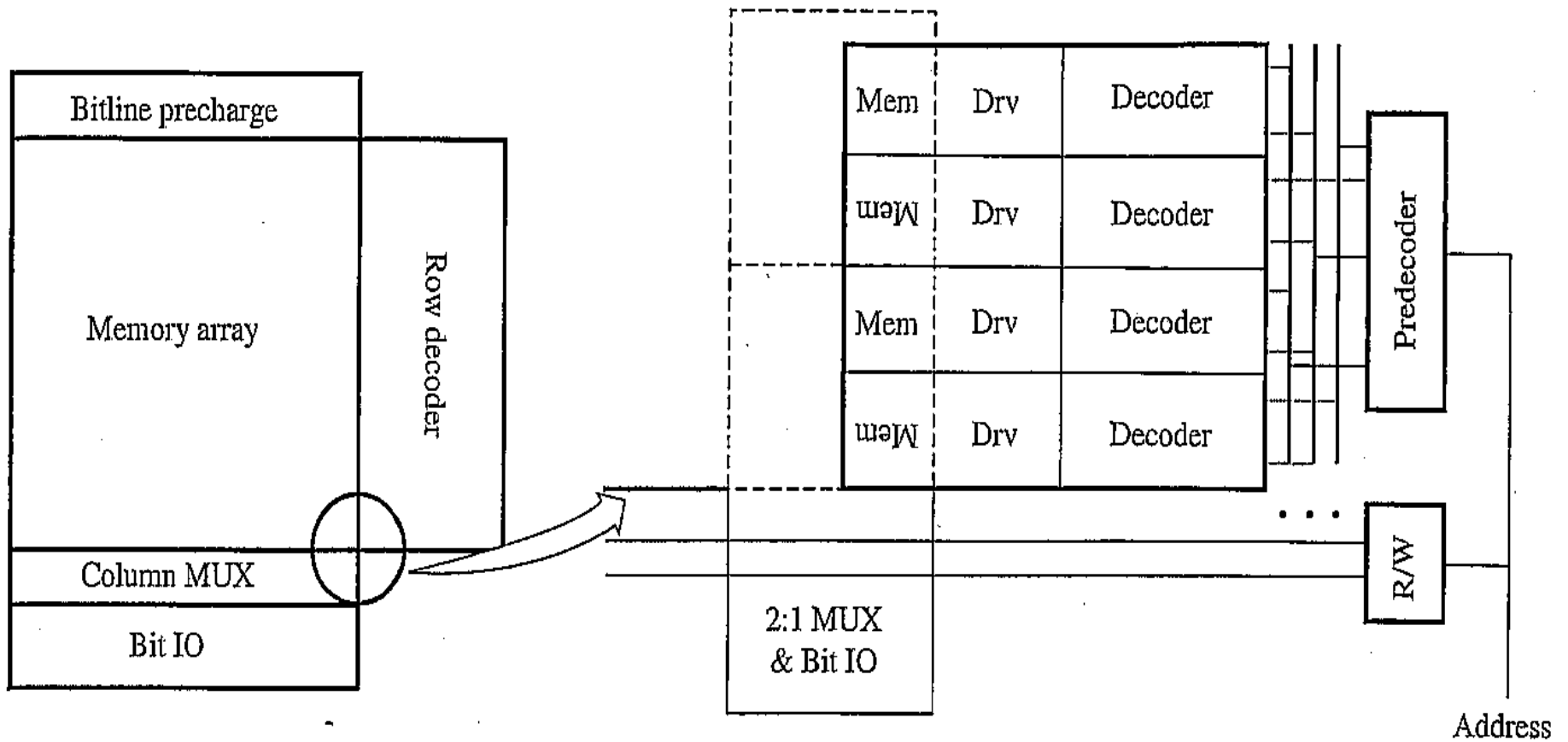

Partitioning - Divided Wordline

 

Partitioning – Divided Bitline

 

Applications

Read / Write Non-volatile Memory

- USB memory sticks
- Digital cameras
- MP3 players
- ...

10^5 R/W operations


1T cell implementation of E²PROM

Two architectures


- NAND
- NOR

Flash Memory


Dual-Gate Structure

 


Symbol

 

Schematic Representation

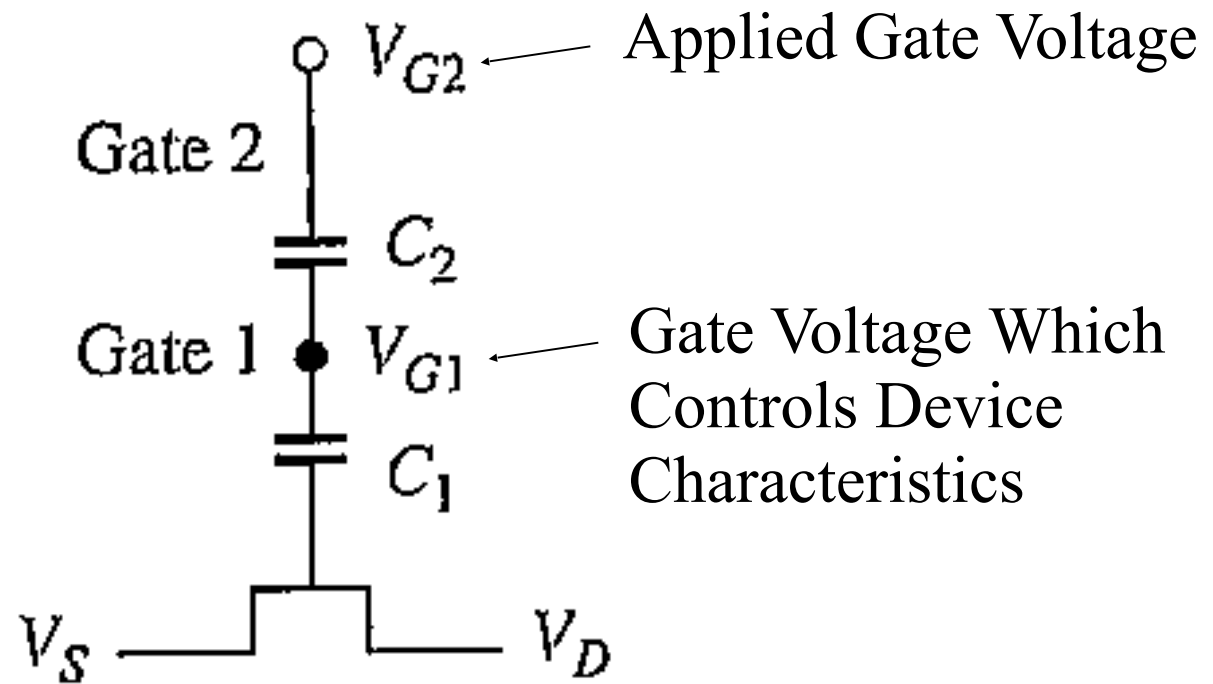


Capacitive Divider at Gate

 

$$\Delta V_{G1} = \Delta V_{G2} \frac{C_2}{C_1 + C_2}$$

To Turn The Device On

 


$$V_{G1} > V_t$$

$$\Rightarrow V_{G1} = V_{G2} \frac{C_2}{C_1 + C_2} > V_t$$

$$\Rightarrow V_{G2} > V_t \frac{C_1 + C_2}{C_2}$$


Device Operation

 

Device operation relies on the ability to store and remove charge from the floating gate → namely node V_{G1}

Write Process

 Write process relies on “Hot Carrier Injection” (HCI)




- Raise V_{G2} and $V_{DS} \gg VDD$
- Avalanche breakdown of Drain/Substrate Junction
- Electrons are injected through the gate oxide onto the floating gate
- Self-terminating process because V_{G1} decreases as electrons are injected onto the floating gate


Example

Assume $C_1 = C_2 = C$

$V_{DD} = 5V$, $V_T = 1V$

 


(a) Initial state

 


(b) After applying 10 V

 Example

Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$




(a) Initial state

 


(b) After applying $10V$

 Example


Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$



(a) Initial state

 

(b) After applying 10 V

 


(c) After programming


Program by applying $V_{DS} = 10V$

 Example


Assume $C_1 = C_2 = C$
 $V_{DD} = 5V, V_T = 1V$



(a) Initial state

 

(b) After applying 10 V

 


(c) After programming

Program by applying $V_{DS} = 10V$


Assume V_{G1} drops to 2V

 Example

Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$




(c) After programming

 

Reduce gate voltage $V_{G2} = 0V$

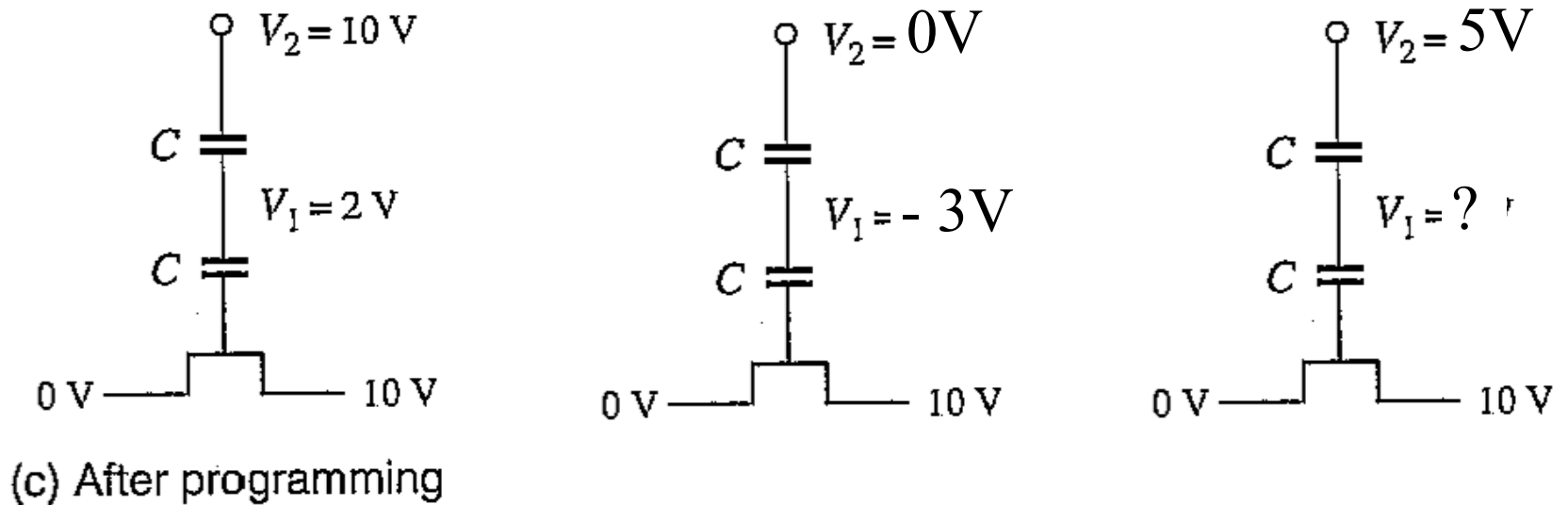Example


Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$





Raise gate voltage $V_{G2} = V_{DD}$

 Example

Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$




(c) After programming

  



Raise gate voltage $V_{G2} = V_{DD}$
TRANSISTOR IS STILL OFF!!
Have written a “1”

 Example

Assume $C_1 = C_2 = C$
 $V_{DD} = 5V$, $V_T = 1V$



(c) After programming

  


Raise gate voltage $V_{G2} = V_{DD}$
TRANSISTOR IS STILL OFF!!

To turn the transistor on: $V_{G2} = 8V$


Different Methods to Erase

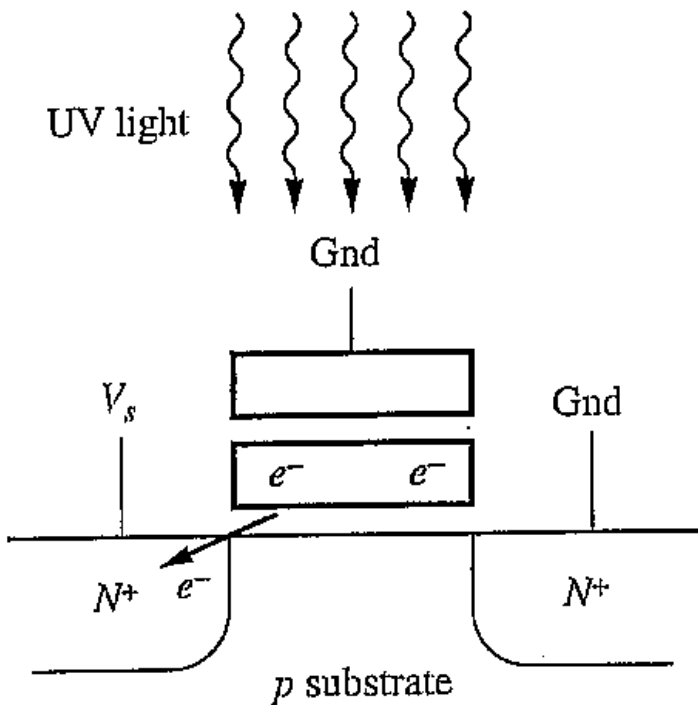In a conventional EPROM, UV light is used generate e/h pairs in the SiO₂ dielectric making the dielectric conductive



(b) Erase process — UV light


Different Methods to Erase

 


In a E²PROM, the charge is removed by “Fowler-Nordheim” (FN) transport.

When the field across the oxide exceed ~ 10 MV/cm, electrons can tunnel across the oxide


1T Cell - FLASH

 

NOR Array

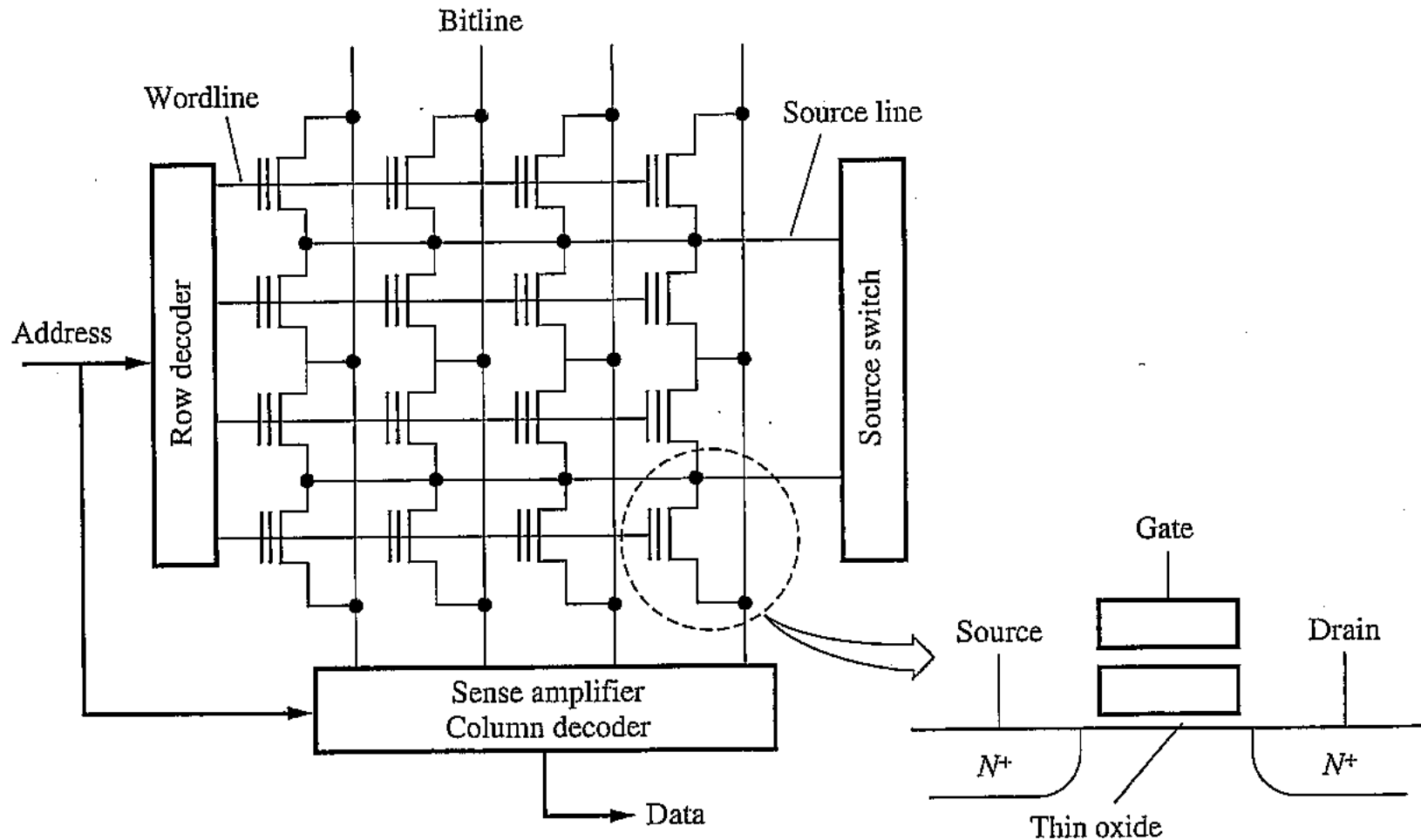

Write – “hot carrier injection”

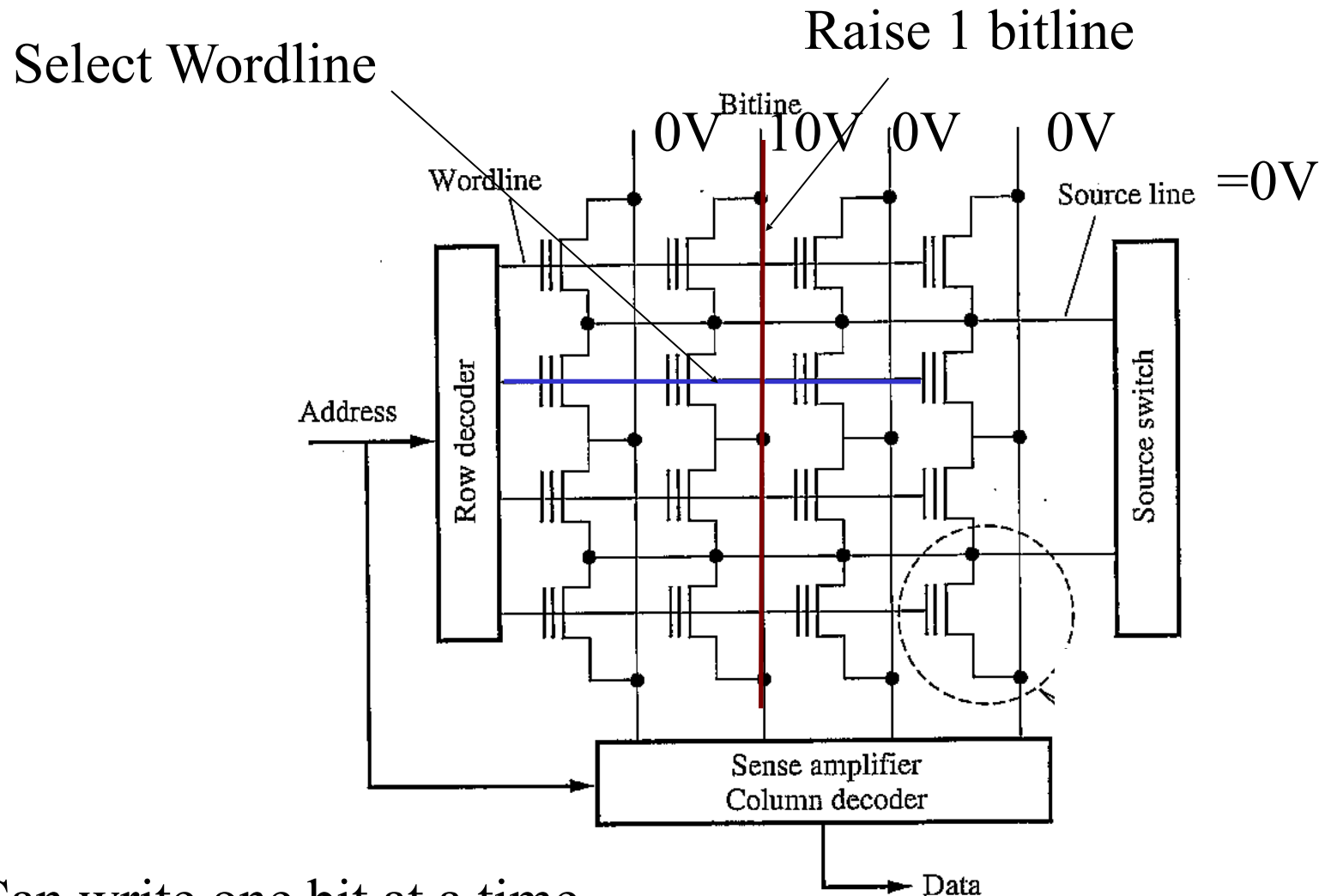

Can write one bit at a time


12/7/20

ECE445

66


Erase – “Fowler-Nordheim Tunneling”

0V on Wordlines

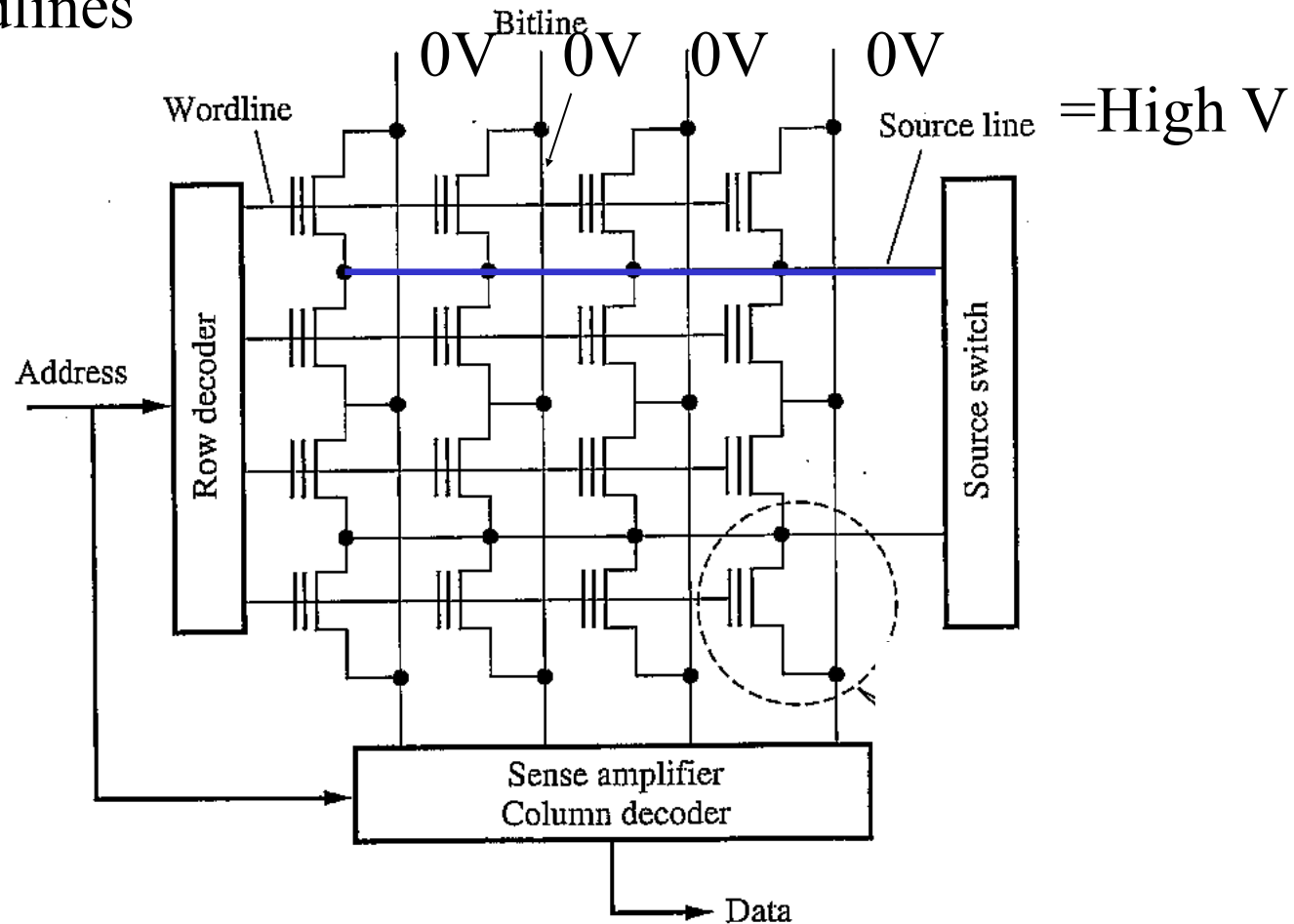


Erase – “Fowler-Nordheim Tunneling”

0V on Wordlines

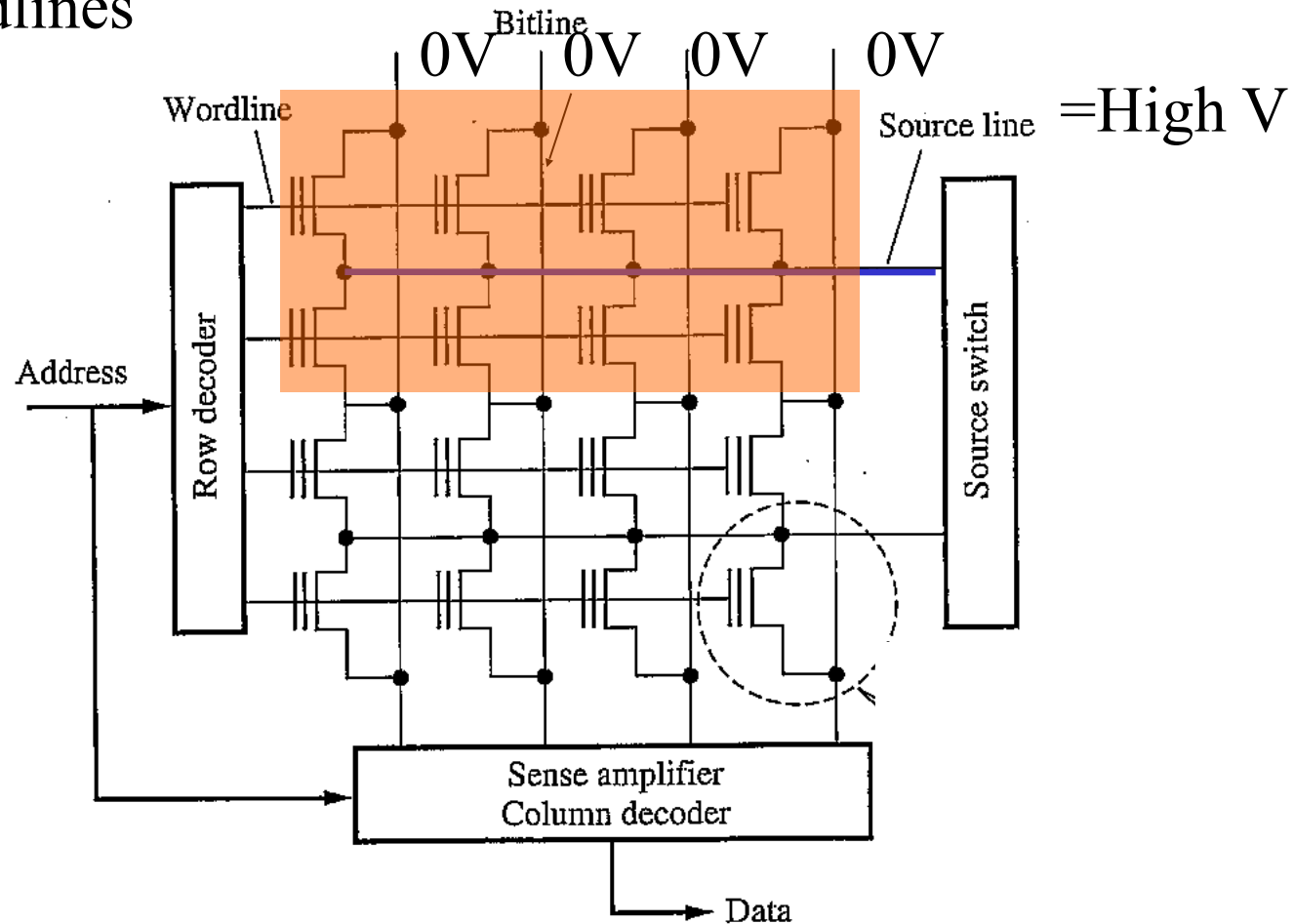

All transistors connected to the source line are erased simultaneously → FLASH



Write / Erase

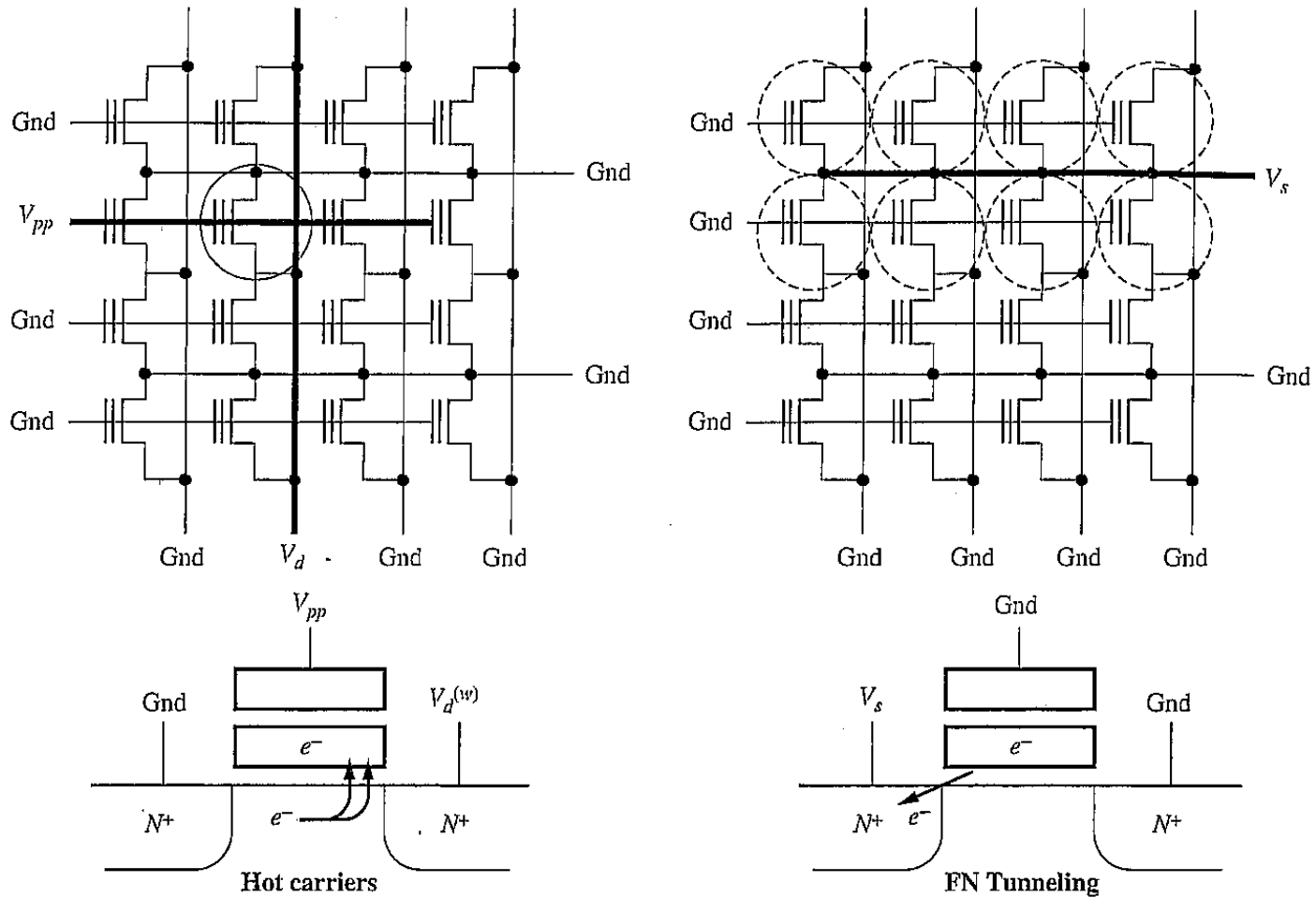

(a) Write operation

(b) Erase operation (blockwise only)

Read Operation

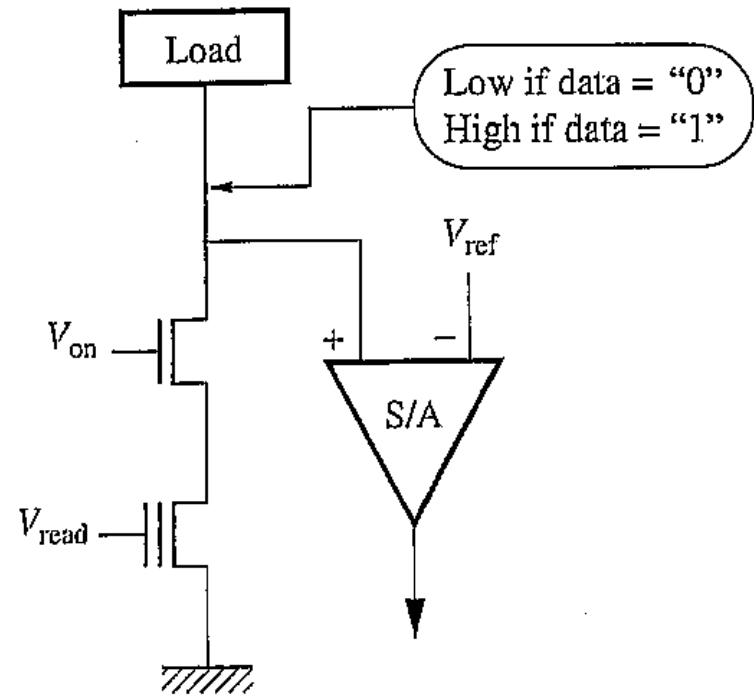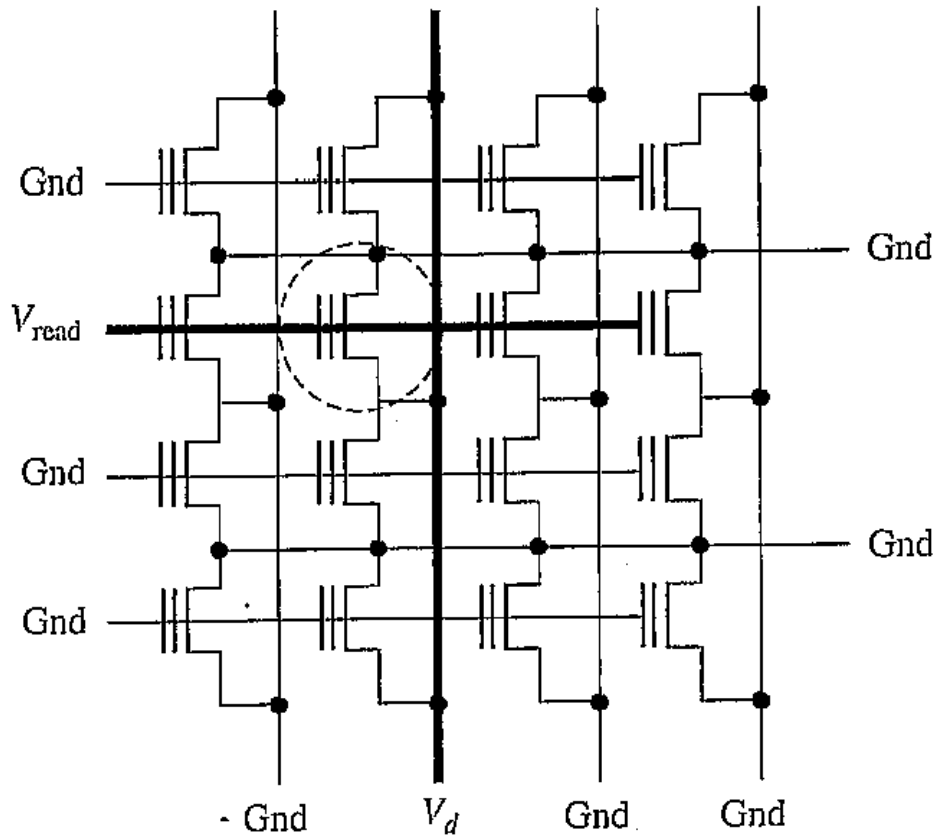


Precharge bitline
 Source line \rightarrow Gnd
 Enable wordline

NAND vs NOR Arrays

	Write	Read	Erase	Density
NAND	Fast	Slow	Fast	High
NOR	Slow	Fast	Slow	Low

NAND Flash Array

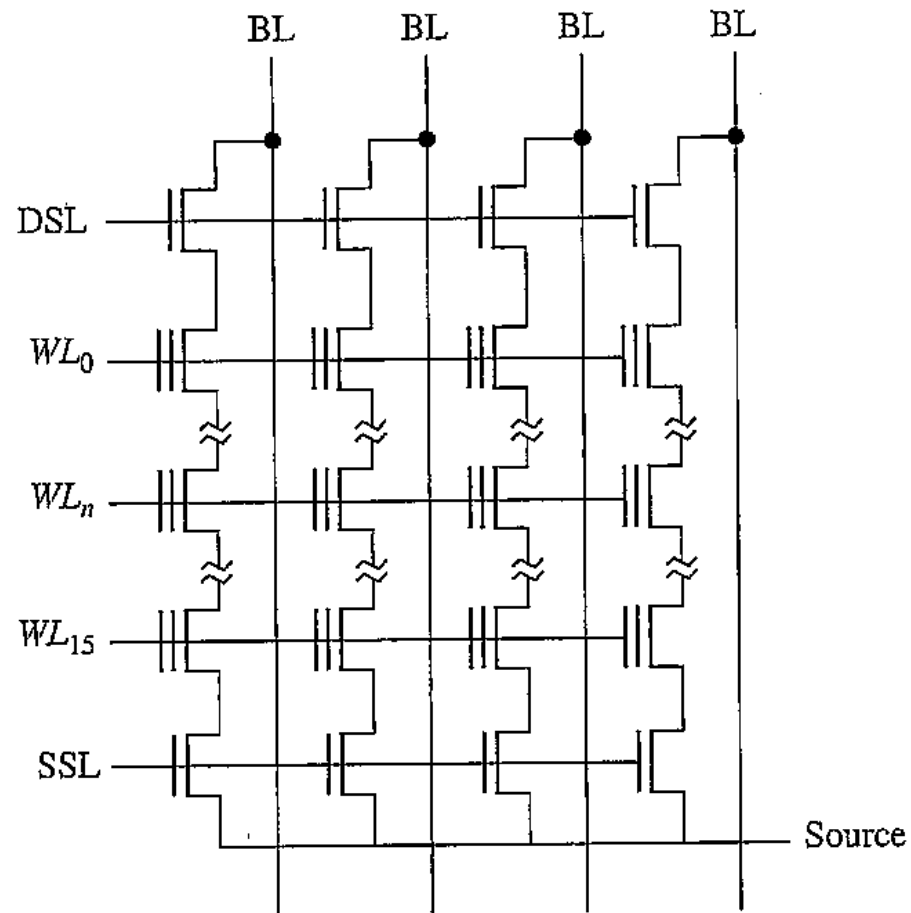

Issues

Read / Write Endurance

- $> 10^5$ Operations

Redundancy for improved yield

Multi-Bit Cell Architectures – in common practice today!