

ECE 445 Design Project – 5-bit Carry-Ripple Adder

Part A: Design an inverter, ring oscillator, and digital buffer, using the 65nm CMOS process, that meet the following specifications.

1. Limitations

(a) Temperature = 27 C.

(b) $V_{DD} \leq 1.2$ V.

2. 1X Inverter

(a) $L_n = L_p = 65$ nm, $W_n \geq 100$ nm, $W_p \geq 100$ nm.

(b) Switching voltage (V_S) $\approx V_{DD}/2$.

(c) $NML \approx NMH$.

(d) $t_{PHL} \approx t_{PLH}$.

(e) t_P minimum.

3. Ring Oscillator and Digital Buffer

(a) Oscillation frequency $f = 3$ GHz $\pm 3\%$.

(b) Digital buffer allows the Ring Oscillator to drive a load capacitance of 1 pF.

Analyze the DC and time response of the inverter. Simulate the time response of the ring oscillator when driving a 1 pF load capacitor. Simulate the average power consumed by the ring oscillator and the digital buffer when driving a 1 pF load capacitor. Submit a short (less than 5 page) report describing the design and simulation results.

Tentative due date: 20 February 2024.

Part B: Design a 5-bit carry-ripple adder, configured as a counter, using the 65nm CMOS process that meets the following specifications:

1. Performance and Limitations:

- (a) The 5-bit counter increments by “1” each clock cycle.
- (b) Clock frequency = 3 GHz \pm 3% generated by the ring oscillator designed in Part A.
- (c) Temperature = 27 C.
- (d) $L_n = L_p = 65$ nm, $W_n \geq 100$ nm, $W_p \geq 100$ nm.
- (e) Average power consumption = minimum. The design with the lowest average power consumption wins!!!

2. Inputs (3):

- (a) Single ground node labeled: “gnd”.
- (b) Single DC voltage source $V_{\text{sup}} \leq 1.2$ V.
- (c) Clock generated by the ring oscillator designed in Part A. The output of the ring oscillator should be labeled “clk”.

3. Outputs (4):

- (a) Most significant bit - labeled as “s4”.
- (b) Next most significant bit - labeled as “s3”.
- (c) Next most significant bit - labeled as “s2”.
- (d) Next most significant bit - labeled as “s1”,
- (e) Least significant bit - labeled as “s0”.

Final Report: Submit a final report, similar to an ECE 342 lab report, describing the design and simulation results of the 5-bit carry ripple adder.

Tentative due date: 25 April 2024.