

ECE 209 — Final Exam

Estimated time for completion: <2 hours
16 December 2014

Rules of the Exam

Rule 1: The examination period begins at 12:15am on Tuesday 16 December 2014 and ends at 2:15pm on Tuesday 16 December 2014.

Rule 2: There are four problems, each problem has equal weight.


Rule 3: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes and a calculator.

Rule 4: Show all work and state all assumptions.

Name

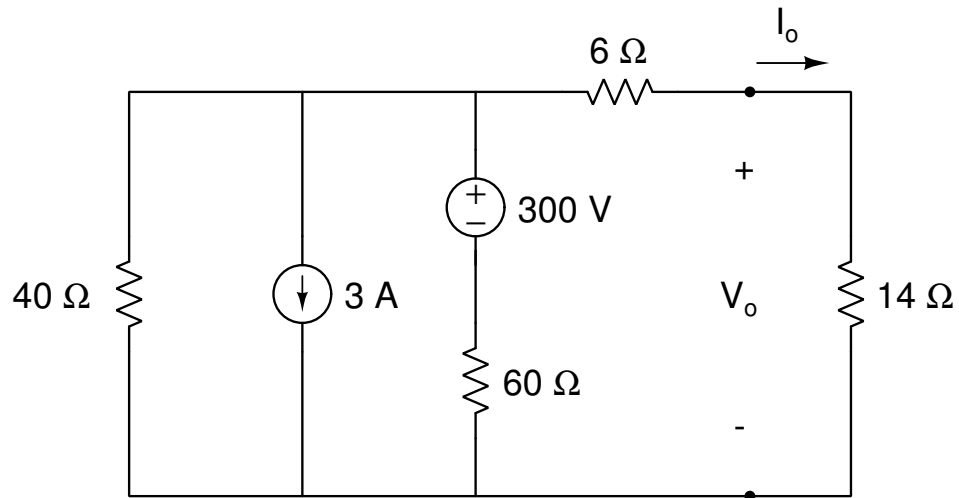Problem 1

Determine the values of V_o and I_o in the circuit below:




$V_o =$ _____

$I_o =$ _____


Problem 2

Determine the Thévenin equivalent circuit with respect to terminals A and B in the circuit below.

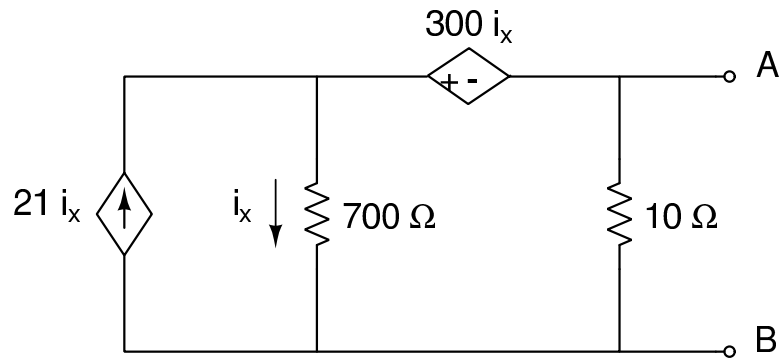

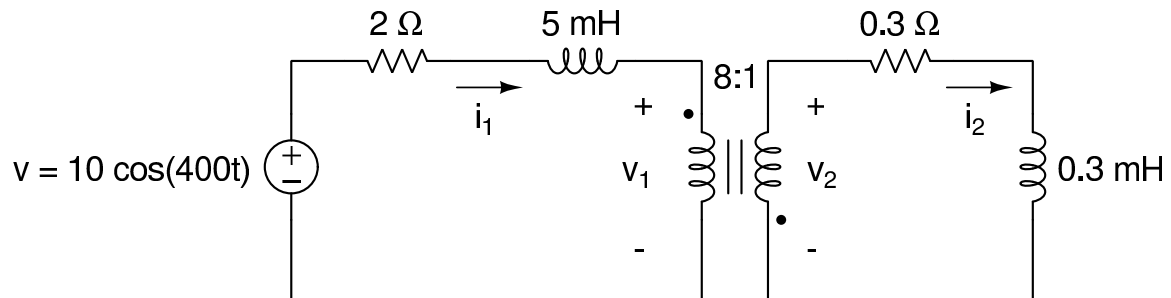Problem 3

Find the steady-state expressions for $i_1(t)$, $i_2(t)$, $v_1(t)$, and $v_2(t)$ in the circuit below. Assume the transformer is ideal.



$$i_1(t) = \underline{\hspace{4cm}}$$


$$i_2(t) = \underline{\hspace{4cm}}$$

$$v_1(t) = \underline{\hspace{4cm}}$$

$$v_2(t) = \underline{\hspace{4cm}}$$

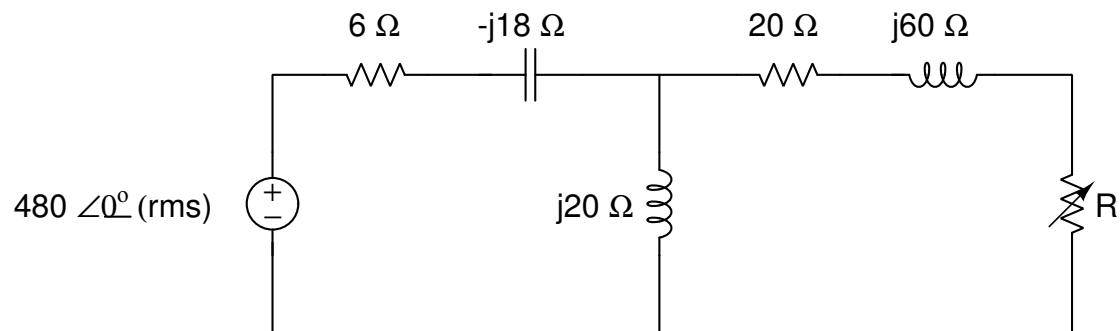Problem 4

The variable resistor R in the circuit below is adjusted until the average power it dissipates is a maximum.



Part A: What is R ? _____

Part B: What is the maximum average power dissipated by R ? _____