

ECE 209 — Exam # 3

Estimated time for completion: <75 minutes
24 November 2015

Rules of the Exam

Rule 1: The examination period begins at 11:00pm on Tuesday 24 November 2015 and ends at 12:15pm on Tuesday 24 November 2015.

Rule 2: There are three problems.


Rule 3: Show all work and state all assumptions. Make sure to include the units along with a numerical answer.

Rule 4: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes. You may use a calculator.

Name

Problem 1 (40 points)

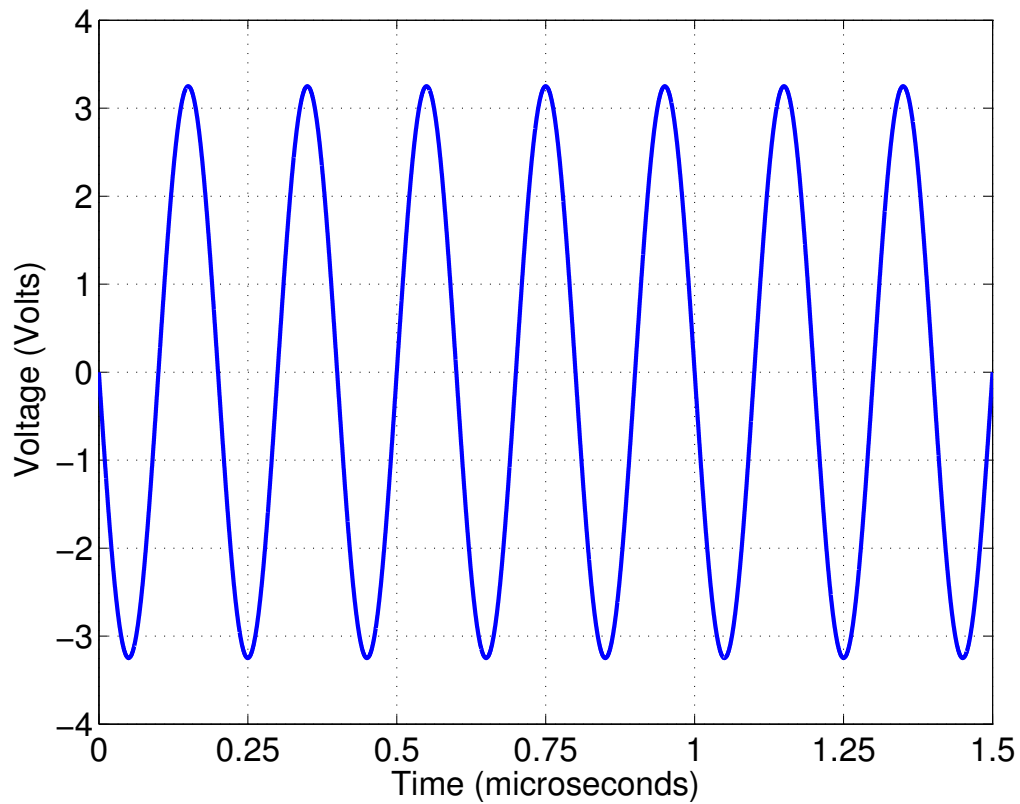Part A: Consider the voltage waveform shown below:



What is V_{RMS} ? _____

What is the peak-to-peak voltage? _____


What is the frequency in Hz? _____

What is the equation for $v(t)$? _____

What is \mathbf{V} the Phasor representation of $v(t)$ _____

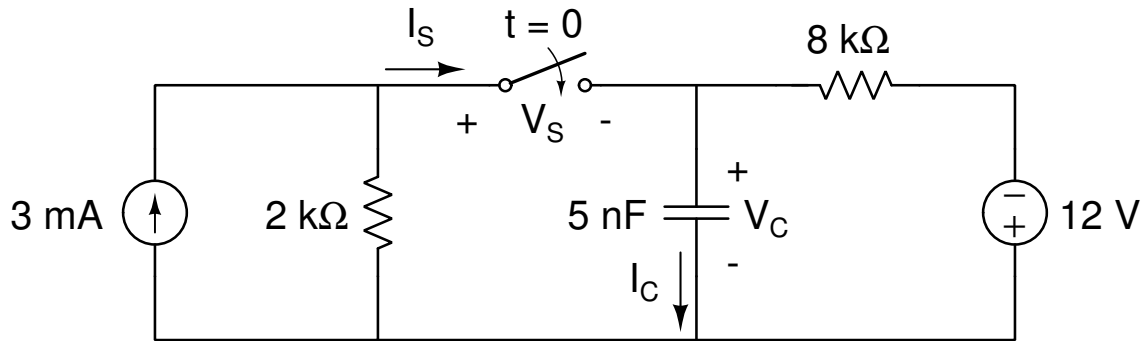Problem 2 (40 points)

In the circuit below, the switch has been open for a very long time and closes at $t = 0$.




Complete the table below:

	$t = 0^-$	$t = 0^+$	$t = 5 \mu\text{s}$	$t = \infty$
V_c				
I_c				
V_s				
I_s				

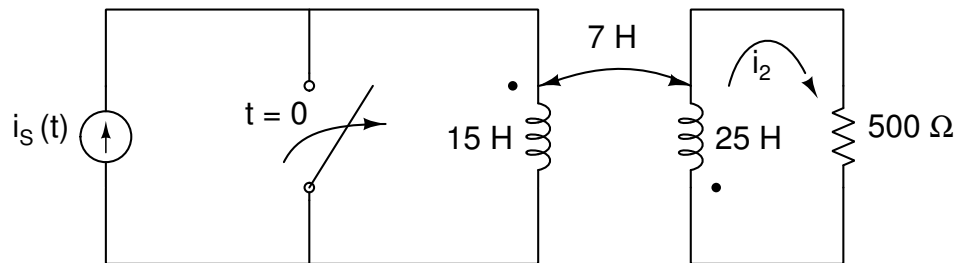Problem 3 (20 points)

In the circuit below, the switch has been closed for a very long time and opens at $t = 0$. There is no energy stored in the circuit at the time the switch opens.



What is $i_2(0^-)$ _____

What is $i_2(0^+)$ _____

For $t \geq 0$, write the differential equation that governs the behavior of $i_2(t)$ _____
(Note: you do not need to solve the equation)

Name: _____

Name: _____

Name: _____