

11/16/16

①

Exam 3 - Fall 2015 (24 November 2015)

Problem 1: Part A

$$V_{\text{rms}} = 2.3 \text{ V}, \quad V_{\text{peak-to-peak}} = 6.5 \text{ V}, \quad f = 5 \text{ MHz}$$

$$v(t) = 3.25 \cos(10^7 \pi t + 90^\circ) \text{ V}$$

$$\bar{V} = 3.25 \angle 90^\circ$$

Problem 1: Part B

$$1 + j2.73 \text{ or } 2.9 \angle 69.9^\circ$$

$$4.39 - j0.122 \text{ or } 4.39 \angle -659^\circ$$

Problem 1: Part C $1600 - j3200 \text{ or } 3578 \angle -63.4^\circ$

Problem 2:

-12 V	-12 V	-5.31 V	2.4 V
0 A	9 mA	4.82 mA	0 A
18 V	0 V	0 V	0 V
0 A	9 mA	5.65 mA	1.8 mA

Problem 3:

$$0 \text{ A}, 0 \text{ A}, \quad \text{KCL @ } i_2: 500i_2 + 25 \frac{di_2}{dt} + 7 \frac{di_2}{dt} = 0$$

Exam 3 - Spring 2015 (3 April 2015)Problem 2: $T = 526 \text{ ns}, \quad T = 30 \text{ ms}$

Problem 3:

0	6.75 mA	0
1 mA	-0.6875 mA	1 mA
-120 V	-120 V	150 V
150 V	-103.125 V	150 V

$$v_c(t) = 150 - 270 e^{-1000t} \text{ V}$$


$$i_c(t) = 6.75 \times 10^{-3} e^{-1000t} \text{ A}$$

Extra Credit: 10 μJ , 40 μJ , 24 mW

Exam 4 - Spring 2015 (22 April 2015)

Problem 1: $2.5V, 2ms, 1.77V, 2.5 \cos(1000\pi t - 60^\circ)$
 $15 \angle 20^\circ \text{ mV}, 25 \angle -25^\circ \text{ A}$
 $12 \cos(50,000\pi t - 40^\circ), 2 \cos(50,000\pi t + 65^\circ)$
 $6.41 - j1.6 \text{ or } 6.6 \angle -13.9^\circ$
 $1.39 + j7.88 \text{ or } 8 \angle 80^\circ$

Problem 2a:

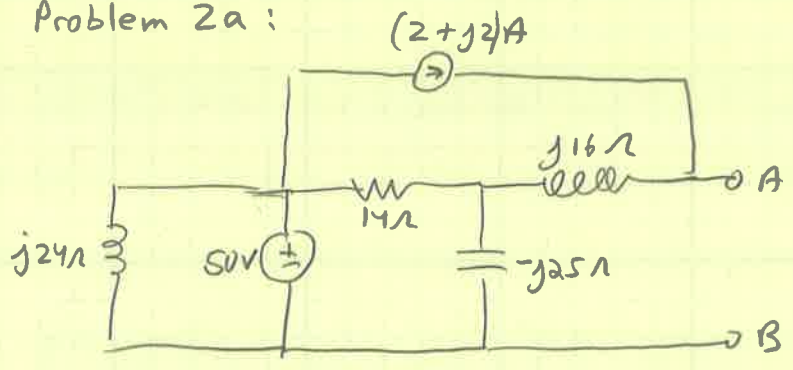

Exam 3 - Fall 2014 (25 November 2014)

Problem 1: $i_2(0^-) = i_2(0^+) = 0 \text{ A}$
 KVL @ i_2 : $i_2 R_0 + 25 \frac{di_2}{dt} - 15 \frac{di_1}{dt} = 0$

Problem 2:

0 A	0.4667 A
0.5833 A	0.5833 A
0.1167 A	0 A
0 V	-7 V
7 V	0 V

Problem 3:

$$V_C(t) = 5 - 5e^{-40(t - 5 \times 10^{-3})} \text{ V}$$

$$V_R(t) = 5e^{-40(t - 5 \times 10^{-3})} \text{ V}$$

Problem 4:

$$4 \angle 45^\circ \text{ V}$$

$$25 \angle -10^\circ \text{ mA}$$

$$6 \cos (10,000 \pi t + 40^\circ) \cdot V$$

$$21 \cos (10,000 \pi t + 65^\circ) A$$

$$6.414 + j1.414 \quad \text{or} \quad 6.568 \angle 12.43^\circ$$

$$10 \angle 70^\circ \quad \text{or} \quad 3.42 + j9.397$$

$$12 - j32 \quad \text{or} \quad 34.18 \angle -69.44^\circ$$

Problem 5:

$$\bar{V}_g = 9 - j15 V$$

$$\bar{I}_g = -j3 A$$

Exam 3 - Spring 2013 (5 April 2013)

Problem 1:

$$i_2 R_0 + 40 \frac{di_2}{dt} + 5 \frac{di_2}{dt} = 0$$

$$i_2(t) = 32 e^{-400t} + 5 \frac{di_2}{dt} \quad V$$

Problem 2:

$$i_1(0^+) = 4.67 A, \quad i_1(\infty) = 10.5 A$$

$$i_1(t) = 10.5 - 5.83 e^{-6000t}$$

Problem 3:

$$v_1(0^- \mu s) = -20 V \quad v_2(0^- \mu s) = 0 V$$

$$v_1(0^+ \mu s) = 0 V \quad v_2(0^+ \mu s) = 0 V$$

$$v_1(5 \mu s) = -1.21 V \quad v_2(5 \mu s) = 0 V$$

$$v_1(15 \mu s) = -2.92 V \quad v_2(15 \mu s) = -32.9 V$$

Exam 4 - Spring 2013 (26 April 2013)

Problem 2:

$$\bar{V}_g = 9 - j15 \text{ V} \quad \text{or} \quad 17.5 \angle -59^\circ \text{ V}$$

$$\bar{I}_g = -j3 \text{ A} \quad \text{or} \quad 3 \angle -90^\circ \text{ A}$$

Extra Credit (switch closes at $t = 10 \text{ ms}$)

$$i_1(10^- \text{ms}) = 0 \text{ A}$$

$$i_1(10^+ \text{ms}) = \frac{14}{3} \text{ A}$$