

ECE 209 — Exam # 1

Estimated time for completion: <1.25 hour
28 September 2017

Rules of the Exam

Rule 1: The examination period begins at 9:30am on Thursday 28 September 2017 and ends at 10:45pm on Thursday 28 September 2017.

Rule 2: There are four problems.

Rule 3: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes and a calculator.

Rule 4: To receive full credit for an answer include the units along with the numerical answer.


Rule 5: Show all work - answers without supporting work will not receive credit.

Answer Key

Name

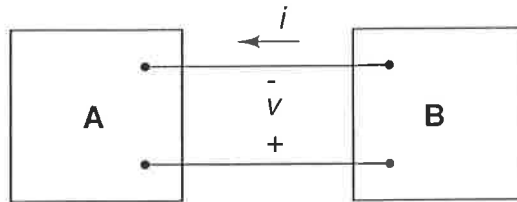Problem 1 (20 points)

Two electric circuits, represented by boxes **A** and **B**, are connected as shown in the figure below. The reference direction for the current i and the reference polarity of the voltage v are also shown.




For each set of values of i and v in the table below, calculate the value of the power associated with circuit **A** and circuit **B**.

Condition	i	v	$P = -v \times i$	$P = v \times i$
			Power for Circuit A	Power for Circuit B
1	-10 A	5 V	50 W	-50 W
2	5 A	2 V	-10 W	10 W
3	12 A	-2 V	24 W	-24 W

Problem 2 (20 points)

Consider the circuit below:

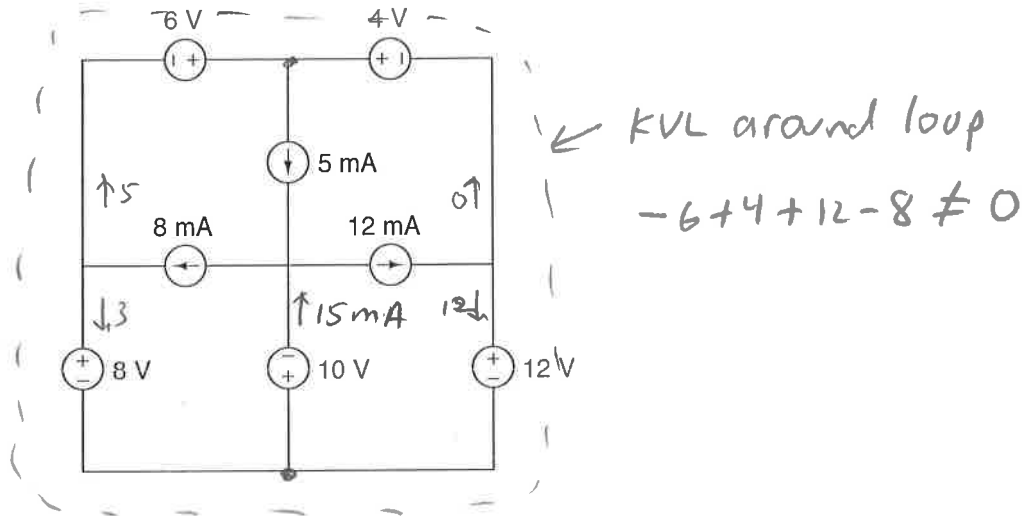

Is the interconnection valid (yes/no)? _____

If the interconnection is valid, identify the voltage and current sources that generate power by circling them in the figure above.




If the circuit is not valid, explain why:

Problem 3 (30 points)

Consider the three series and parallel resistor combinations below:

B
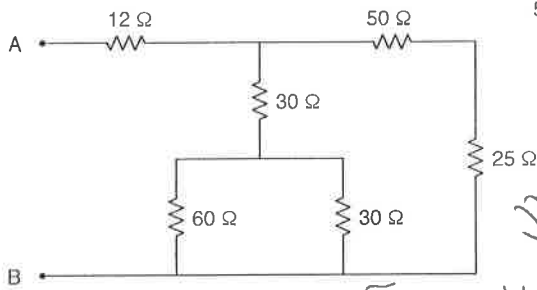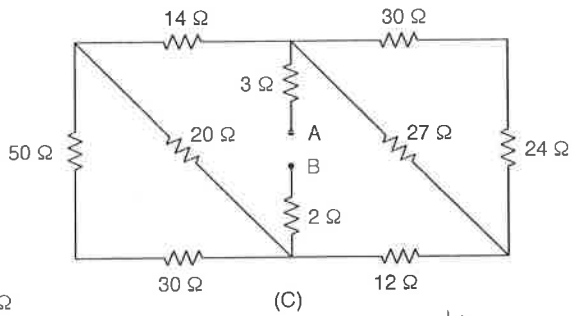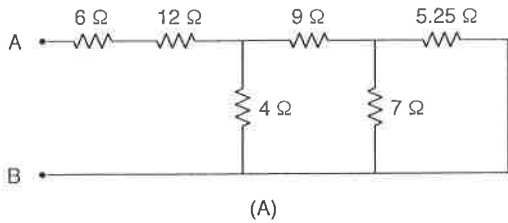
$$R_{AB} = \left[\left((5.25 \parallel 7) + 9 \right) \parallel 4 \right] + 18 = 21 \Omega$$






$$R_{AB} = \left[(50 + 25) \parallel (30 + 30 \parallel 60) \right] + 12 = 30 + 12 = 42 \Omega$$

For circuits (A), (B), and (C) calculate R_{ab} , the equivalent resistance between terminals A and B:

R_{ab} for circuit (A): 21 Ω


R_{ab} for circuit (B): 42 Ω

R_{ab} for circuit (C): 20 Ω

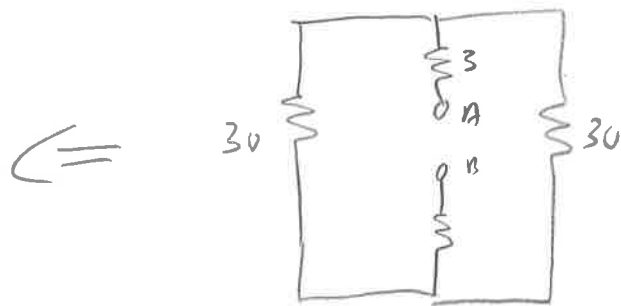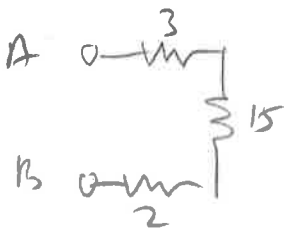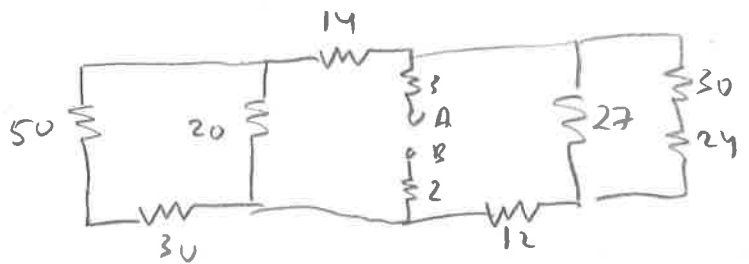

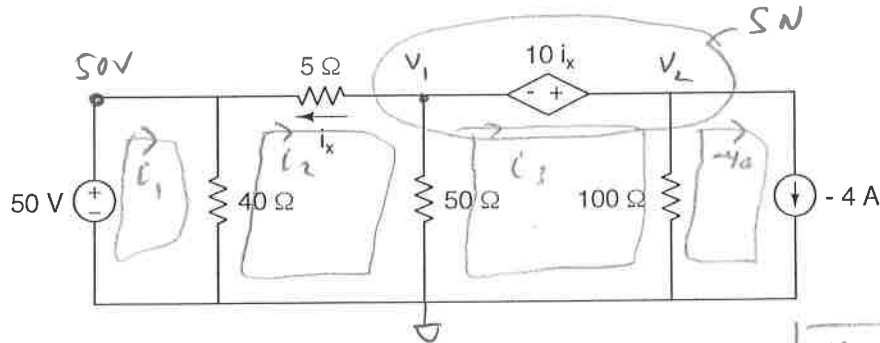Problem 4 (30 points)

In the circuit shown below, calculate the power associated with each circuit component, the total power generated and the total power dissipated (or absorbed).



Power associated with the 50 V independent source? 37.5 W

Power associated with the -4 A independent source? -320 W

Power associated with the $10i_x$ dependent voltage source? 64 W

Power associated with the 40Ω resistor? 62.5 W

Power associated with the 5Ω resistor? 20 W

Power associated with the 50Ω resistor? 72 W

Power associated with the 100Ω resistor? 64 W

How much power is generated in the circuit? 320 W

How much power is dissipated or absorbed in the circuit? 320 W

NODAL ANALYSIS

$$V_2 - V_1 = 10i_x$$

$$\frac{V_1 - 50}{5} + \frac{V_1}{50} + \frac{V_2}{100} - 4 = 0$$

$$i_x = \frac{V_1 - 50}{5}$$

Solve $V_1 = 60V$

$V_2 = 80V$

$i_x = 2A$

Mesh Analysis

$$40(i_1 - i_2) - 50 = 0$$

$$5i_2 + 50(i_2 - i_3) + 40(i_2 - i_1) = 0$$

$$-10i_x + 100(i_3 + 4)$$

$$+ 50(i_3 - i_2) = 0$$

$$i_x = -i_2$$

Solve

$$i_1 = -3/4 A$$

$$i_2 = -i_x = -2 A$$

$$i_3 = -16/5 A$$

(Blank Page)

(Blank Page)