

ECE 209 — Exam # 2

Estimated time for completion: <1.25 hour
24 October 2017

Rules of the Exam

Rule 1: The examination period begins at 9:30am on Tuesday 24 October 2017 and ends at 10:45pm on Tuesday 24 October 2017.

Rule 2: There are four problems.

Rule 3: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes and a calculator.

Rule 4: Do not leave the room until you have completed the exam.

Rule 5: To receive full credit for an answer include the units along with the numerical answer.


Rule 6: Show all work - answers without supporting work will not receive credit.

Answer Key

Name

Problem 1 (30 points)

Consider the circuit below:

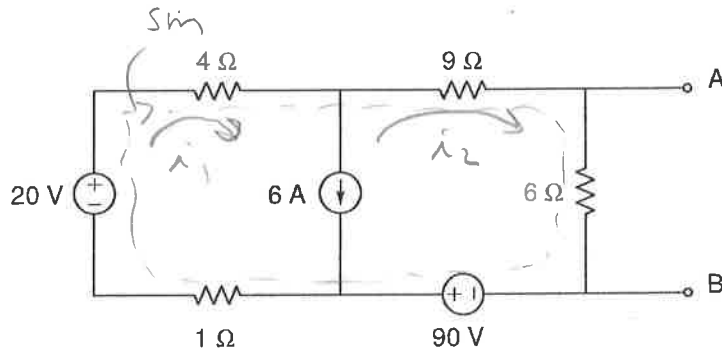

Part A: Draw the Thévenin Equivalent Circuit with respect to terminals A and B.

Supermesh: $4i_1 + 9i_2 + 6i_2 - 90 + i_1 - 20 = 0$

$i_1 - i_2 = 6 \Rightarrow i_1 = 6 + i_2$

$5i_1 + 15i_2 = 110$

$30 + 5i_2 + 15i_2 = 110$


$20i_2 = 80$

$i_2 = 4A$

$V_{AB} = 6i_2 = 24V$

$R_{AB} = 6 \parallel 14$
 $= 4.2\Omega$

$P = \frac{24^2}{4 \times 4.2}$

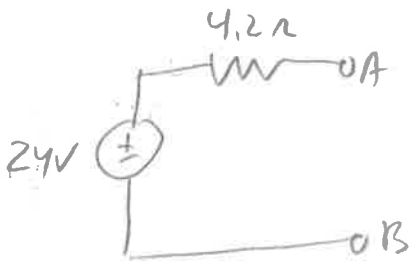


Part B: If a load resistor R_L is placed between terminals A and B:

What value of R_L produces maximum power transfer to the load? 4.2Ω

What is the maximum power dissipated by R_L ? 34.3 W

Problem 2 (20 points)

Consider the circuit below:

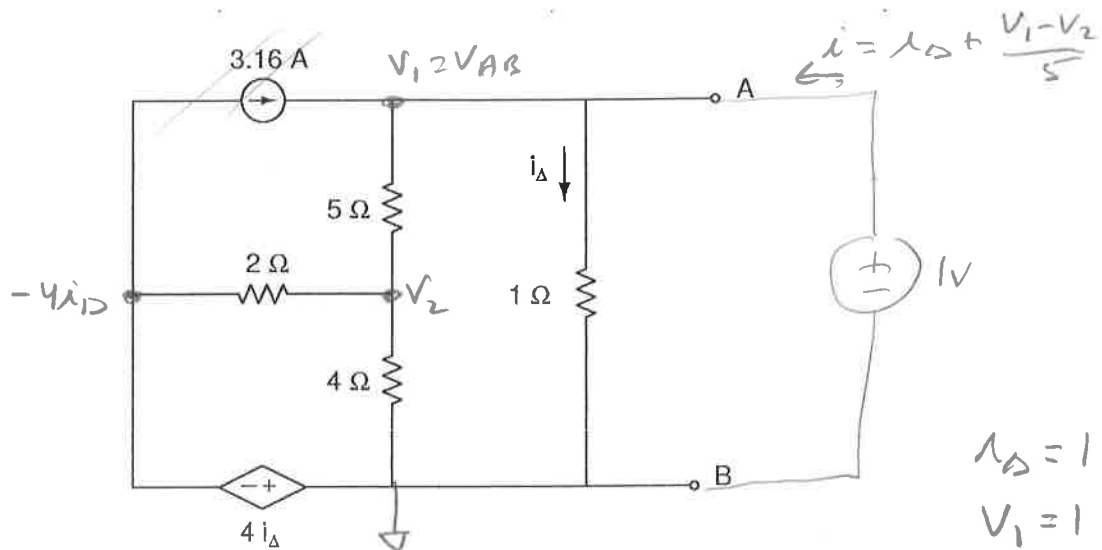

Draw the Thévenin Equivalent Circuit with respect to terminals A and B.

$$\text{KCL @ } V_1: -3.16 + \frac{V_1 - V_2}{5} + V_1 = 0$$


$$\text{KCL @ } V_2: \frac{V_2 + 4i_\Delta}{2} + \frac{V_2}{4} + \frac{V_2 - V_1}{5} = 0$$

$$\text{Constraint: } i_\Delta = V_1$$

$$V_1 = 2.0 \text{ V}$$

$$V_2 = -3.8 \text{ V}$$

$$V_{AB} = 2.0 \text{ V}$$

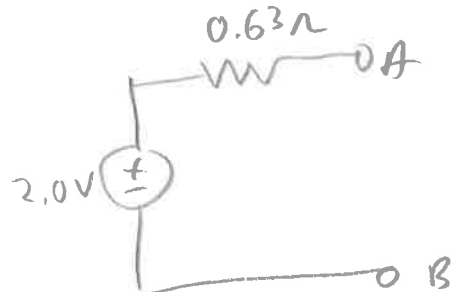

$$i_\Delta = 1$$

$$V_1 = 1$$

$$\text{KCL @ } V_2:$$

$$\frac{V_2}{4} + \frac{V_2 + 4i_\Delta}{2} + \frac{V_2 - 1}{5} = 0$$





$$V_2 = \frac{-36}{19}$$

$$i = 1 + \frac{V_1 - V_2}{5} = \frac{30}{19} \text{ A}$$

$$R_{Th} = 0.63 \Omega$$

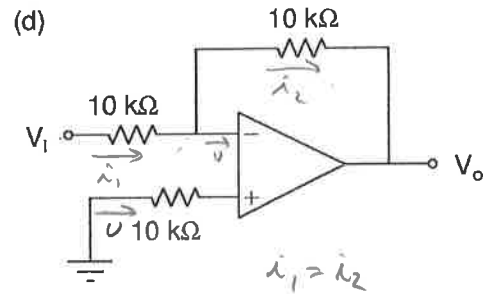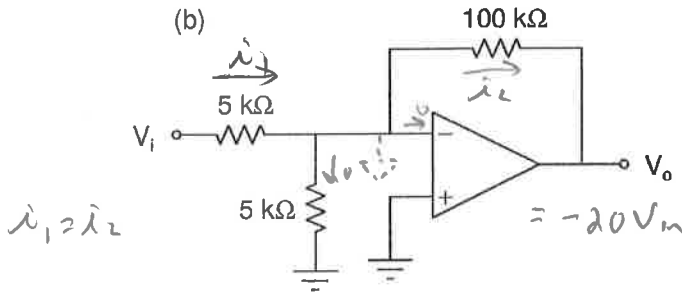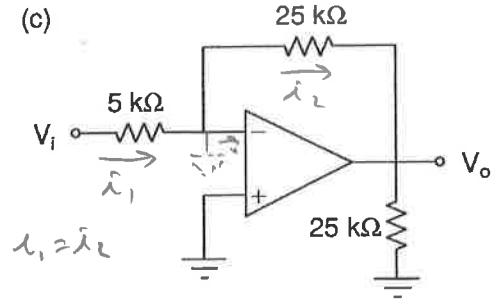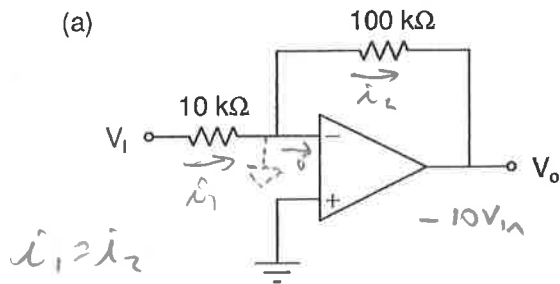Problem 3 (20 points)

The OpAmp in the circuits below is ideal. For each of the circuits, find the voltage gain, V_o / V_i .



Circuit (a) Voltage Gain = -10


Circuit (b) Voltage Gain = -20

Circuit (c) Voltage Gain = -5


Circuit (d) Voltage Gain = -1

Problem 4 (30 points)

Consider the circuits below:

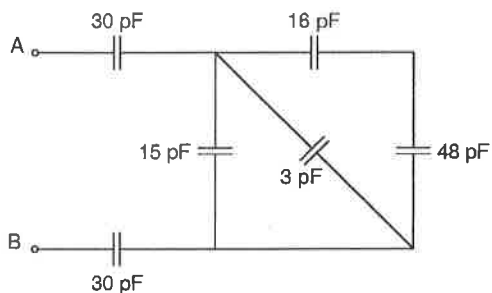

Circuit A

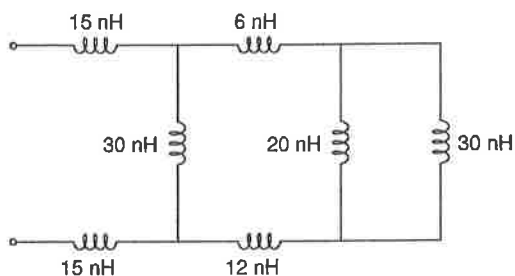

Circuit B

Circuit A: What is the equivalent capacitance between terminals A and B? 10 pF

Circuit B: What is the equivalent inductance between terminals A and B? 45 nH

(A)

$$48 + 16 = 12$$

$$12 || 3 || 15 = 30$$

$$30 + 30 + 30 = 10$$

(B)

$$30 || 20 = 12$$

$$12 + 12 + 6 = 30$$

$$30 || 30 = 15$$

$$15 + 15 + 15$$