

## ECE 210 — Exam # 3

Estimated time for completion: <1 hour  
5 April 2013

### Rules of the Exam

**Rule 1:** The examination period begins at 1:10pm on Friday 5 April 2013 and ends at 2:00pm on Friday 5 April 2013.

**Rule 2:** There are three problems.


**Rule 3:** The exam is closed book and closed notes but you may use a 4" x 6" sheet of paper with notes during the exam. You may use a calculator.

---

Name

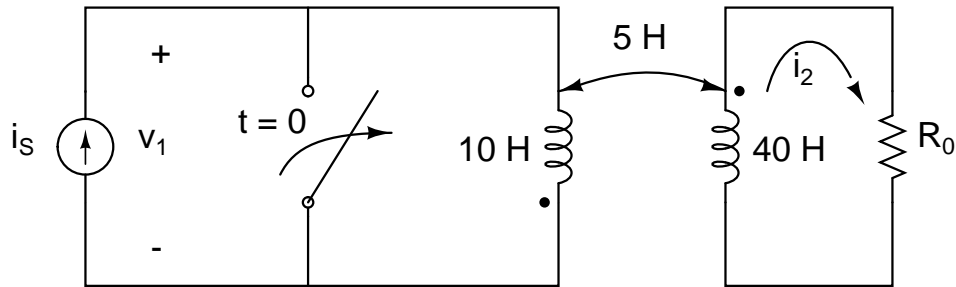**Problem 1.** (5 pts.) In the circuit below, the switch has been closed for a very long time and there is no energy stored in the circuit before the switch opens.


The current source  $i_s(t) = 8 - 8e^{-400t}$  mA



Use KVL to derive an equation for  $i_2(t)$  for  $t \geq 0$ . (You do not need to solve the equation.)

Find the expression for the voltage  $v_1(t)$  for  $t \geq 0$ .

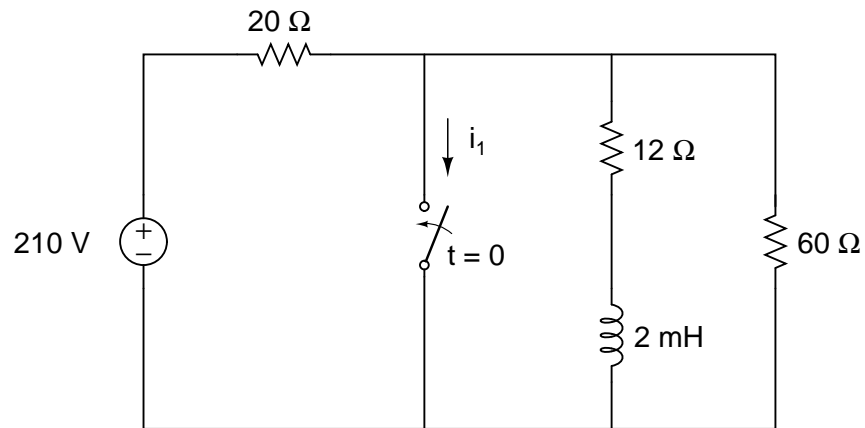**Problem 2.** (5 pts.) In the circuit below, the switch has been open for a very long time and closes at  $t = 0$ .




What is  $i_1(0^+)$ ? \_\_\_\_\_

What is  $i_1(\infty)$ ? \_\_\_\_\_

Write an equation for  $i_1(t)$  for  $t \geq 0^+$ ?

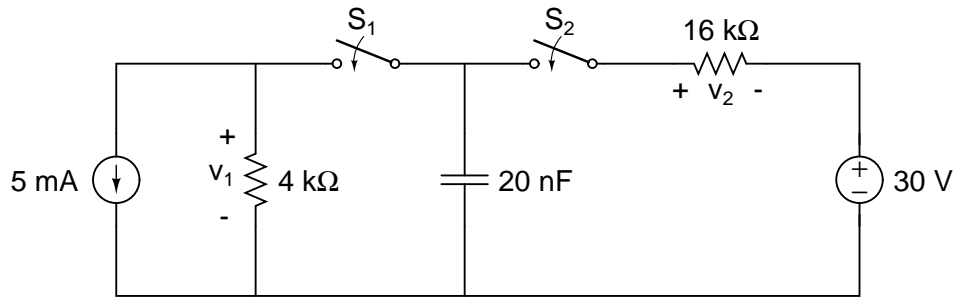**Problem 3.** (10 pts.) Consider the circuit below. For  $t < 0$ , both switches are open and there is no energy stored in the capacitor. At  $t = 0$ , switch  $S_1$  closes; at  $t = 10\mu\text{s}$ , switch  $S_2$  closes.



What is  $v_1(0^- \mu\text{s})$ ? \_\_\_\_\_

What is  $v_2(0^- \mu\text{s})$ ? \_\_\_\_\_

What is  $v_1(0^+ \mu\text{s})$ ? \_\_\_\_\_

What is  $v_2(0^+ \mu\text{s})$ ? \_\_\_\_\_

What is  $v_1(5\mu\text{s})$ ? \_\_\_\_\_

What is  $v_2(5\mu\text{s})$ ? \_\_\_\_\_

What is  $v_1(15\mu\text{s})$ ? \_\_\_\_\_

What is  $v_2(15\mu\text{s})$ ? \_\_\_\_\_

Extra Page 1

Extra Page 2

Extra Page 3